
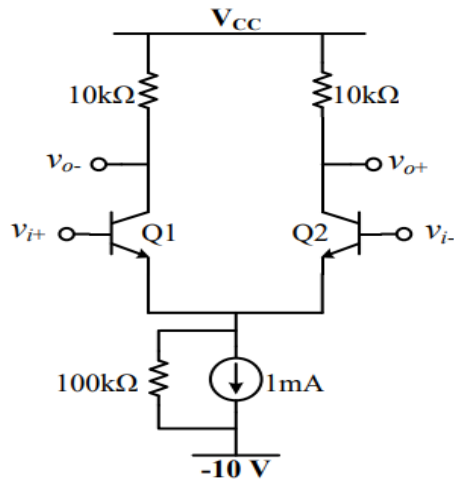


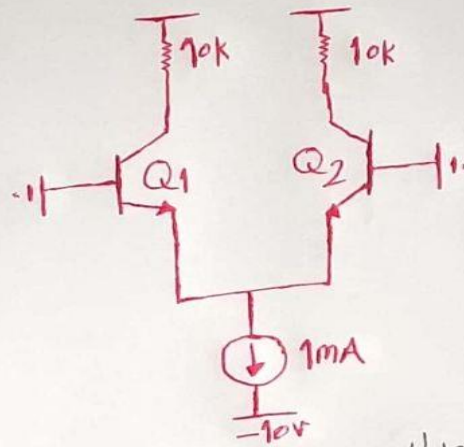1- Determine v_{o-} , v_{o+} , and $v_{od} = (v_{o+} - v_{o-})$ for the following circuit.



$$\begin{cases} V_A = \infty \\ V_T = 25mV \\ \beta = 100 \\ V_{i+} = +0.5 \times V_{id} \\ V_{i-} = -0.5 \times V_{id} \\ V_{id} = 10 \sin 10t \text{ mV} \end{cases}$$

DC)




$$i_{C1} = i_{C2} = \frac{1}{2} \text{ mA}$$

$$g_{m1,2} = 20 \text{ mS}$$

$$r_{\pi 1,2} = 5 \text{ k}\Omega$$

$$r_{o1,2} = \infty$$

ac)

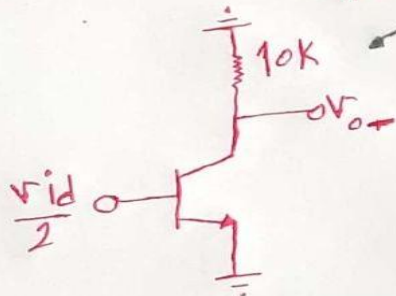

$$\frac{v_{o-}}{v_{id}} = -\frac{1}{2} g_m R_C = -100$$

$$\frac{v_{o+}}{v_{id}} = \frac{1}{2} g_m R_C = +100$$

$$v_{id} = 10 \text{ mV} \sin(10t)$$


$$v_{o-} = -100 \text{ mV} \sin(10t)$$

$$v_{o+} = +100 \text{ mV} \sin(10t)$$

$$v_{o+} - v_{o-} = +2 \text{ V} \sin(10t)$$

2- Calculate the voltage gain ($A_v = \frac{v_{out}}{v_{in}}$) of the circuit shown below using the following methods:

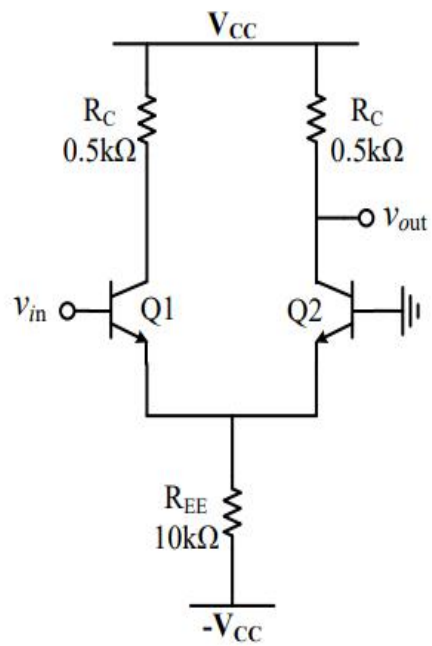- Direct analysis.
- Half-circuit analysis (break the input voltage to a differential term and a common-mode one, compute the differential and common-mode output voltages and add the results together).




$$\begin{cases} I_{C1} = I_{C2} = 1\text{mA} \\ \beta = 100 \\ V_A = \infty \\ V_T = 25\text{mV} \end{cases}$$

$$i_{C1} = i_{C2} = 1\text{mA} \rightarrow g_{m1,2} = 40\text{mA/V}$$

$$r_{\pi 1,2} = 2.5\text{k}\Omega$$

$$r_{o1,2} = \infty$$

$$A_v = ?^{-2}$$

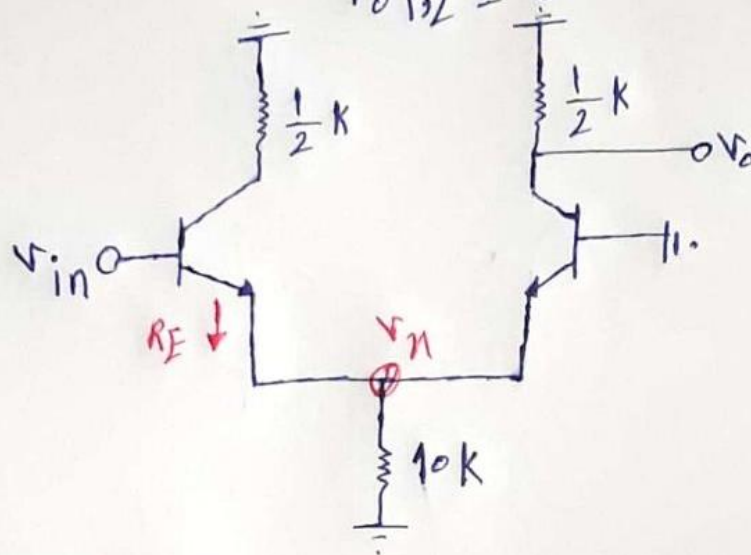

$$A_v = \frac{v_o}{v_{in}} \times \frac{v_n}{v_{in}}$$


$$\frac{v_o}{v_n} = +g_m R_C = +40 \times \frac{1}{2} = +20$$

$$\frac{v_n}{v_{in}} = \frac{R_E}{R_E + \frac{1}{g_m}}$$

$$R_E = 10\text{k}\Omega \parallel \frac{1}{g_m} = 0.02493765$$

$$\frac{v_n}{v_{in}} = 0.49937572$$


$$A_v = \frac{v_o}{v_{in}} = 9.98751$$

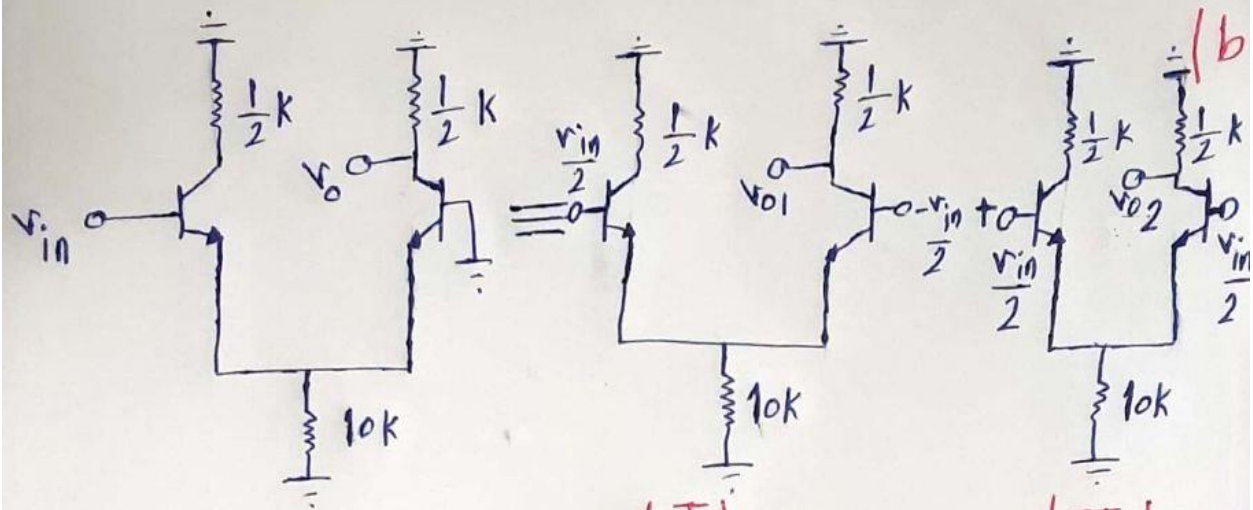

(I)
تفاضلی

(II)
مستمر

$$V_o = V_{o1} + V_{o2}$$

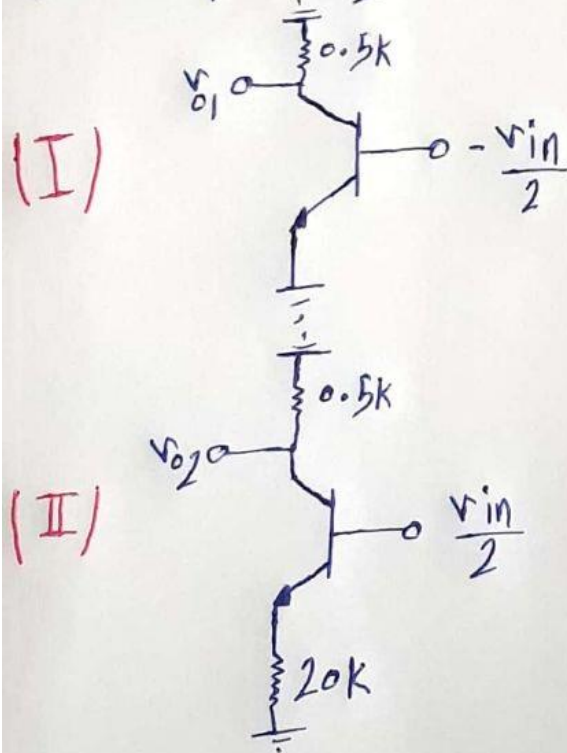

(I)

(II)

$$\frac{V_{o1}}{-v_{in}/2} = -g_m R_C \Rightarrow V_{o1} = \frac{1}{2} g_m R_C v_{in}$$

$$V_{o1} = 10 v_{in}$$


$$\frac{V_{o2}}{v_{in}/2} = \frac{-R_C}{R_E + \frac{1}{g_m}} \Rightarrow$$

$$\frac{V_{o2}}{v_{in}} = \frac{1}{2} \frac{-0.5}{20 + \frac{1}{40}} = -0.012484$$


$$V_{o2} = -0.012484 v_{in}$$

$$V_o = V_{o1} + V_{o2} \Rightarrow V_o = 9.98751 v_{in} \rightarrow A_v = 9.98751$$

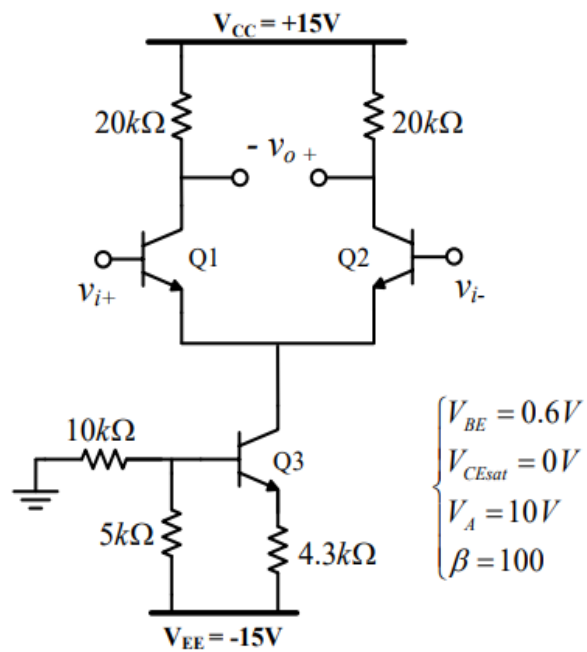- 3- In the circuit shown below, the transistors are the same. Neglect β effect in DC analysis.
- Calculate the input DC common-mode voltage range and the output swing.
 - Determine CMRR.



(3)

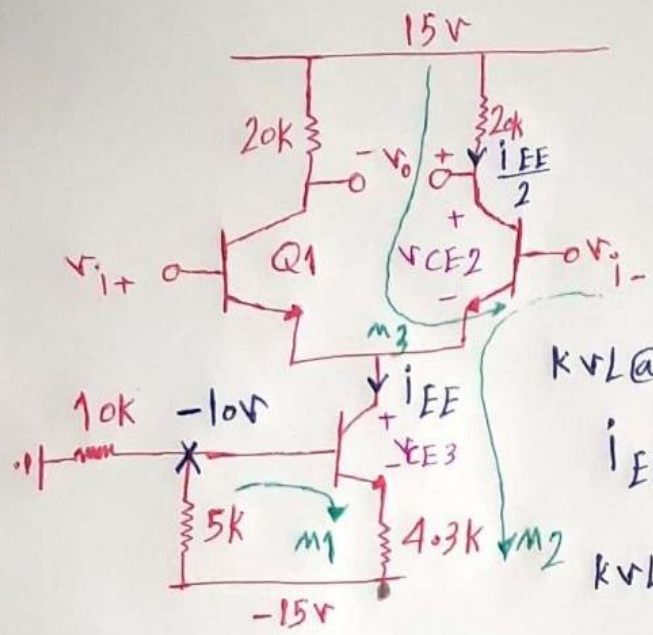

$$V_{BE} = 0.6V$$

$$V_{CS} = 0V$$

$$V_A = 10V$$

$$\beta = 100$$

$$KVL @ M_1: +10 + 6 + 4.3 I_{EE} - 15 = 0$$

$$I_{EE} \approx 1mA$$

$$KVL @ M_2: -V_{in,dc} + 0.6 + V_{CE3} + 4.3 I_{EE} - 15 = 0$$

$$V_{CE3} = V_{in,dc} + 10.1 \gg 0 \rightarrow V_{in,dc} \gg -10.1 \quad (I)$$

$$KVL @ M_3: -15 + \frac{20 \times I_{EE}}{2} + V_{CE2} - 0.6 + V_{in,dc} = 0 \rightarrow$$

$$V_{CE2} = -V_{in,dc} + 5.6 \gg 0 \rightarrow V_{in,dc} \leq 5.6V \quad (II)$$


$$\underline{I \sim II} \rightarrow -10.1 \ll V_{in,dc} \leq 5.6V$$

حاسبه $\{V_o\}$ swing

$$V_{Q,dc} = V_{O-dc} = V_{CC} - R_C \frac{I_{EE}}{2}$$


$$V_{i+} \rightarrow Q_1: off \rightarrow V_{O-} = V_{CC} = 15V$$
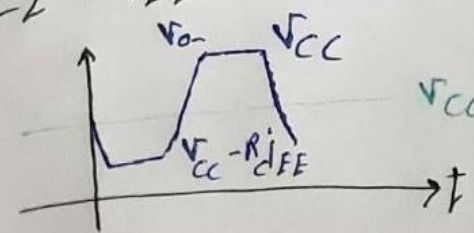
$$I_{C2} = I_{EE} \rightarrow V_{O+} = V_{CC} - R_C I_{EE}$$



$$V_{CC} - R_C \frac{I_{EE}}{2}$$
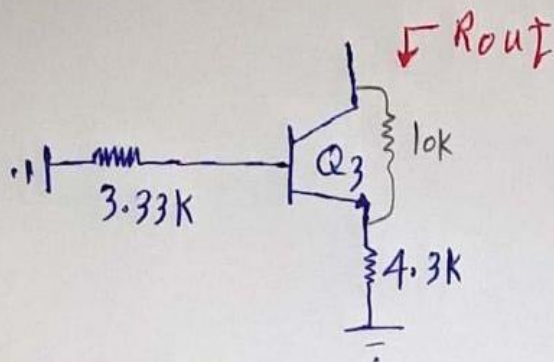
$$swing\{V_o\} = \frac{2R_C I_{EE}}{2} = 20V$$



$$CMRR = \frac{A_d}{A_{cm}} = ? \quad |b$$

$$g_{m1} = g_{m2} = 20 \text{ mS}$$

$$V_{\pi 1,2} = 5 \text{ k}\Omega$$

$$r_{o1,2} = 20 \text{ k}\Omega$$


$$r_{o3} = \frac{10}{1} = 10 \text{ k}\Omega$$

$$g_{m3} = 40 \text{ mS}$$

$$r_{\pi 3} = 2.5 \text{ k}\Omega$$


$$R_{out} = r_o \left(1 + \frac{\beta R_E}{R_E + r_{\pi} + R_B} \right)$$
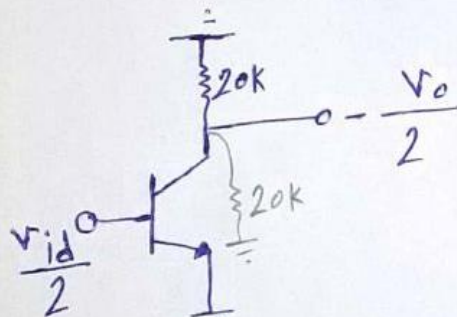
$$R_{out} = 10 \left(1 + \frac{100 \times 4.3}{4.3 + 2.5 + 3.33} \right) = 434.5 \text{ k}\Omega$$



$$\frac{-\frac{V_o}{2}}{\frac{v_{id}}{2}} = -g_m (R_C || r_o) =$$

$$\frac{V_o}{v_{id}} = +20 (20 || 20) = +200 = A_d$$

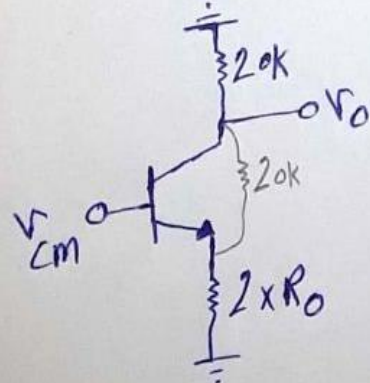


$$\frac{V_o}{v_{cm}} \approx \frac{-R_C}{R_E + \frac{1}{g_m}} = \frac{-20}{2 \times 434.5 + \frac{1}{20}}$$


$$\frac{V_o}{v_{cm}} = -0.023 = A_{cm}$$

$$CMRR = 8695.65$$

- 4- In the following circuit, Q_1 and Q_2 are the same and are biased in the active region.

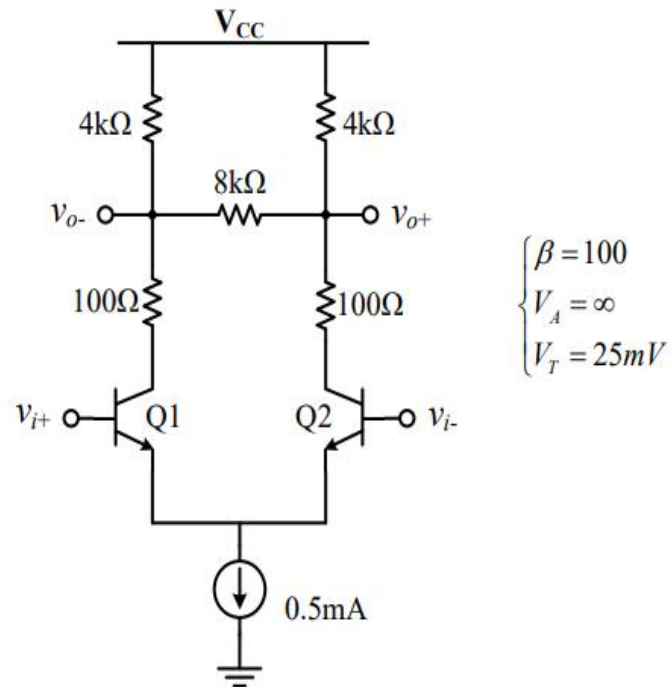Calculate the differential voltage gain ($A_d = \frac{v_{od}}{v_{id}} = \frac{v_{o+} - v_{o-}}{v_{i+} - v_{i-}}$).



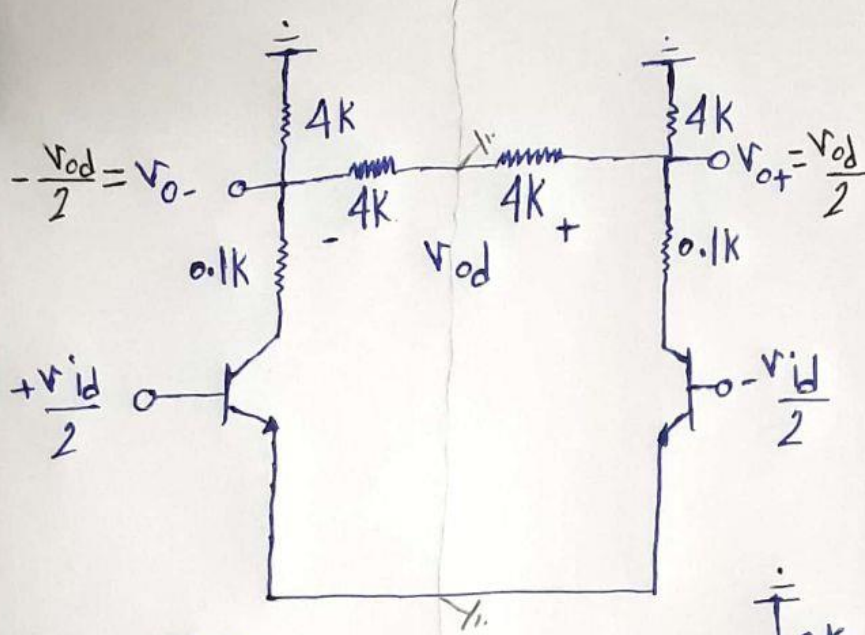

-4

$A_d = ?$

$$i_{C1} = i_{C2} = \frac{1}{4} \text{ mA}$$



$$g_{m1,2} = 10 \text{ mS}$$

$$r_{\pi 1,2} = 10 \text{ k}\Omega$$

$$V_0 = \infty$$

$$A_d = \frac{v_{od}}{v_{id}}$$

$$A_d = \frac{v_{o+} - v_{o-}}{v_{id}}$$

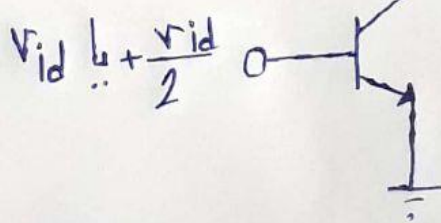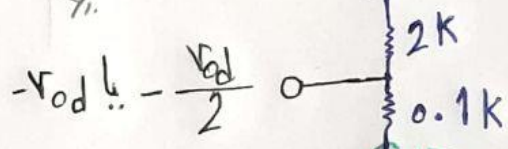


$$\frac{v_{od}}{v_{id}} = \frac{v_{od}}{v_n} \times \frac{v_n}{v_{id}}$$


$$\frac{v_{od}}{v_n} = \frac{-2}{2.1}$$

$$\frac{v_n}{v_{id}} = -g_m R_C = -10 \times 2.1 = -21$$

$$A_d = +20$$

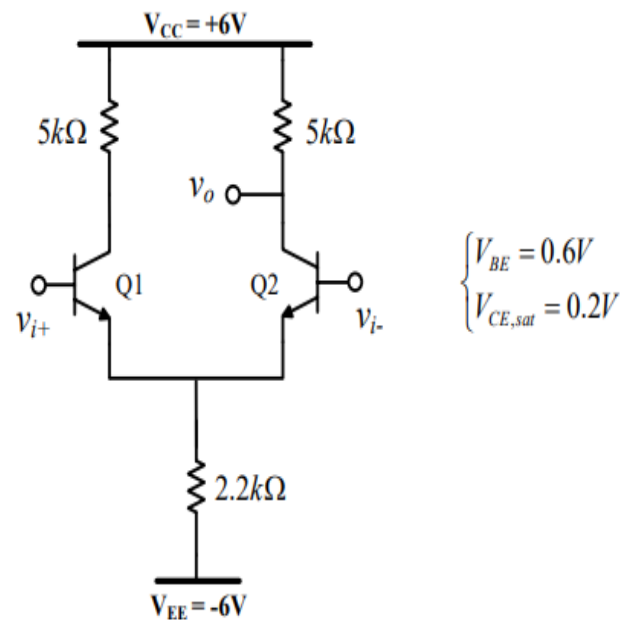5- In the following differential amplifier circuit, determine the input DC common-mode range.



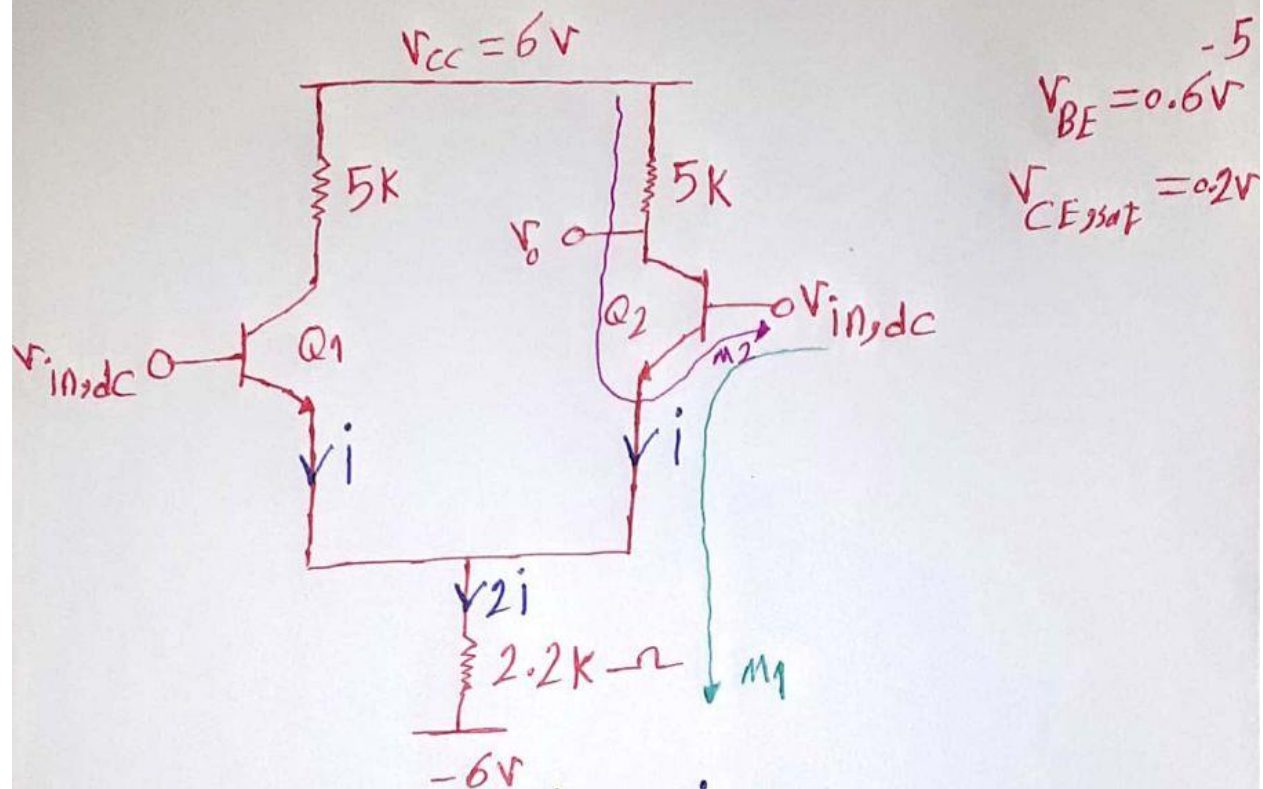

$$V_{BE1} = V_{BE2} \rightarrow i_{C1} = i_{C2} = i$$

$$\text{KVL @ } M_1: -V_{in,dc} + 0.6 + 4.4i - 6 = 0 \rightarrow i = \frac{5.4 + V_{in,dc}}{4.4}$$


$$\text{KVL @ } M_2: -6 + 5i + V_{CE2} - 0.6 + V_{in,dc} = 0$$

$$V_{CE2} = 6.6 - 5i - V_{in,dc} = 6.6 - 6.136 - 1.1363V_{in,dc} - V_{in,dc}$$


$$V_{CE2} = 0.464 - 2.1363V_{in,dc} \geq 0.2$$

$$V_{in,dc} \leq 0.123V$$

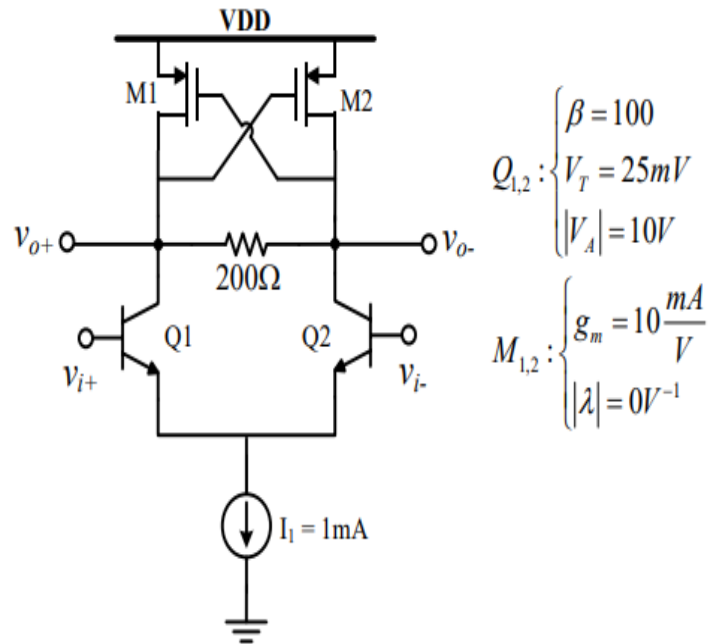- 6- Calculate the single-ended voltage gain $\{v_{o+}/(v_{i+} - v_{i-})\}$ as well as the fully-differential voltage gain $\{(v_{o+} - v_{o-})/(v_{i+} - v_{i-})\}$ for the following circuit.



-6

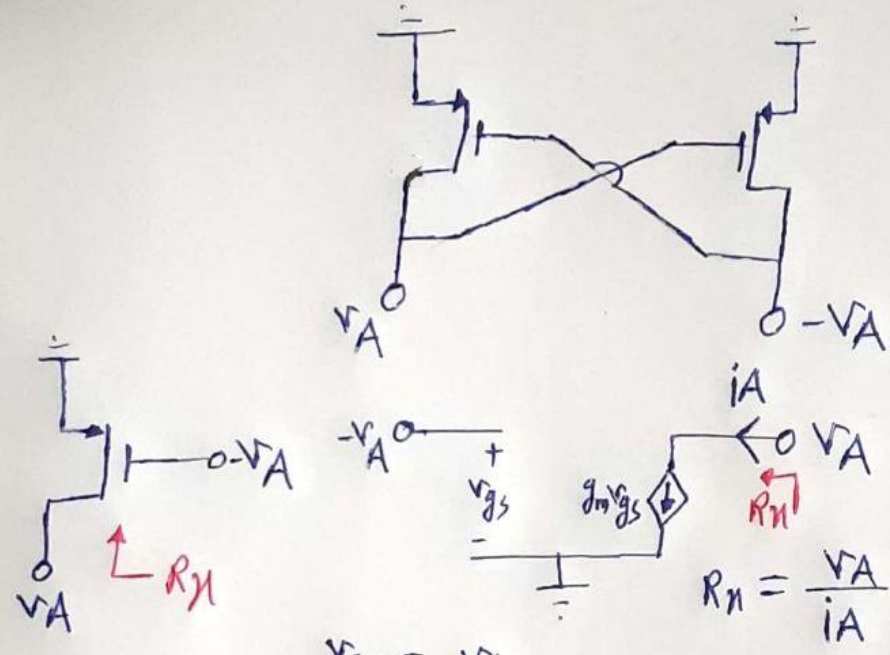


1- تفاضلی
2- تقارن

$$V_{gs} = -V_A$$

$$i_A = g_m V_{gs} = -g_m V_A = i_A \rightarrow R_N = -\frac{1}{g_m}$$

$$i_{C1} = i_{C2} = 0.5 \text{ mA} \rightarrow g_{mQ1,2} = 20 \text{ mS} \rightarrow r_{\pi 1,2} = 5 \text{ k}\Omega$$
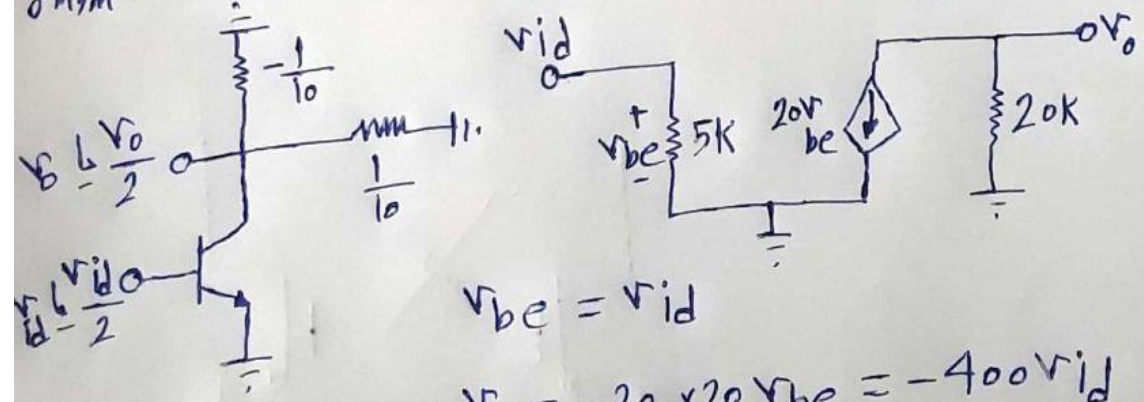
$$g_{mNM} = 10 \text{ mS} \quad V_{O1,2} = 20 \text{ k}\Omega$$




$$v_{be} = v_{id}$$

$$v_O = -20 \times 20 v_{be} = -400 v_{id}$$

$$\frac{v_O}{v_{id}} = A_d = -400$$

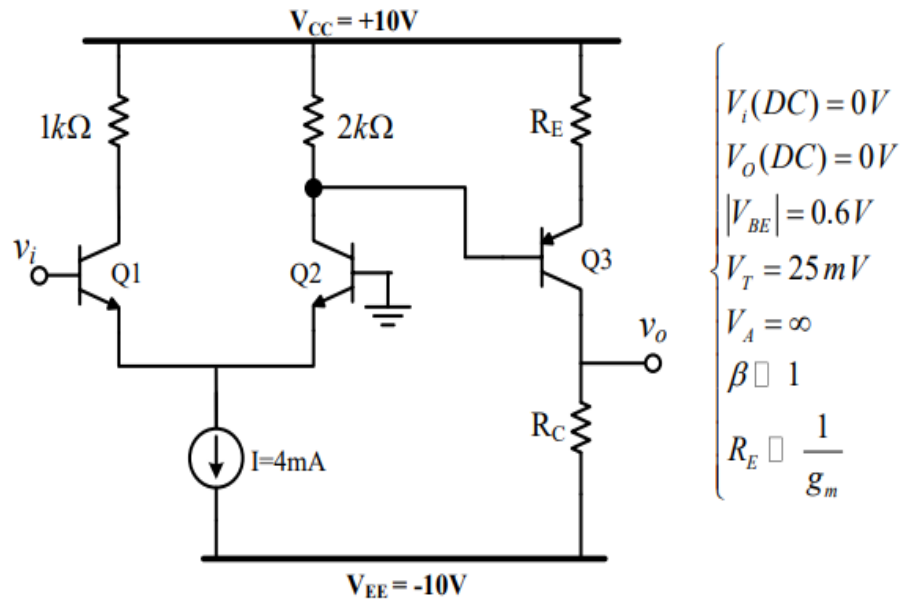7- In the following circuit, the DC output voltage is equal to zero. Calculate the voltage gain.



DC)

$$V_{BE1} = V_{BE2} \rightarrow i_{C1} = i_{C2} = 2 \text{ mA}$$


$$V_o = 0 \rightarrow i_{C3} = \frac{10}{R_C} \simeq i_{E3} \quad i_{B3} \simeq 0$$

$$\text{KVL @ } E: -10 + R_E i_{E3} + 0.6 - 2i_{C2} + 10 = 0$$

$$\frac{R_E \times 10}{R_C} = 3.4 \rightarrow \frac{R_C}{R_E} = \frac{10}{3.4} \quad (\text{I})$$

$$g_{m1,2} = 80 \frac{\text{mA}}{\text{V}}$$

AC)

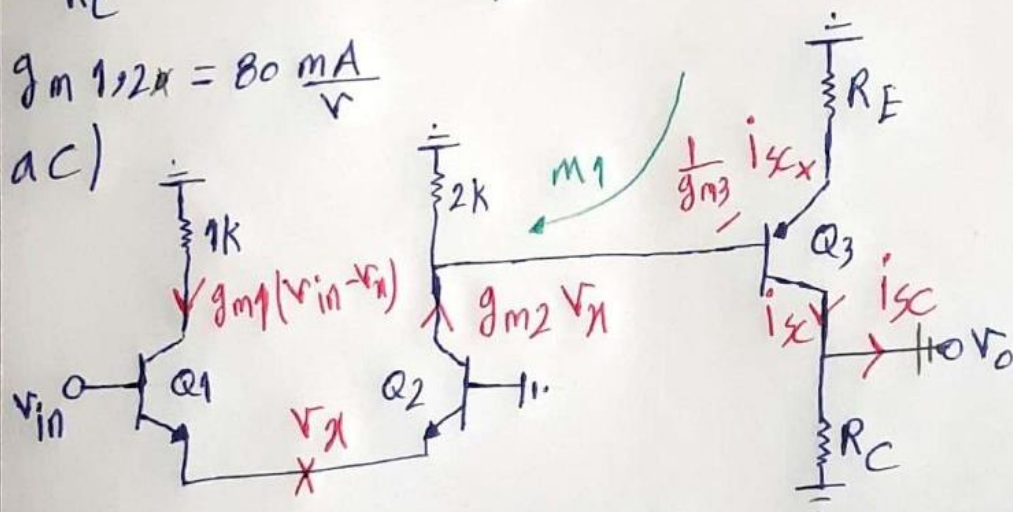

$$A_v = G_m \times R_{out} \quad R_{out} = R_C \quad G_m = ?$$

$$G_m = \frac{i_{sc}}{v_{in}}$$

$$g_{m1}(v_{in} - v_n) = g_{m2} v_n$$

$$v_n = \frac{g_{m1} v_{in}}{g_{m1} + g_{m2}}$$

$$\text{KVL @ } M_1: R_E i_{sc} + \frac{1}{g_{m3}} i_{sc} + 2g_{m2} \left(\frac{g_{m1} v_{in}}{g_{m1} + g_{m2}} \right) = 0$$

$$G_m = \frac{i_{sc}}{v_{in}} = \frac{-2g_{m1}g_{m2}}{(g_{m1} + g_{m2})(R_E + \frac{1}{g_{m3}})} = \frac{-2}{(\frac{1}{g_{m1}} + \frac{1}{g_{m2}})(R_E + \frac{1}{g_{m3}})}$$

$$A_v = G_m \times R_{out} = \frac{-2 R_C}{\left(\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \right) \left(R_E + \frac{1}{g_{m3}} \right)}$$

$$R_E \gg \frac{1}{g_m} \rightarrow A_v = \frac{-2 R_C}{\left(\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \right) R_E} \xrightarrow{(I)}$$

$$A_v = \frac{-2}{\frac{1}{80} + \frac{1}{80}} \times \frac{10}{3.4} \rightarrow A_v = -235.3$$