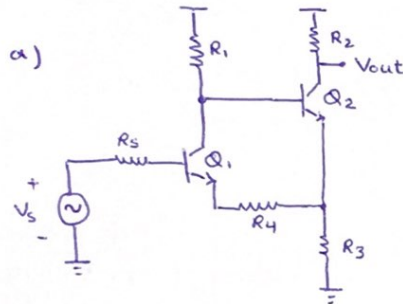



In the name of God

Assignment 8 :


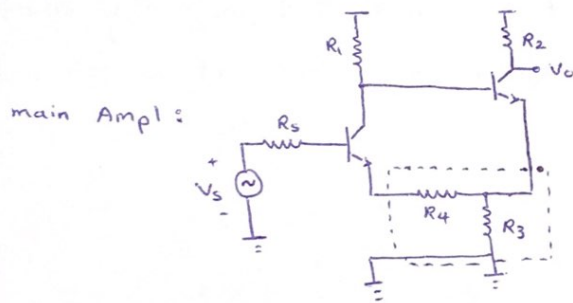
1. In the following circuits, specify the feedback network, main Amplifier section and the type of the feed back.



input of main ampl.
↑
input - output
series - series
 $\textcircled{\tilde{V}} - \textcircled{I}$





feedback network :

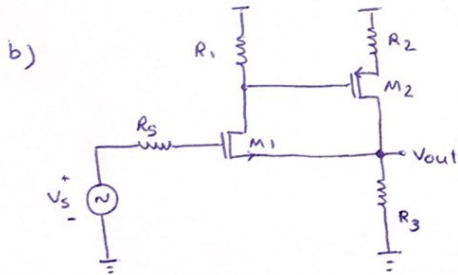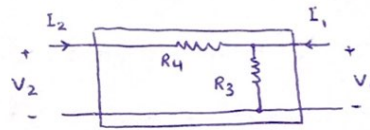


input - output
series - shunt
 $\textcircled{\tilde{V}} - \textcircled{\tilde{V}}$

Feedback network :

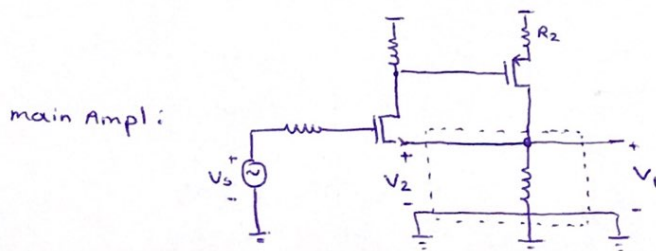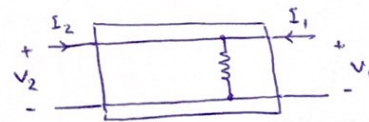


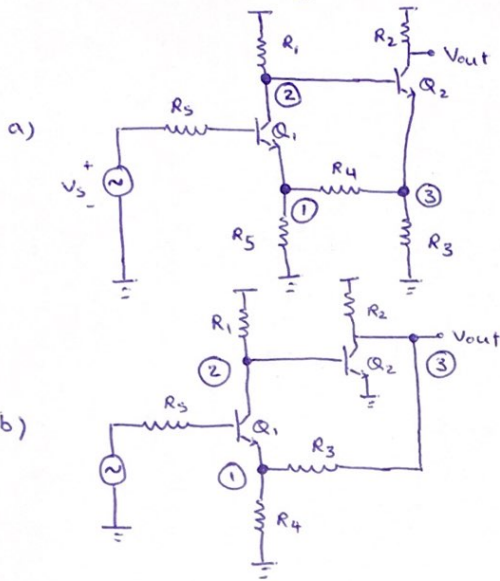
2. Determine the sign of the feedback in the following Circuits.




if $1 \uparrow (+) \Rightarrow 2 \uparrow (+) \Rightarrow 3 \uparrow (+)$
 $\Rightarrow 1 \uparrow (+)$: Positive feedback

if $1 \uparrow (+) \Rightarrow 2 \uparrow (+) \Rightarrow 3 \downarrow (-)$
 $\Rightarrow 1 \uparrow (+)$: negative feedback

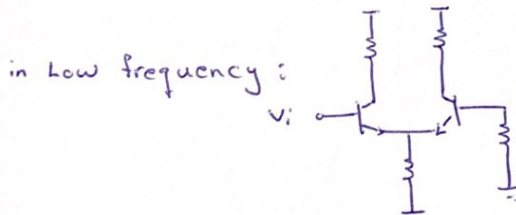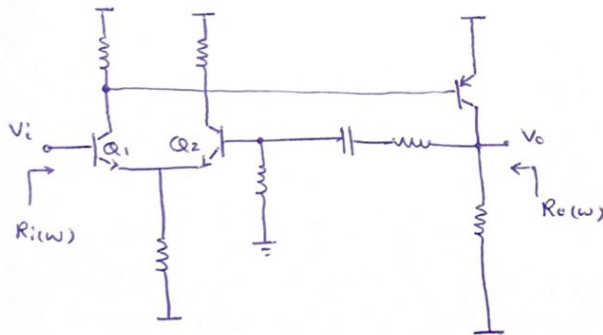3. In the circuit shown below, $R_i(\omega)$ and $R_o(\omega)$ are the input resistance and output resistance in term of ω . How do $R_i(\omega)$ and $R_o(\omega)$ change as the frequency varies from 0 to infinity. (Hint: Capacitor is modeled as an open-circuit in $\omega = 0$ and as the frequency goes to infinity)



there is no feedback

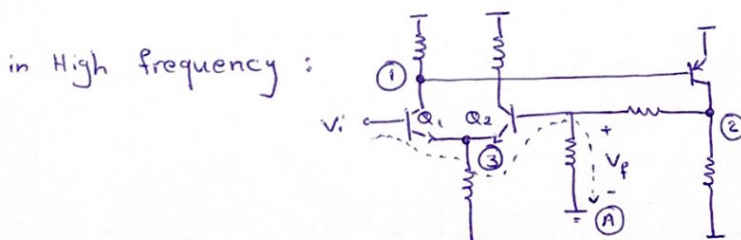

if $1 \uparrow (+) \rightarrow 2 \downarrow (-) \rightarrow 3 \downarrow (-)$
 $\Rightarrow 1 \downarrow (-)$: negative feedback

input - output
 series - shunt
 $\hat{V} - \hat{V}$

KVL @ A: $-V_i + V_{BE1} - V_{BE2} + V_f = 0$
 $V_i - V_f = (V_{BE1} - V_{BE2})$ error


$$R_{o(OL)} = \frac{R_{o(OL)}}{1 + af}$$

open loop gain
feedback network gain

$$R_{i(OL)} = R_{i(OL)} (1 + af)$$

پس با اثر ایس، مقاومت ورودی و مقاومت خروجی کاهش می یابد.

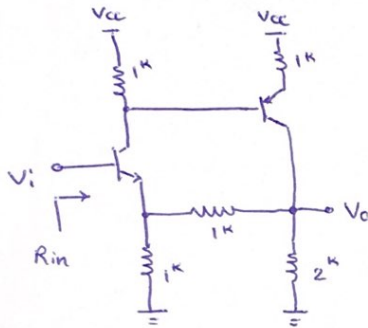4. Calculate the input resistance of the following circuit.




$$\begin{cases} r_{\pi} = 1k \\ \beta = 50 \end{cases}$$

Feedback network :



input — output
series — shunt


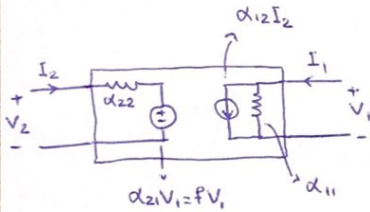


$$\begin{cases} I_1 = \alpha_{11} V_1 + \alpha_{12} I_2 \\ \bar{V}_2 = \alpha_{21} V_1 + \alpha_{22} I_2 \\ \quad \quad \quad = f \end{cases}$$


$$\alpha_{11} = \frac{I_1}{V_1} \Big|_{I_2=0} : \alpha_{11} = 1 + 1 = 2k$$

$$\alpha_{21} = f = \frac{V_2}{V_1} \Big|_{I_2=0} : \alpha_{21} = f = \frac{1k}{1k + 1k} = 0.5$$

$$\alpha_{22} = \frac{V_2}{I_2} \Big|_{V_1=0} : \alpha_{22} = 1k \parallel 1k = 0.5k$$

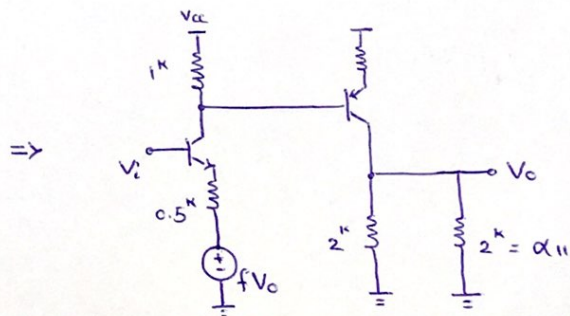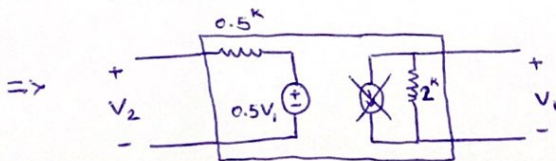

$$R_{in}|_{f=0} =$$

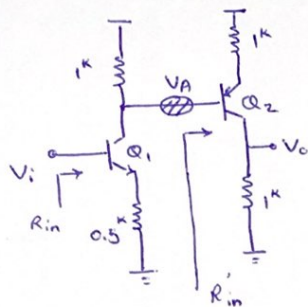

$$R'_{in} = r_{\pi 2} + (\beta + 1) R_{E2} = 1^k + 50(1^k) = 52^k$$

$$R_{in}|_{f=0} = r_{\pi 1} + (\beta + 1) R_{E1} = 1^k + 50(0.5) = 26.5$$

open loop input resistance

calculate open loop gain (a):

$$a = \frac{V_o}{V_i}|_{f=0} = \frac{V_o}{V_A} \times \frac{V_A}{V_i} = \frac{-R_{C2}}{R_{E2} + \frac{1}{g_{m2}}} \times$$


$$r_{\pi} = \frac{\beta}{g_m} \Rightarrow g_m = \frac{\beta}{r_{\pi}} = \frac{50}{1} = 50 \text{ mho}$$

$$\frac{-R_{C1}}{R_{E1} + \frac{1}{g_{m1}}}$$


$$= \left[\frac{-1^k}{1^k + \frac{1}{50}} \right] \times \left[\frac{-1^k || 52^k}{0.5^k + \frac{1}{50}} \right] = 0.98 \times 1.92 = 1.88$$

$$R_{in} = R_i|_{f=0} (1 + af) = 26.5 (1 + 1.88 \times 0.5) = 52^k$$

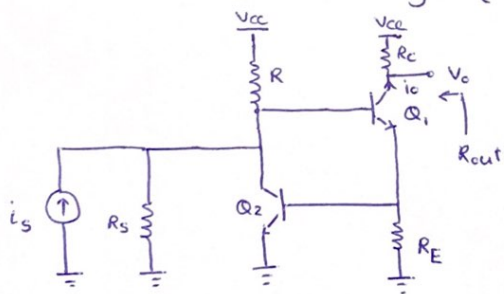5. In the following circuit, specify the type of the feedback configuration. In addition calculate the current gain ($\frac{i_o}{i_s}$) and the output resistance.



Input — output
shunt — series
ⓐ — ⓐ

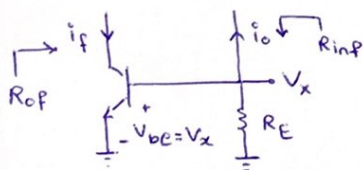

$$\beta = \frac{i_f}{i_o}$$

$$V_x = \frac{1}{g_{m2}} i_f$$


$$\text{KCL @ } V_x: \frac{V_x}{R_E} + \frac{i_f}{\beta_2} = -i_o$$

$$\Rightarrow \frac{1}{R_E g_{m2}} i_f + \frac{i_f}{\beta_2} = -i_o$$

$$\Rightarrow \frac{i_f}{i_o} = \frac{-\beta_2 R_E g_{m2}}{\beta_2 + R_E g_{m2}} = \beta \rightarrow$$

$$\begin{cases} R_{if} = R_E || r_{\pi 2} \\ R_{of} = r_{o2} \end{cases}$$

Open Loop Analysis :

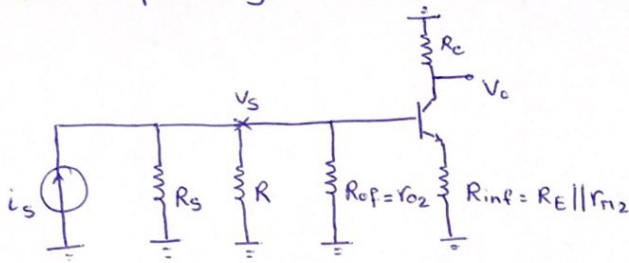

$$= \frac{-R || R_s}{R_E || r_{\pi 2}}$$

$$A_{OL} = a = \frac{i_o}{i_s} = \frac{i_o}{V_o} \times \frac{V_o}{V_s} \times \frac{V_s}{i_s}$$


$$= \left[\frac{1}{R_c} \right] \times \left[\frac{-R_c}{R_E || r_{\pi 2} + \frac{1}{g_{m1}}} \right] \times \left[\frac{R_s || R}{R_E || r_{\pi 2} + \frac{1}{g_{m1}}} \right] \approx \frac{-R || R_s}{R_E || r_{\pi 2} + \frac{1}{g_{m1}}}$$

$$R_{out(OL)} = r_{o1} [1 + g_{m1} (R_E || r_{\pi 2} || r_{\pi 1})] \quad , \quad T = af = a\beta = \frac{(R || R_s)(\beta_2 R_E g_{m2})}{(R_E || r_{\pi 2})(\beta_2 + R_E g_{m2})}$$

$$A_i = \left[\frac{i_o}{i_s} \right]_{CL} = \frac{A_{OL}}{1+T} = \frac{a}{1+af} = \frac{a}{1+a\beta}$$

$$R_{out(CL)} = R_{out(OL)} (1+af) \approx \cancel{R_c} \quad , \quad R_{out} = R_c || R_{out(CL)} \approx R_c$$

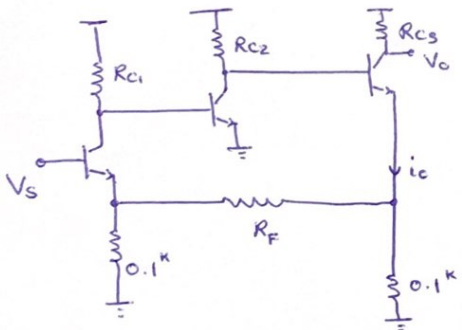
6. In the following circuit, specify R_f so that $\frac{i_o}{V_s} = 0.1$. The gain of the main Amplifier is assumed be very large.



$$A_{OL} = \frac{i_o}{V_s} \gg 1 \rightarrow A_{CL} = \frac{i_o}{V_s} = \frac{a}{1+af} \approx \frac{1}{f}$$

$$f = \frac{V_f}{i_o}$$

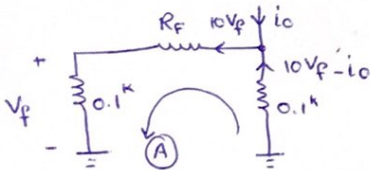
$$\frac{1}{f} = \frac{1}{10} \Rightarrow f = 10$$



$$\text{KVL @ A: } V_f - 0.1 i_o + 10 V_f R_F + V_f = 0 \Rightarrow (2 + 10 R_F) V_f = 0.1 i_o$$

$$\Rightarrow \frac{V_f}{i_o} = \frac{1}{10(2 + 10 R_F)} = 10 \Rightarrow \boxed{R_F = 0.8k}$$

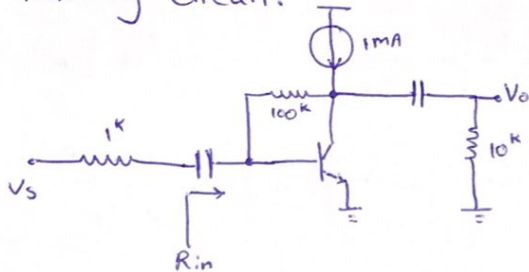7. Calculate the voltage gain ($\frac{V_o}{V_s}$) and the input resistance (R_{in}) of the following circuit.




$$\begin{cases} V_T = 25 \text{ mV} \\ \beta = 100 \end{cases}$$

input - output
shunt - shunt
 $\odot \bar{V}$ - $\odot \bar{V}$

$$I_C = 1 \text{ mA} \rightarrow g_m = 40 \text{ mmho}$$

$$r_\pi = 2.5 \text{ k}$$


Feedback network :

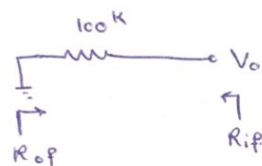

$$R_{of} = R_{if} = 100 \text{ k}$$

$$f = \frac{i_f}{V_o} = \frac{-1}{100}$$

open loop Analysis :

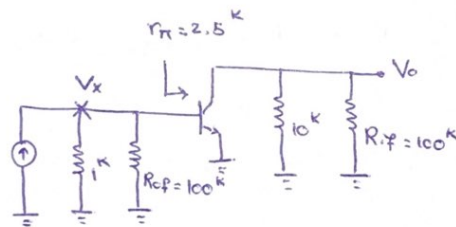

$$A_{OL} = a = \frac{V_o}{i_s} = \frac{V_o}{V_x} \times \frac{V_x}{i_s} = -g_m R_C \cdot [1 \text{ k} \parallel 100 \text{ k} \parallel 2.5 \text{ k}] = -400 (0.7 \text{ k}) = \boxed{-280}$$


$$R_{in(OL)} = 0.7 \text{ k}$$

$$A_{CL} = \frac{V_o}{i_s} = \frac{a}{1 + af} = \frac{-280}{1 + 2.8} = -73.68$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{V_o}{i_s} \times \frac{i_s}{V_s} = \boxed{-73.68}$$

$$R_{in(CL)} = \frac{R_{in(OL)}}{1 + af} = 0.2 \text{ k}, \quad R_{in(CL)} = R_{in} \parallel 1 \text{ k} \Rightarrow R_{in} = 1 \text{ k} \parallel -R_{in(CL)}$$

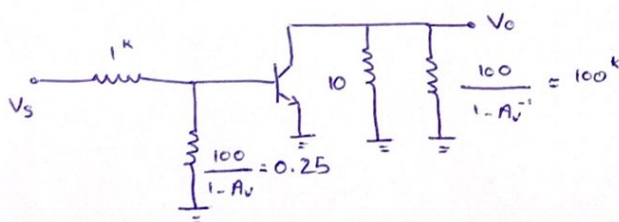
$$R_{in} = 1 \text{ k} \parallel 0.2 \text{ k} = \boxed{0.25 \text{ k}}$$



این مسئله با تعریف میله نینر حل می شود :

8. In the following circuit, Prove that the feedback sign is negative. in addition specify the type of the feedback configuration.

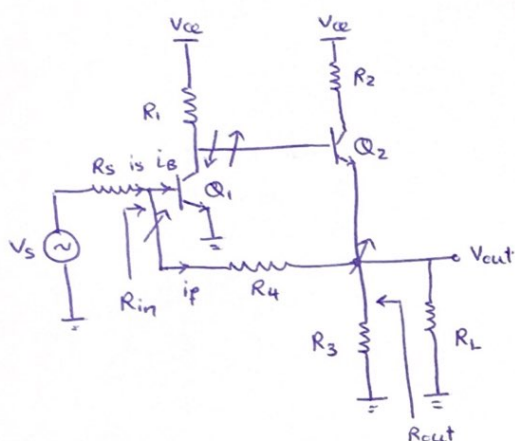b) calculate the voltage gain, input resistance and output resistance of the circuit.




$$(R_1 = R_3 = R_L = 10^k, R_2 = R_4 = 5^k, \beta = 100, g_m = 40 \text{ mmho})$$

$$V_A = \infty, V_{CC} = 10^V$$

input — output
shunt — shunt



feedback network:

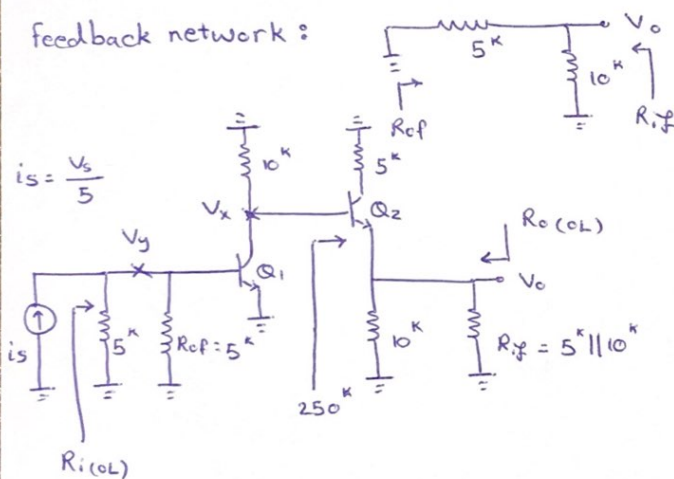

$$f = \frac{i_f}{V_o} = \frac{-1}{5^k}$$

$$R_{if} = 5^k \parallel 10^k = 3.33^k$$

$$R_{of} = 5^k$$

$$A_{OL} = a = \frac{V_o}{i_s} = \frac{V_o}{V_x} \times \frac{V_x}{V_y} \times \frac{V_y}{i_s} = \left[\frac{2.5}{2.5 + \frac{1}{40}} \right] \times [-40(10)] \times [5^k \parallel 5^k \parallel 2.5^k] \approx -500$$

$$\begin{cases} R_{O(OL)} = 2.5 \parallel \left(\frac{1}{40} + \frac{10}{100} \right) = 1.19^{\Omega} \\ R_{i(OL)} = 1.25^k \end{cases}$$

$$A_{CL} = \frac{A_{OL}}{1 + a f} = \frac{-500}{1 + 100} = -4.95^k = \frac{V_o}{i_s}$$

$$\frac{V_o}{V_s} = \frac{V_o}{i_s} \times \frac{i_s}{V_s} = -4.95 \left(\frac{1}{5} \right) = -0.99$$

$$R_{in(CL)} = \frac{R_{in(OL)}}{1 + a f} = \frac{1.25}{101} = 12.5^{\Omega}$$

$$R_{in(CL)} = 5^k \parallel R_{in} \Rightarrow R_{in} = 12.5$$

$$R_{O(CL)} = \frac{R_{O(OL)}}{1 + a f} = 1.19^{\Omega} \Rightarrow R_{O(CL)} = R_L \parallel R_O \Rightarrow R_O = 1.19$$


9. In the following circuit, suppose that $I_C = 1\text{mA}$ and $\beta = 100$ for all of the transistor.

a) Specify the feedback loop of the circuit and show that the feedback sign is negative.

b) specify the type of the feedback configuration.

c) Calculate the voltage gain.

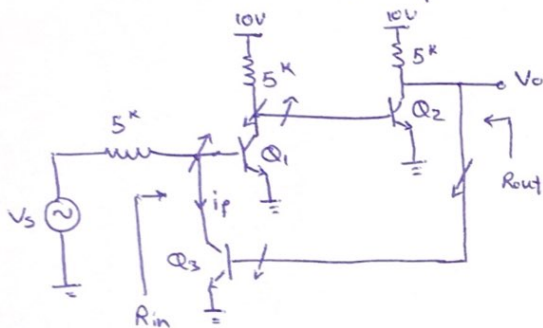d) Calculate the input and output resistance (R_{in} and R_{out})





$$\begin{aligned} I_C &= 1\text{mA} \\ \beta &= 100 \\ g_m &= 40\text{mmho} \\ r_{\pi} &= 2.5\text{k}\Omega \end{aligned}$$

a) negative feedback

b) input — output
shunt — shunt



c, d) Feedback network:

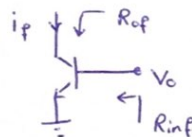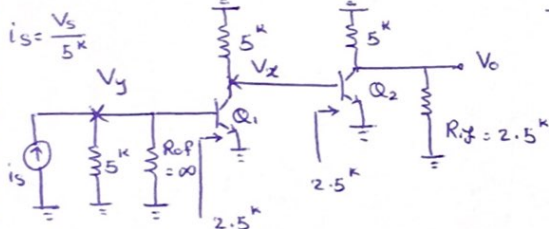

$$f = \frac{i_f}{V_o} = g_m = 40$$

$$R_{if} = r_{\pi} = 2.5\text{k}\Omega$$

$$R_{of} = r_o = \infty$$

$$\frac{V_o}{i_s} = (A_v)_{OL} = a = \frac{V_o}{V_x} \times \frac{V_x}{V_y} \times \frac{V_y}{i_s} = [-40(1.66)] \times [-1.66 \times 40] \times [1.66] = 7319$$

$$R_{in(OL)} = 1.66\text{k}\Omega, R_{o(OL)} = 1.66\text{k}\Omega$$

$$A_{CL} = \frac{V_o}{i_s} = \frac{A_{OL}}{1 + af} \xrightarrow{af \gg 1} A_{CL} = \frac{1}{f} = \frac{1}{40} = 25^{-2} = \frac{V_o}{i_s}$$

$$\frac{V_o}{V_s} = \frac{V_o}{i_s} \times \frac{i_s}{V_s} = 25 \times \frac{1}{500} = 5 \times 10^{-3} = \frac{1}{200} = \frac{V_o}{V_s}$$

$$R_{in(CL)} = \frac{1.66\text{k}\Omega}{1 + af} = 5.67\text{M}\Omega \Rightarrow 5.67\text{M}\Omega = R_{in} \parallel 5\text{k}\Omega \Rightarrow R_{in} = 5.67\text{M}\Omega$$

$$R_{o(CL)} = R_o = \frac{1.66\text{k}\Omega}{1 + af} = 5.67\text{M}\Omega = R_o$$