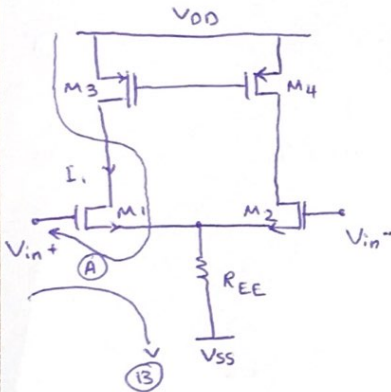


In the name of God

Assignment 7 :

1. Compare the following circuit in terms of input DC common mode range, output voltage swing, differential voltage gain and common-mode voltage gain




a) ICMR : KVL @ A : $-V_{DD} + V_{SD3} - V_{gs} + V_{SD1} + V_{indc} = 0$

$$V_{in,dc} = V_{DD} - V_{SD3} - V_{SD1} + V_{gs}$$


KVL @ B : $-V_{in,dc} + V_{gs} + 2I_1 R_{EE} - V_{SS} = 0$

$$V_{in,dc} = V_{gs} + 2I_1 R_{EE} - V_{SS}$$

b) output swing :

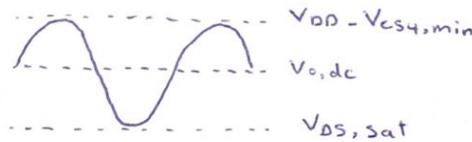


c) differential half circuit :

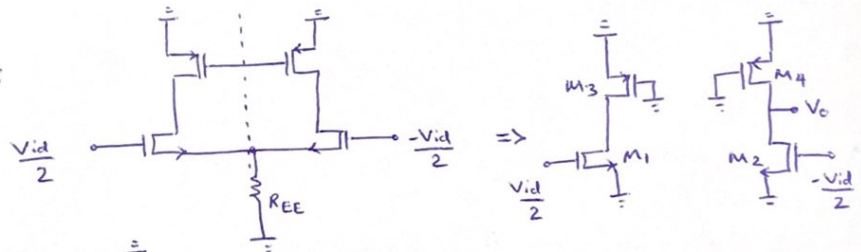

hint : $\frac{V_o}{V_{id}} \equiv r_{ds}$

=>

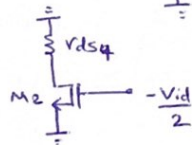


$$\frac{V_o}{V_{id}} = g_m (R_D || r_{ds}) = g_m (r_{ds2} || r_{ds4})$$


$$\text{If } r_{ds2} = r_{ds4}, \frac{V_o}{V_{id}} = \frac{1}{2} g_m r_{ds}$$

$$\Rightarrow \frac{V_o}{V_{id}} = \frac{1}{4} g_m r_{ds}$$

Common mode gain :

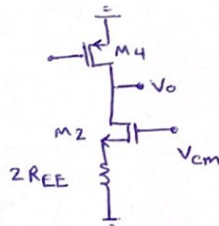
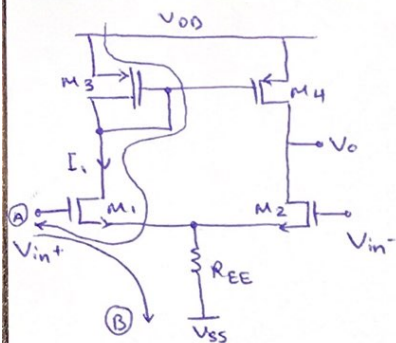
$$A_{vcm} = \frac{V_o}{V_{cm}} = \frac{-R_D}{R_S + \frac{1}{g_m}} = \frac{-r_{ds4}}{2R_{EE} + \frac{1}{g_m}}$$




a) ICMR : KVL @ A : $-V_{DD} + V_{SG3} + V_{OS1} - V_{SG1} + V_{in,dc} = 0$

$$V_{in,dc,max} = V_{DD} - V_{SG3} - V_{OS1} + V_{SG1}$$

KVL @ B : $-V_{in,dc} + V_{SG1} + 2I_1 R_{EE} - V_{SS} = 0$
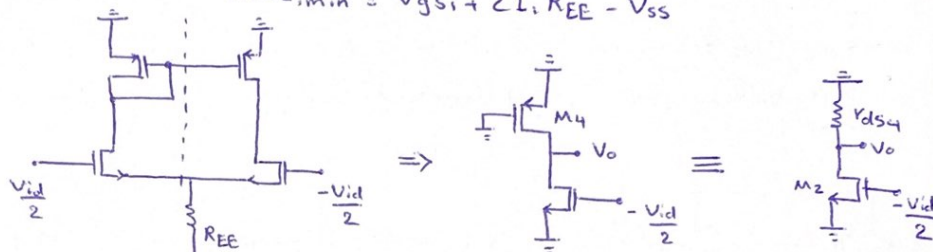
$$V_{in,dc,min} = V_{SG1} + 2I_1 R_{EE} - V_{SS}$$




b) differential gain :

$$\frac{V_o}{-V_{id}/2} = -g_{m2} (R_o || r_{ds}) = -g_{m2} (r_{ds4} || r_{ds2}) \Rightarrow A_{vd} = \frac{V_o}{V_{id}} = \frac{1}{2} g_{m2} (r_{ds4} || r_{ds2}) \xrightarrow{r_{ds2} = r_{ds4}}$$


$$A_{vd} = \frac{1}{4} g_{m2} r_{ds}$$

common mode gain :

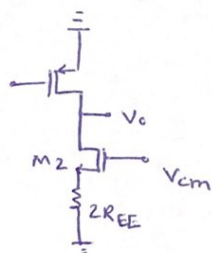

$$\Rightarrow A_{vcm} = \frac{V_o}{V_{cm}} = \frac{-R_o}{R_s + \frac{1}{g_m}} = \frac{-r_{ds4}}{2R_{EE} + \frac{1}{g_{m2}}}$$


c) output swing :

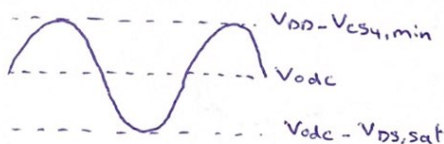

2. In the following circuit, the specification of the ~~transistors~~ transistors are the same.

a) calculate the differential Voltage gain directly. Discuss about the result.

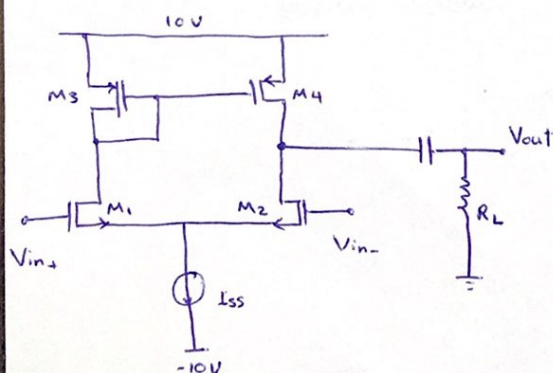b) Determine the common-mode Voltage gain directly. Discuss about the result.



$$\beta = 1 \frac{mA}{V^2}$$

$$|V_{th}| = 2V$$


$$\lambda = \frac{1}{75} V^{-1}$$

$$R_L = 50k$$

$$I_{SS} = 1mA$$


dc analysis: $I_{D1} = I_{D2} = 0.5 \text{ mA}$ $\rightarrow g_{m1} = g_{m2} = 2\sqrt{k I_D} = 2\sqrt{\frac{1}{2} \times \frac{1}{2}} = 1 \text{ mmho}$
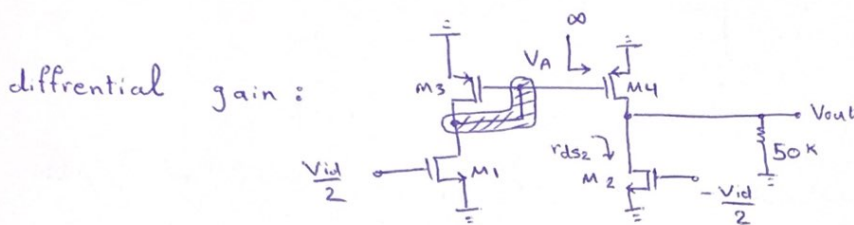
$$r_{ds} = \frac{1}{\lambda I_D} = \frac{1}{\frac{1}{75} \times \frac{1}{2}} = 150 \text{ k}$$



$$\frac{V_{out}}{\frac{V_{id}}{2}} = \frac{V_{out}}{V_A} \times \frac{V_A}{\frac{V_{id}}{2}} = \left[-g_{m4} (r_{ds2} \parallel 50 \text{ k} \parallel r_{ds4}) \right] \times \left[-g_{m1} (r_{ds1} \parallel r_{ds3}) \right]$$
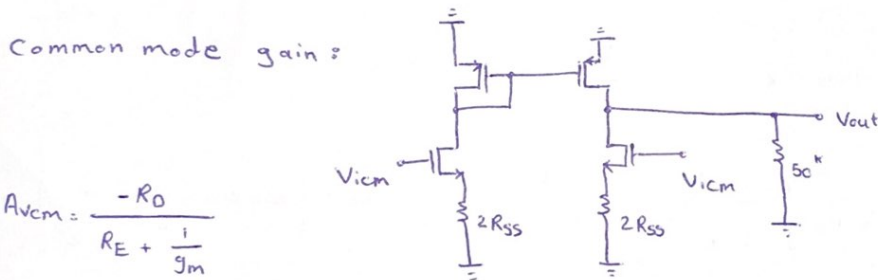
$$= \left(-1 (150 \text{ k} \parallel 50 \text{ k} \parallel 150 \text{ k}) \right) \times \left(-1 (150 \text{ k} \parallel 150 \text{ k}) \right) = -30(-75) = 2250$$




$$A_{vcm} = \frac{-R_O}{R_E + \frac{1}{g_m}}$$

هزینه R_{ss} زیادتر باشد، بهره حالت مشترک کوچکتر می شود (حالت ایده آل: $R_{ss} = \infty$)

$$= \frac{-r_{ds3}}{2R_{ss} + \frac{1}{g_m}}$$

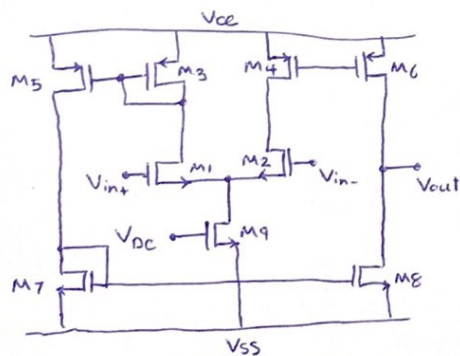3. In the following circuit determine the CMRR and input differential resistance.



$$V_{eff1,2} = 0.1 \text{ V}, V_{eff3,4} = 0.2 \text{ V}$$

$$\lambda = 0.1 \text{ V}^{-1}$$

$$I_{D9} = 1 \text{ mA}$$

$$\left(\frac{W}{L}\right)_{5,6} = 2 \left(\frac{W}{L}\right)_{3,4} \rightarrow I_{D5} = I_{D6} = 2 I_{D3} = 2 I_{D4}$$

$$\left(\frac{W}{L}\right)_7 = \left(\frac{W}{L}\right)_8$$

dc analysis: $I_{D9} = 1 \text{ mA}$, $I_{D1} = I_{D2} = I_{D5} = I_{D4} = 0.5 \text{ mA}$, $I_{D5} = I_{D6} = I_{D7} = I_{D8} = 1 \text{ mA}$

$$g_{m1,2} = \frac{2I_D}{V_{eff}} = \frac{2 \times \frac{1}{2}}{0.1} = 10 \text{ mmho}$$

$$g_{m5,6} = \frac{2(1)}{0.2} = 10 \text{ mmho}$$


$$g_{m3,4} = \frac{2(0.5)}{0.2} = 5 \text{ mmho}$$

$$g_{m7,8} = \frac{2(1)}{0.2} = 10 \text{ mmho}$$

$$r_{ds1,4} = \frac{1}{\lambda I_D} = 20 \text{ k}$$


$$r_{ds5,9} = 10 \text{ k}$$

differential gain:

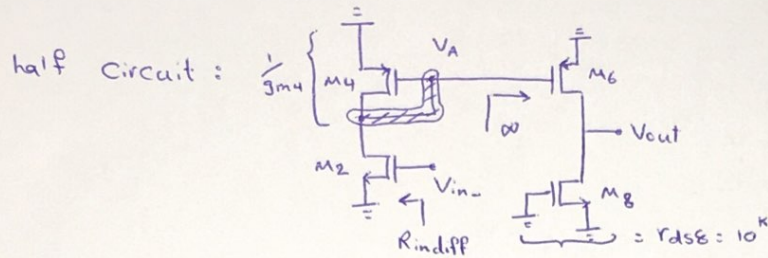

$$A_{vd} = \frac{V_{out}}{V_{in-}} = \frac{V_{out}}{V_A} \times \frac{V_A}{V_{in-}} = \left[-g_{m6} (R_D \parallel r_{ds8}) \right] \times \left[-g_{m2} (R_D \parallel r_{ds2}) \right] = \left[-10 (10^4 \parallel 10^4) \right] \times \left[-10 (20^4 \parallel \frac{1}{5^4}) \right] = (-2) \times (-50) = 100$$

Common mode input:

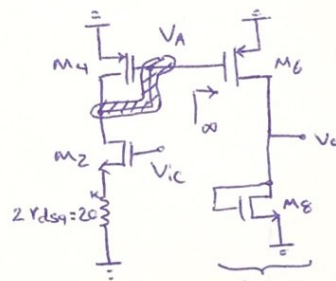

$$A_{vcm} = \frac{V_o}{V_A} \times \frac{V_A}{V_{ic}} = \left[-g_{m6} (R_D \parallel r_{ds6}) \right] \times \left[\frac{-R_{D2}}{R_{S2} + \frac{1}{g_{m2}}} \right] = \left[-10 \left(\frac{1}{10^4} \parallel 10^4 \right) \right] \times \left[\frac{-\frac{1}{g_{m4}}}{20^4 + \frac{1}{10^4}} \right] = -0.1 \left(\frac{-0.2}{20.1} \right) = 0.00099 \approx 0.001$$

$$CMRR = \frac{A_{vd}}{A_{vcm}} = \frac{100}{0.001} = 100000 \Rightarrow 20 \log(100000) = 100 \text{ dB}$$

$$R_{in \text{ diff}} = \infty$$