

$$i = -10^{-3}V_o + 2 \times 10^{-4}V_o^2 + 3 \times 10^{-5}V_o^3$$

$$V_o(t) = V_o \cos \omega_o t \quad \text{حروف حرونی اصلی}$$

$$i(t) = -10^{-3}V_o \cos \omega_o t + 2 \times 10^{-4}V_o^2 \cos \omega_o t$$

$$+ 3 \times 10^{-5}(V_o \cos \omega_o t)^3$$

$$i(t) = -10^{-3}V_o \cos \omega_o t + 2 \times 10^{-4}V_o^2 \underbrace{(1 + \cos 2\omega_o t)}_z + 3 \times 10^{-5}V_o^3 (\cos \omega_o t)(1 + \cos 2\omega_o t)$$

$$i_1(t) = (-10^{-3}V_o + 3/2 \times 10^{-5}V_o^3) \cos \omega_o t \quad \text{حروف حرونی اصلی}$$

: kcl

$$V_o \left(\frac{1}{j\omega L} + j\omega C + G \right) + (-10^{-3}V_o + 3/2 \times 10^{-5}V_o^3) = 0$$

$$j(\omega_0 C - \frac{1}{\omega_0 L}) + (G - \bar{I}_0^3) + 1.5 \times \bar{I}_0^{-5} V_0^2 = 0$$

$\circ \rightarrow \omega_0 = \frac{1}{\sqrt{LC}} = 75.187 \text{ Mrad/sec}$

$$f_0 \approx 11.966 \text{ MHz}$$

$$G - \bar{I}_0^{-3} + 1.5 \times \bar{I}_0^{-5} V_0^2 = 0$$

$$\frac{1}{5000} - \bar{I}_0^{-3} + 1.5 \times \bar{I}_0^{-5} V_0^2 = 0 \Rightarrow V_0^2 = 53.33$$

دائم و محرفي $V_0 = 7.30$ و ω


لطفاً رسن دم حرفی تری؟

$$\left| \frac{V_n}{V_1} \right| = \frac{I_n}{I_1} \times \frac{n}{(n^2 - 1) \theta_T}$$


$$\left| \frac{V_2}{V_1} \right| = \frac{\left(\bar{I}_0^{-4} \times 7.3^2 \right)}{\left(\bar{I}_0^{-3} \times 7.3 - 1.5 \times \bar{I}_0^{-5} \times 7.3^3 \right)} \times \frac{2}{(4-1)} \times 30.2$$


$$\theta_T = \frac{R}{\omega_0 L} = 30.2$$

$$\left| \frac{V_2}{V_1} \right| = 0.018 \Rightarrow V_2 = 0.132 \text{ Volt}$$

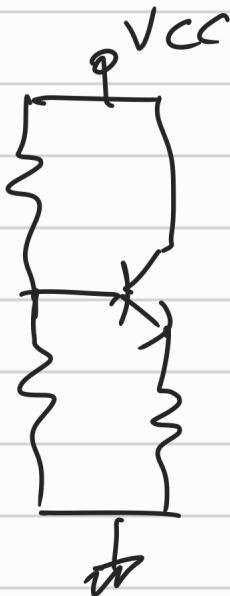

DC Jsw, h (Y)

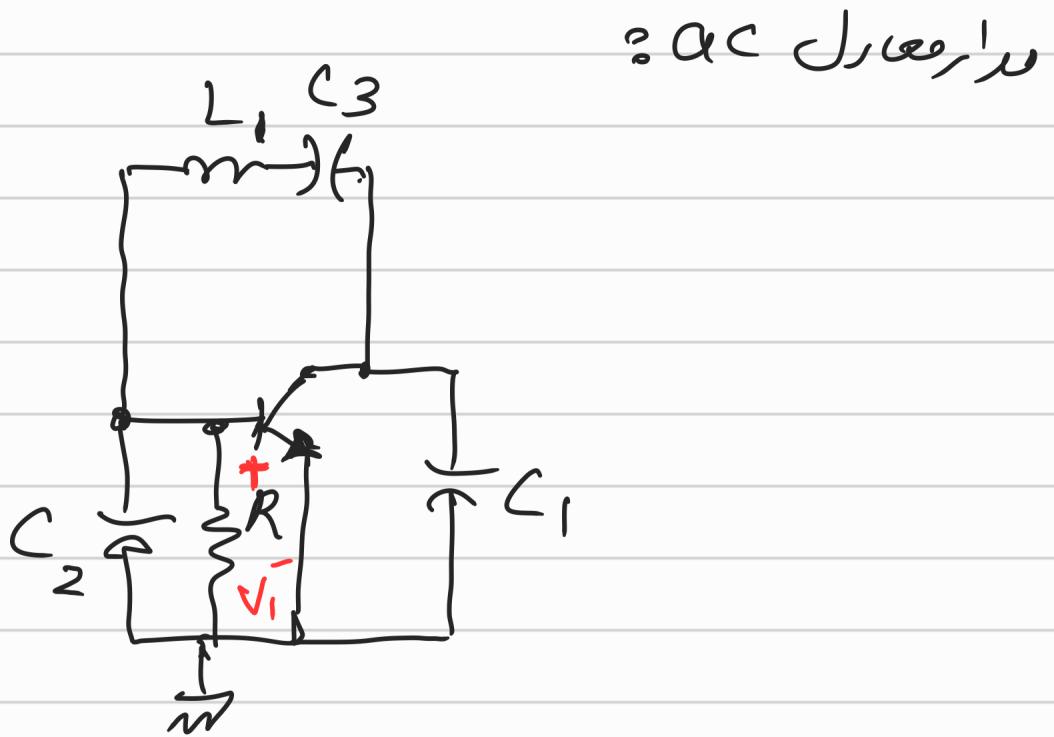

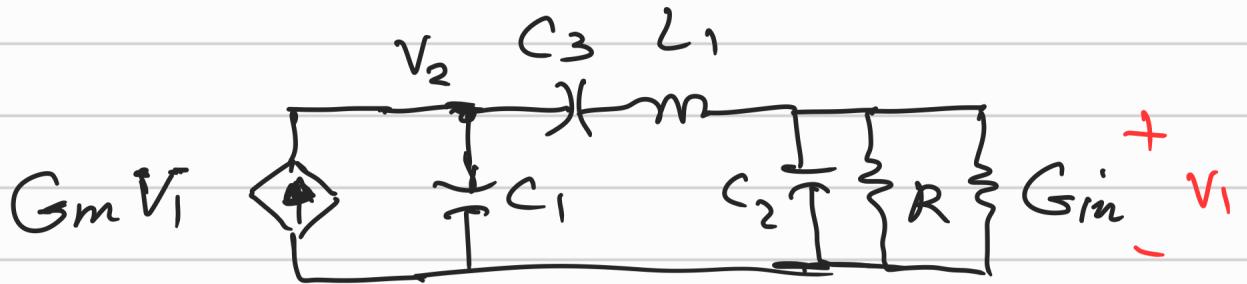

$$\left\{ \begin{array}{l} \textcircled{1} \\ G_m V_1 + V_2 (j\omega C_1) + (V_2 - V_1) \left(\frac{1}{\frac{1}{j\omega C_3} + j\omega L_1} \right) = 0 \\ (V_1 - V_2) \frac{1}{\frac{1}{j\omega C_3} + j\omega L_1} + V_1 (j\omega C_2 + G + G_{in}) = 0 \end{array} \right.$$

$$V_1 \left(\frac{j\omega C_3}{1 - \omega^2 C_3 L_1} + j\omega C_2 + G + G_{in} \right) = \frac{V_2 j\omega C_3}{1 - \omega^2 C_3 L_1}$$

$$V_2 = \frac{V_1 \left(j\omega C_3 / 1 - \omega^2 C_3 L_1 + j\omega C_2 + G + G_{in} \right)}{j\omega C_3 / 1 - \omega^2 C_3 L_1}$$

$$V_2 = V_1 \left(1 + \frac{C_2}{C_3} (1 - \omega^2 C_3 L_1) + \frac{-j(G + G_{in})(1 - \omega^2 C_3 L_1)}{\omega C_3} \right)$$

١

$$(G_m - \frac{j\omega C_3}{1 - \omega^2 C_3 L_1}) V_1 + \left(j\omega C_1 + \frac{j\omega C_3}{1 - \omega^2 C_3 L_1} \right) V_2 = 0$$

$$G_m - \frac{j\omega C_3}{1 - \omega^2 C_3 L_1} + \left(j\omega C_1 + \frac{j\omega C_3}{1 - \omega^2 C_3 L_1} \right) (1 +$$

$$\frac{C_2}{C_3} (1 - \omega^2 C_3 L_1) - j \frac{(G + G_{in})(1 - \omega^2 C_3 L_1)}{\omega C_3} = 0$$

$$G_m + \frac{C_1}{C_3} (G + G_{in})(1 - \omega^2 C_3 L_1) + (G + G_{in}) +$$

$$j(\omega C_1 + \omega C_2) + \frac{\omega C_1 C_2}{C_3} (1 - \omega^2 C_3 L_1) = 0$$

$$C_1 + C_2 + \frac{C_1 C_2}{C_3} - C_1 C_2 L_1 \omega^2 = 0$$

$$\omega_0 = \sqrt{\frac{C_1 + C_2 + \frac{C_1 C_2}{C_3}}{C_1 C_2 L_1}}$$

فرط سریع

$$G_{in} = \frac{C_b}{V_{be}} = \frac{C_b}{C_C} \cdot \frac{C_C}{V_{be}} = \frac{1}{\beta} G_m$$


$$G_m + \frac{C_1}{C_3} (G + G_{in}) (1 - \omega_0^2 C_3 L_1) + G + G_{in} = 0$$

$$G_m \left(1 + \frac{C_1}{C_3} \frac{1}{\beta} (1 - \omega_0^2 C_3 L_1) + \frac{1}{\beta} \right)$$

$$+ \frac{C_1}{C_3} G (1 - \omega_0^2 C_3 L_1) + G = 0$$


$$G_m = \frac{G \left(\frac{C_1}{C_3} (1 - \omega_0^2 C_3 L_1) + 1 \right)}{\frac{C_1}{\beta C_3} (\omega_0^2 C_3 L_1 - 1) - \left(1 + \frac{1}{\beta} \right)}$$

PC chís (β Drs)

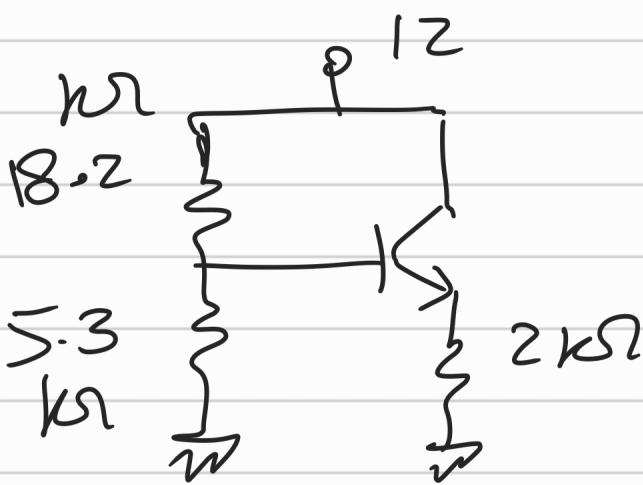


$$\beta = \infty$$

$$\alpha = 1$$

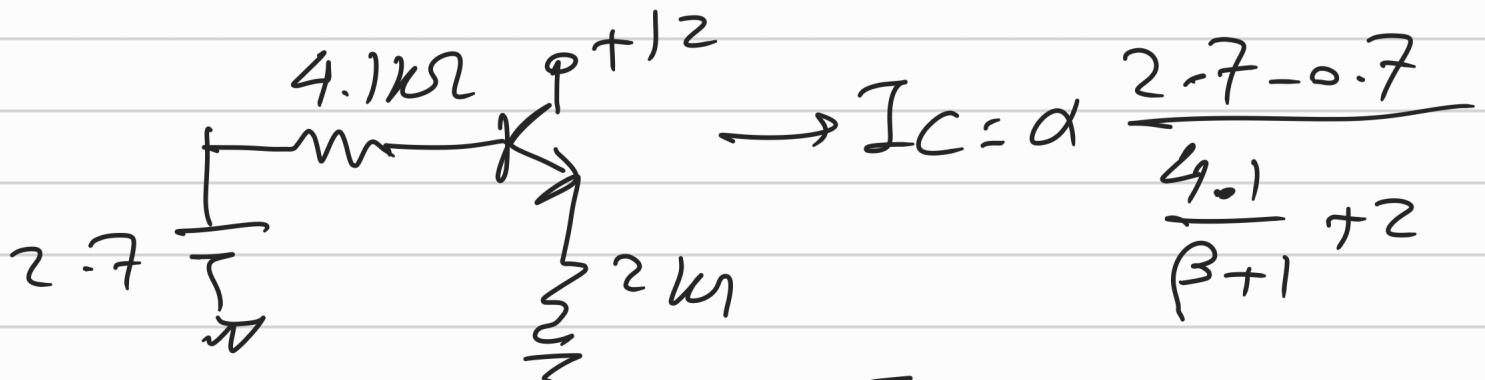



$$I_C = \alpha \frac{2.7 - 0.7}{\frac{4.1}{\beta + 1} + 2}$$

$$I_C = 1 \text{ mA}$$

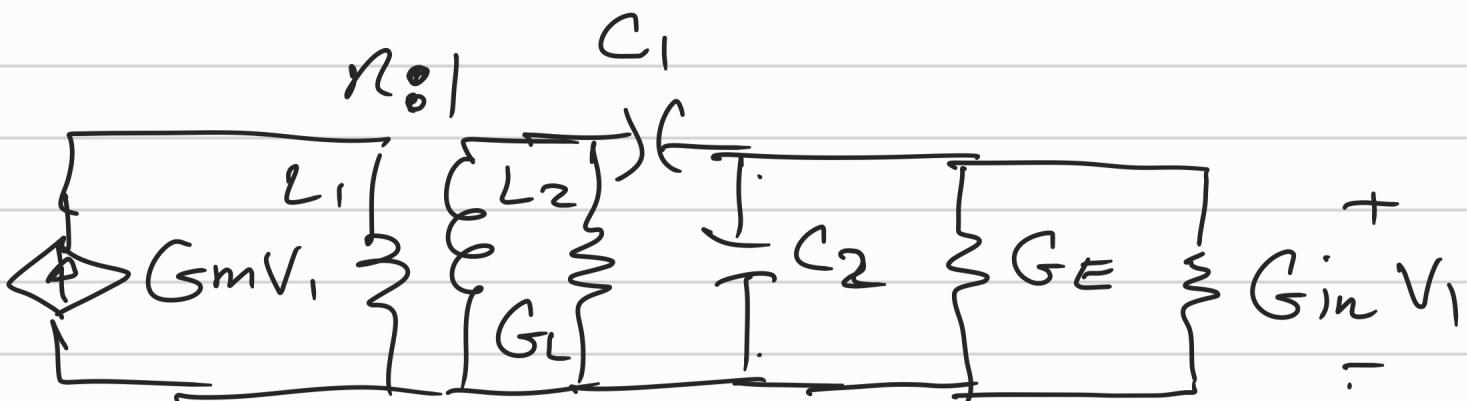
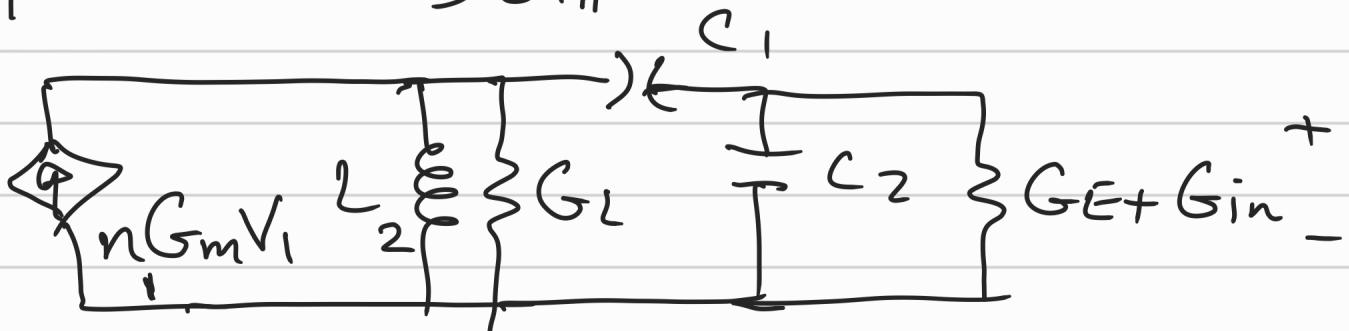
$$n_1 = M/L_2 = \frac{200nH}{500nH} = 0.4$$



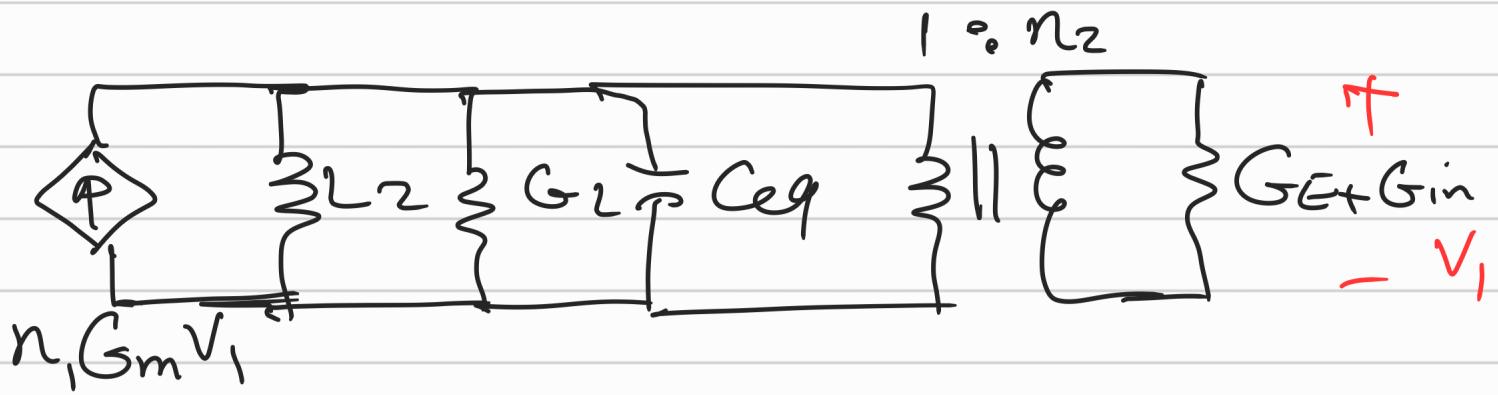

$$n_1 G_m V_1 = \frac{V_1}{n_2} \left(\frac{1}{j\omega L_2} + j\omega C_{eq} + G_L + n_2^2 (G_E + G_{in}) \right)$$

$$\frac{n_2 n_1 G_m}{j(\omega C_{eq} - \frac{1}{\omega L_2}) + G_L + n_2^2 (G_E + G_{in})} = 1$$

$$\omega C_{eq} - \frac{1}{\omega L_2} = 0$$

جواب بحث

$$\omega_o = \frac{1}{\sqrt{L_2 C_{eq}}}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\frac{n_2 n_1 G_m}{G_L + n_2^2 (G_E + G_{in})} = 1$$

$$G_{in} = \frac{i_e}{i_c} \cdot \frac{i_c}{V_{be}} = \frac{1}{\alpha} G_m$$

$$n_1 n_2 G_m = G_L + n_2^2 G_E + n_2^2 \frac{G_m}{\alpha}$$

$$G_m = \frac{G_L + n_2^2 G_E}{n_2 (n_1 - n_2 / \alpha)}$$

$$n_1 = M/L_2$$

$$n_2 = \frac{C_1}{C_1 + C_2}$$

$$G_E = 1/R_E$$