
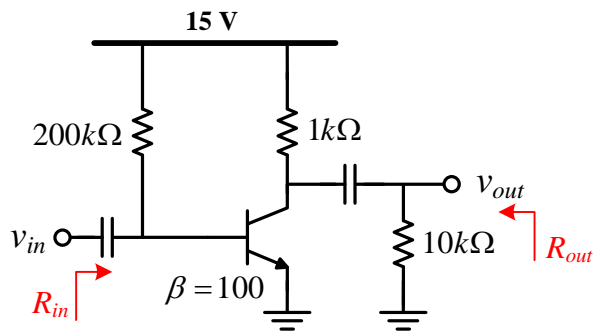


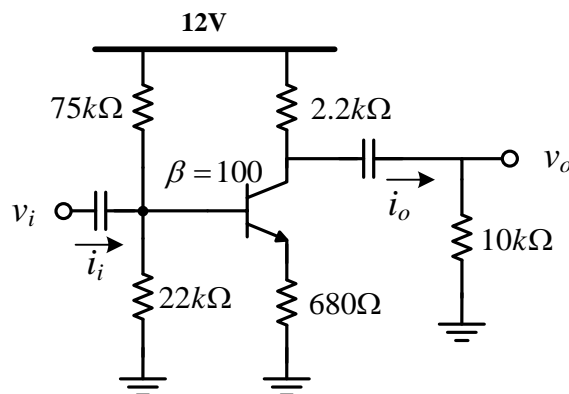
1. In the following circuit, determine the input resistance, R_{in} , output resistance, R_{out} , and the small-signal voltage gain, $A_v = v_o/v_i$.




2. In the following circuit, determine the current gain, $A_i = i_o/i_i$, and the voltage gain, $A_v = v_o/v_i$.



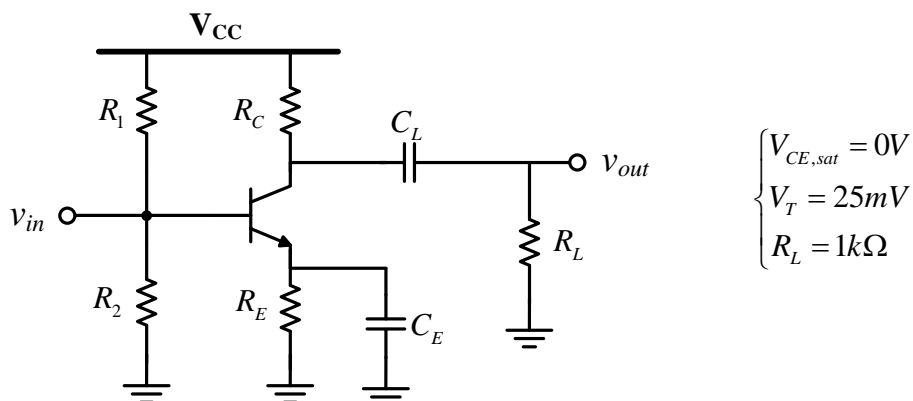3. The small-signal voltage gain of the following circuit is supposed to be 48 and the DC voltage across R_C is 3 V. Determine the value of R_C .




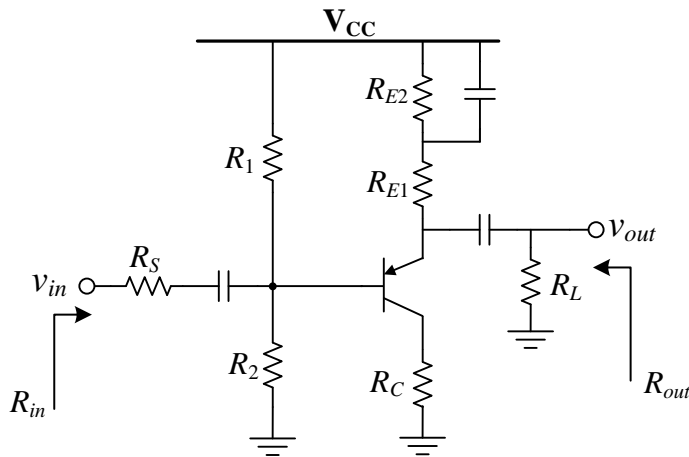4. In the following circuit, determine the input resistance, R_{in} , output resistance, R_{out} , and the small-signal voltage gain, $A_v = v_o/v_i$.




$$\begin{cases} R_S = 2k\Omega, R_1 = 3k\Omega, R_2 = 7k\Omega \\ R_{E1} = 1k\Omega, R_{E2} = 1.3k\Omega \\ R_C = 2k\Omega, R_L = 1k\Omega \\ |V_{BE,on}| = 0.7V, |V_{CEsat}| = 0.2V \\ V_A = \infty, V_T = 25mV, \beta = 100 \\ V_{CC} = 10V \end{cases}$$

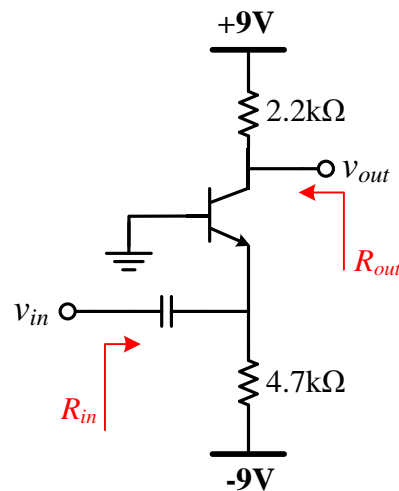5. Calculate the small-signal voltage gain, input resistance, and output resistance of the structure shown below.




$$\begin{cases} V_{BE} = 0.7V \\ V_{CEsat} = 0.2V \\ V_A = \infty \\ V_T = 25mV \\ \beta = 100 \end{cases}$$

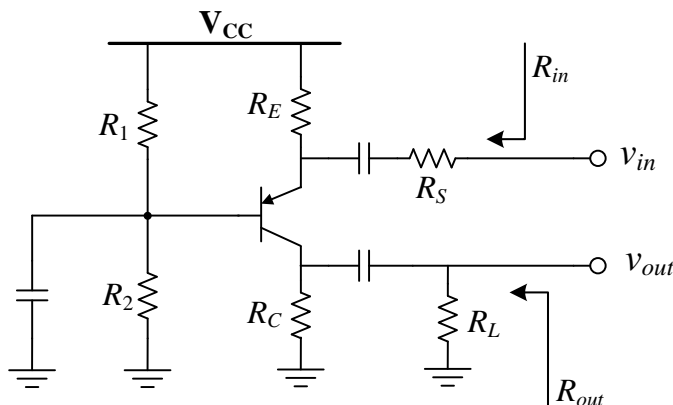6. In the following circuit, determine the input resistance, R_{in} , output resistance, R_{out} , and the small-signal voltage gain, $A_v = v_o/v_i$.



$$\begin{cases} R_S = 25\Omega, R_1 = 3k\Omega, R_2 = 7k\Omega \\ R_E = 2.3k\Omega, R_C = 2k\Omega, R_L = 2k\Omega \\ V_{EB,on} = 0.7V, V_{ECsat} = 0.2V \\ V_A = \infty, V_T = 25mV, \beta = 100 \\ V_{CC} = 10V \end{cases}$$

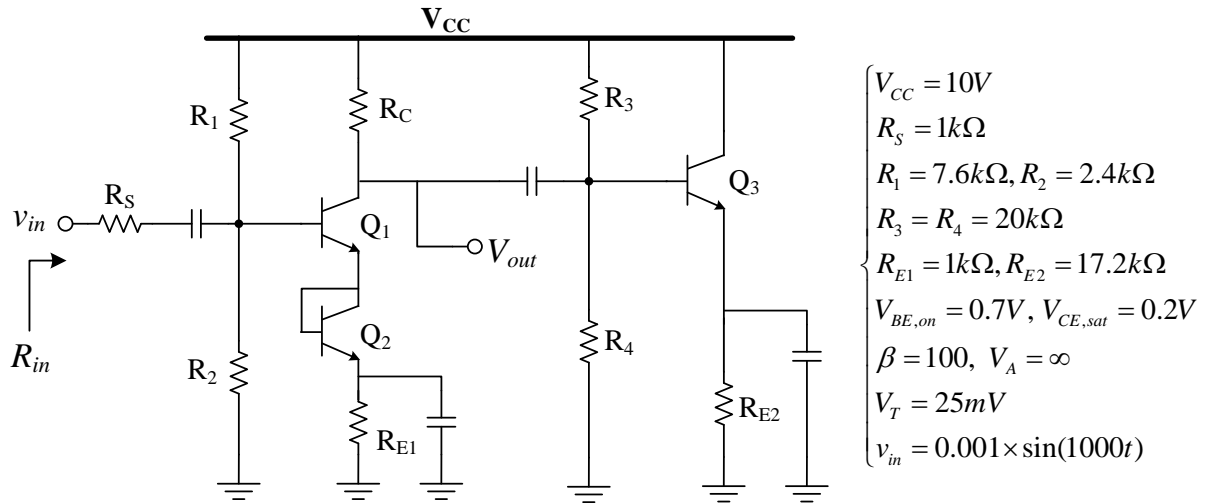7. a) Prove that the bias current of the transistor Q_1 is 1 mA. Assume that the transistor operates in F.A. region.
- b) Determine R_C so that $V_{CE1}=3.3$ V.
- c) Calculate the output voltage (V_{out}).



Good luck – M.R. Ashraf