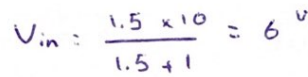


$$\beta = 100, |V_{be, on}| = 0.7^V, |V_{ce, sat}| = 0.2^V$$


$$10^3 \downarrow R_C + R_E \gg \frac{R_B}{\beta + 1} = 0.6^k$$

$$10 I_C = 5.3 \Rightarrow I_C = 0.53^{mA}$$
 می توان از میان پس صرف نظر کرد

b)

10V

3.3k Ω


10k Ω

8.2k Ω

(A)

(B)
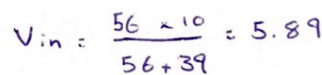
$$I_C = 0.808 \text{ mA} \quad V_{CE} = 0.72 \text{ V} > V_{CE, \text{sat}}$$



$$\text{KVL @ B: } -10 + i^* I_c + V_{CE} + 2.2 I_c = 0$$

$$I_c = 2.79 \text{ mA} \quad \text{V}_{CE} = 1.35 > V_{CE, \text{sat}}$$


#2. calculate the input resistance (R_i) as well as the voltage gain ($A_v = \frac{V_o}{V_i}$) in the circuit shown below.

$V_A = \infty$, $V_T = 25 \text{ mV}$, $\beta = 100$


capacitor in dc : open circuit

hint.

capacitor in ac : short circuit

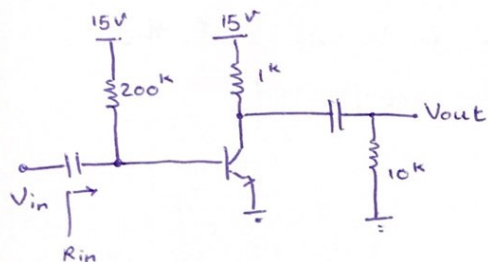

dc Analysis :

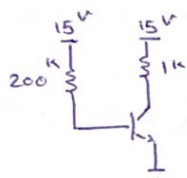


$$\text{KVL : } -15 + 200^k \left(\frac{I_C}{100} \right) + 0.7 = 0$$

$$\Rightarrow I_C = 7.15 \text{ mA}$$

$$\text{KVL : } -15 + 1^k I_C + V_{CE} = 0 \xrightarrow{I_C = 7.15 \text{ mA}} V_{CE} = 7.85 > V_{CE, \text{sat}}$$

ac Analysis :

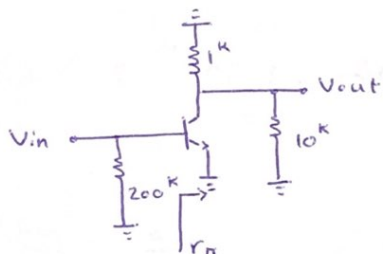

$$g_m = \frac{I_C}{V_T} = 40 \text{ mA/V} \quad I_C = 7.15 \text{ mA}$$


$$r_\pi = \frac{\beta}{g_m} = \frac{100}{40} = 2.5 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = \infty$$


$$A_v = \frac{V_{out}}{V_{in}} = -g_m R_c = -40 \left(10^k \parallel 1^k \right) = -259.99$$

$$R_{in} = 200^k \parallel r_\pi = 200^k \parallel 2.5^k \approx 2.3^k$$
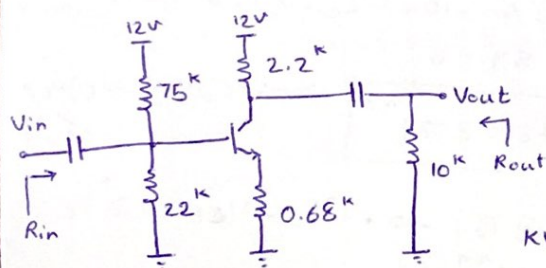
#3. In the following circuit, calculate the voltage gain, input resistance and output resistance. $V_{BE} = 0.6$, $V_{CE, \text{sat}} = 0.2$, $V_A = 100$, $V_T = 25 \text{ mV}$, $\beta = 100$



dc Analysis :

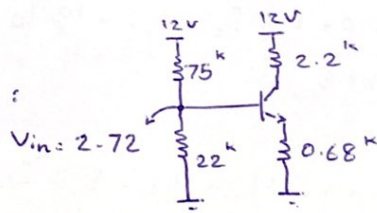

$$\text{KVL : } -2.72 + 22^k \parallel 75^k \left(\frac{I_C}{100} \right) + 0.6 + 0.68^k I_C = 0$$


$$\Rightarrow I_C = 2.5 \text{ mA}$$

$$\text{KVL : } -12 + 2.2^k I_C + V_{CE} + 0.68^k I_C = 0$$

$$\Rightarrow V_{CE} = 4.8 > V_{CE, \text{sat}}$$

ac Analysis: $g_m = 40 I_c = 40 \times 2.5 = 100 \text{ mmho}$, $r_{\pi} = \frac{\beta}{g_m} = \frac{100}{100} = 1^k$

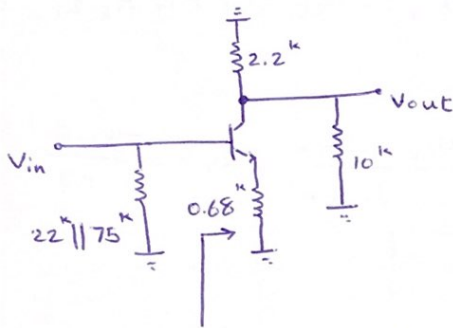$r_o = \frac{V_A}{I_c} = \frac{100}{2.5} = 40^k$



$A_v = \frac{V_{out}}{V_{in}} = \frac{-R_c}{R_E + r_m} = \frac{-(2.2^k \parallel 10^k)}{0.68^k + \frac{1}{100}} = -2.61$

$R_{in} = 22^k \parallel 75^k \parallel 70^k \approx 13.7^k$


$R_{out} = 10^k \parallel 2.2^k \parallel [40^k (1 + 100(0.68^k \parallel 1^k))] \approx 70^k$

$r_{\pi} + (1 + \beta) R_E = 1^k + 101(0.68^k) \approx 70^k$


hint:



$r_{\pi} + (\beta + 1) R_E$

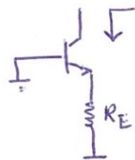

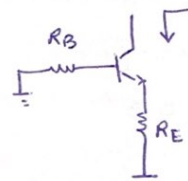$(1 + g_m r_o)(R_E \parallel r_{\pi}) + r_o$
 $\approx r_o (1 + g_m (R_E \parallel r_{\pi}))$




$r_o \left[1 + \frac{\beta R_E}{R_E + r_{\pi} + R_B} \right]$
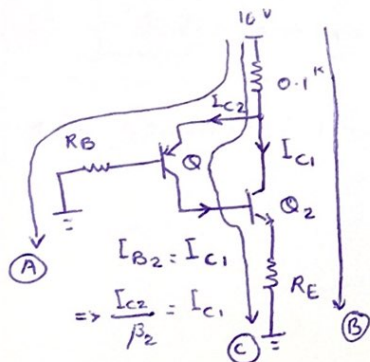
#4. In the following circuit:

- Determine the bias points of the transistors. Assume $R_E = \infty$
- Calculate the maximum value of R_E for which Q_1 remains in the active region.

$V_{CC} = 16^V$, $R_c = 0.1^k$, $R_B = 1500^k$, $V_{CE, sat} = 0.2^V$, $V_{BE, on} = 0.7$, $\beta_1 = 160$, $\beta_2 = 200$




a) KVL @ A: $-16 + 0.1^k (I_{C1} + I_{C2}) + 0.7 + 1500^k I_{B1} = 0$
 $\Rightarrow 9.475 I_{C1} + 0.1 I_{C2} = 15.3$ $\frac{I_{C2} = \beta_2 I_{C1}}{\beta_2 = 200}$
 $I_{C1} = 0.51 \text{ mA}$, $I_{C2} = 103 \text{ mA}$

KVL @ B: $-16 + 0.1 (I_{C1} + I_{C2}) + V_{CE2} = 0$
 $\Rightarrow V_{CE2} = 5.649 > V_{CE, sat}$

KVL @ C: $-16 + 0.1^k (I_{C1} + I_{C2}) + V_{CE1} + 0.7 = 0 \Rightarrow V_{CE1} = 4.95 > V_{CE, sat}$

b) $I_{C1} = 0.51 \text{ mA}$

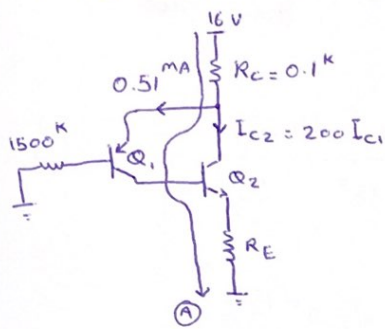

$$I_{B2} = I_{C1} = 0.51 \Rightarrow \frac{I_{C2}}{\beta_2} = 0.51$$

$$\Rightarrow I_{C2} = 200 (0.51) = 102 \text{ mA}$$

$$\text{KVL @ A: } -16 + 0.1^k (I_{C1} + I_{C2}) + V_{CE1} + 0.7 + R_E I_{C2} = 0$$


$$\Rightarrow 102 R_E = 5.049 - V_{CE}$$

$$R_E = \frac{5.049 - V_{CE}}{102} \xrightarrow[V_E \rightarrow \max]{V_{CE} \rightarrow \min} R_E = \frac{5.049 - 0.2}{102}$$

$$R_{E, \max} = 0.047^k = \boxed{47.5 \Omega}$$
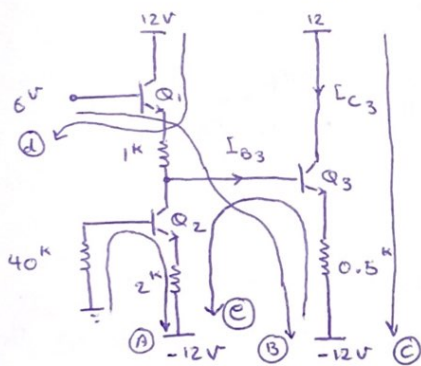
#5. In the circuit shown below, the transistors are the same. Determine the bias points.

$$\beta = 100, V_{BE, on} = 0.6 \text{ V}$$



$$\text{KVL @ A: } 40^k \left(\frac{I_{C2}}{100} \right) + 0.6 - 12 + 2^k I_{C2} = 0$$

$$\Rightarrow I_{C2} = 4.75 \text{ mA} = \boxed{I_{C1}}$$

$$\text{KVL @ B: } -6 + 0.6 + 1^k I_{C1} + 0.6 + 0.5^k I_{C3} - 12 = 0$$

$$\Rightarrow I_{C3} = \boxed{24.1 \text{ mA}}$$

$$\text{KVL @ C: } -12 + V_{CE3} + 0.5 I_{C3} - 12 = 0$$


$$\Rightarrow V_{CE3} = \boxed{11.95 \text{ V}}$$

$$\text{KVL @ d: } -12 + V_{CE1} - 0.6 + 6 = 0 \Rightarrow V_{CE1} = \boxed{6.6 \text{ V}}$$


$$\text{KVL @ e: } +12 - 0.5^k I_{C3} - 0.6 + V_{CE2} + 2^k I_{C2} - 12 = 0 \Rightarrow V_{CE2} = \boxed{3.15 \text{ V}}$$
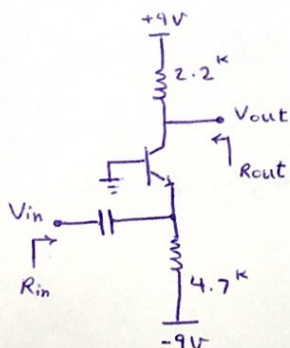
#6. Calculate the voltage gain, input resistance and output resistance of the following scheme.

$$V_{BE} = 0.7, V_{CE, \text{sat}} = 0.2, V_A = \infty, V_T = 25 \text{ mV}, \beta = 100$$



dc Analysis:

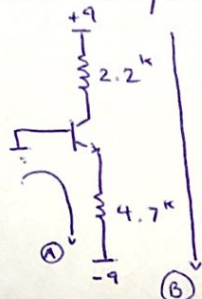

$$\text{KVL @ A: } +0.7 + 4.7^k I_C - 9 = 0$$


$$\Rightarrow I_C = \boxed{1.76 \text{ mA}}$$

$$\text{KVL @ B: } -9 + 2.2^k I_C + V_{CE} + 4.7^k I_C - 9 = 0$$

$$\Rightarrow V_{CE} = 5.85 \text{ V} > V_{CE, \text{sat}}$$

ac Analysis:
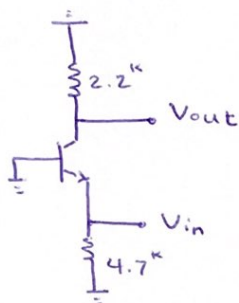
$$g_m = 40 I_c = 70.4 \text{ mho}, \quad r_{\pi} = \frac{\beta}{g_m} = 1.42 \text{ k}, \quad r_o = \infty$$




$$A_v = +g_m R_c = 70.4 \times 2.2 \text{ k} = 154.88$$

$$R_{out} = 2.2 \text{ k} \parallel \infty = 2.2 \text{ k}$$

$$R_{in} = 4.7 \text{ k} \parallel r_{\pi} = 0.013 \text{ k} = 13.9 \Omega$$


hint:

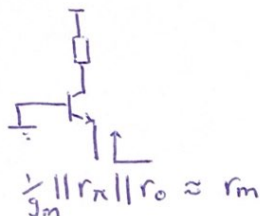


$$\frac{1}{g_m} \parallel r_{\pi} \parallel r_o \approx r_m$$
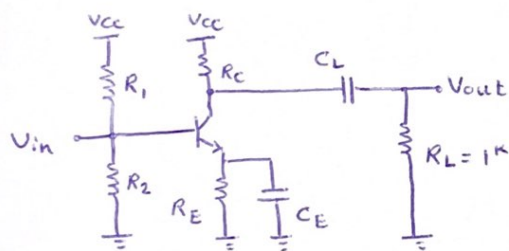
#7. In the following circuit, the voltage gain and the dc voltage drop on R_c is $-48 \frac{V}{V}$ and $3V$, respectively. Determine R_c .

$$V_{CE, \text{sat}} = 0V, \quad V_T = 25 \text{ mV}, \quad R_L = 1 \text{ k}$$




dc Analysis:

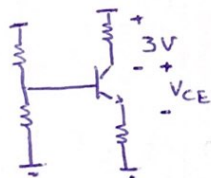

$$V_c = I_c R_c \Rightarrow I_c = \frac{3}{R_c}$$

$$g_m = 40 I_c = \frac{120}{R_c}$$

ac Analysis:

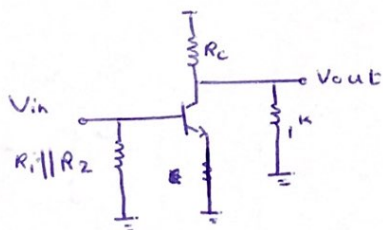

$$A_v = \frac{V_{out}}{V_{in}} = -g_m R_c = -\frac{120}{R_c} (R_c \parallel R_L) = -48$$

$$\frac{-120}{R_c} \left[\frac{R_c \times 1 \text{ k}}{R_c + 1 \text{ k}} \right] = -48 \Rightarrow R_c = 1.5 \text{ k}$$


#8. In the following circuit:

a) calculate the voltage gain ($V_{BE,on} = 0.7$)


b) determine the output voltage (V_o) swing.

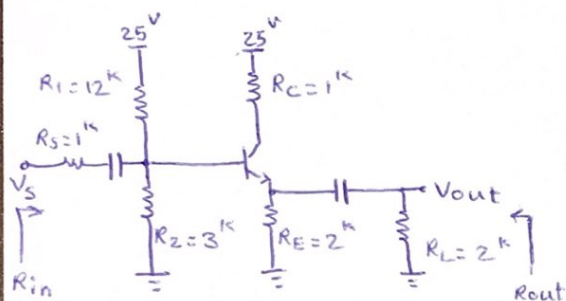c) Modify R_i in order to maximize the ~~ac~~ output voltage swing

$$V_{BE} = 0.6, V_{CE,sat} = 0.2V, V_A = \infty, V_T = 25mV, \beta = 80$$



DC Analysis:

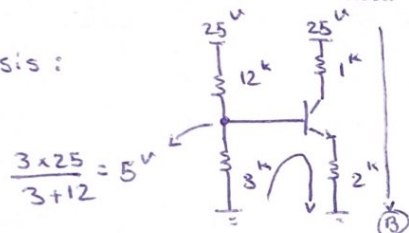


$$KVL: -5V + 3k \parallel 12k \left(\frac{I_C}{80} \right) + 0.6 + 2k I_C = 0$$

$$\Rightarrow I_C = 2.1mA$$

$$KVL @ C: -25 + 1k(2.1) + V_{CE} + 2k(2.1) = 0$$

$$\Rightarrow V_{CE} = 18.7 > V_{CE,sat}$$

ac Analysis:

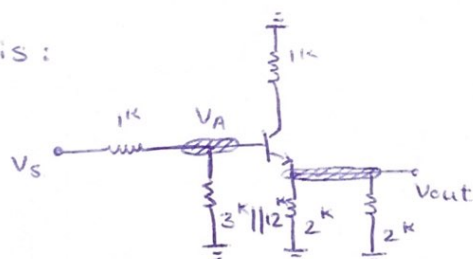

$$\begin{cases} g_m = 40 I_C = 40(2.1) = 84 \text{ mho} \\ \beta = 80 \\ r_\pi = \frac{\beta}{g_m} = 0.95k \\ r_o = \infty \end{cases}$$

$$A_v = \frac{V_{out}}{V_s} = \frac{V_{out}}{V_A} \times \frac{V_A}{V_s} = \left[\frac{R_E}{R_E + r_m} \right] \times \left[\frac{(3k \parallel 12k) \parallel r_\pi + (1+\beta)R_E}{(3k \parallel 12k \parallel r_\pi + (1+\beta)R_E) + 1} \right]$$

$$= \left[\frac{2k \parallel 2k}{2k \parallel 2k + \frac{1}{84}} \right] \times \left[\frac{3k \parallel 12k \parallel 80.95k}{(3k \parallel 12k \parallel 80.95k) + 1k} \right] \approx 0.98 \times 0.7 = 0.686 \frac{V}{V}$$

b) Swing V_o :

$$\text{Swing } V_{CE} = \min \{ V_{CE,Q} - V_{CE,sat}, R_{AC} I_C \}$$

$$R_{AC} = [R_E + R_C]_{in \text{ ac}}$$


$$= \min \{ 18.7 - 0.2, 2k \times 2.1mA \} = \min \{ 18.5, 4.2 \}$$

$$R_{OC} = [R_E + R_C]_{in \text{ dc}}$$

$$= 4.2 \Rightarrow \text{Swing } V_o = \frac{R_C}{R_C + R_E} \cdot \text{Swing } V_{CE} = 2.1V$$

c) $R_{ac} = 2^k$ $R_{dc} = 3^k$ $I_c = \frac{V_{cc} - V_{ce,sat}}{R_{ac} + R_{dc}} = \frac{25 - 0.2}{3 + 2} = 5^{mA}$

DC Analysis :

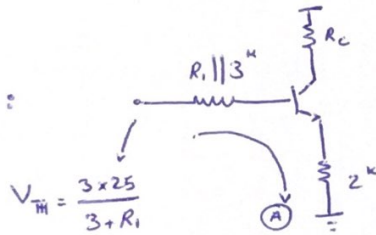

KVL @ A : $\frac{-75}{R_1 + 3} + 0.6 + 2(5^{mA}) = 0 \Rightarrow 10.6 R_1 = 43.2 \Rightarrow R_1 = 4^k$