

$$I_E = \frac{12 - 0.7}{(2 - \alpha) 20 k\Omega} \approx \frac{11.3}{20 k\Omega} = 0.565 \text{ mA}$$

(P-4)

$$C_T = \frac{C_1 C_2}{C_1 + C_2} + C_{CB} = 83.3 \text{ pF} + \frac{10 \text{ pF}}{\sqrt{1 + V_{CB}/0.7}}$$

$$V_{CB} = V_C - V_B = V_{CC} - 3f(t)$$

$$C_T = 83.3 \text{ pF} + \frac{10 \text{ pF}}{\sqrt{1 + \frac{12 - 3f(t)}{0.7}}} = 83.3 \text{ pF} + \frac{2.34 \text{ pF}}{\sqrt{1 - 0.23f(t)}} \approx 83.3 \text{ pF} + 2.34 \text{ pF} + \frac{0.23}{2} f(t)$$

$$\omega(t) = \frac{1}{\sqrt{L C_T}} = \frac{1}{\sqrt{1.2 \mu\text{H} (85.64 + 0.115f(t))}} + \dots$$

$$\omega(t) = \frac{1}{\sqrt{1.2\mu H \times 85.64 \text{ pF}}} \sqrt{1 + 0.0013 f(t)}$$

$$\omega(t) = 9.864 \times 10^6 \left(1 - \frac{0.0013}{2} f(t) + \dots \right)$$

$$= \underbrace{9.864 \times 10^6}_{\omega_0} - \underbrace{6.411 \times 10^3}_{\Delta \omega} f(t)$$

$\frac{1}{16}$ سرعت
فرط

$\frac{1}{16}$ /
الحرارة

$$G_m = \frac{G_L}{n(1-n/\alpha)} = \frac{1/2kT}{1/6(1-1/6)} = 3.6 \text{ mS}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.565}{0.025} = 22.6 \text{ mS}$$

$$n = \frac{C_1}{C_1 + C_2} = \frac{100}{600} = 1/6$$


$$\frac{G_m}{g_m} = 0.16 \rightarrow \chi \approx 13$$

مودعاً $\hookrightarrow V_i = V_T \cdot \chi = 0.325$

$$V_o = 1/n \cdot V_i = 1.95 \text{ Volt} \quad \begin{matrix} \text{راسبوند} \\ \text{حربي} \end{matrix}$$

$$v_o(t) = 1.95 \cos(\omega_0 + \Delta\omega \int f(\tau) d\tau)$$

8-4

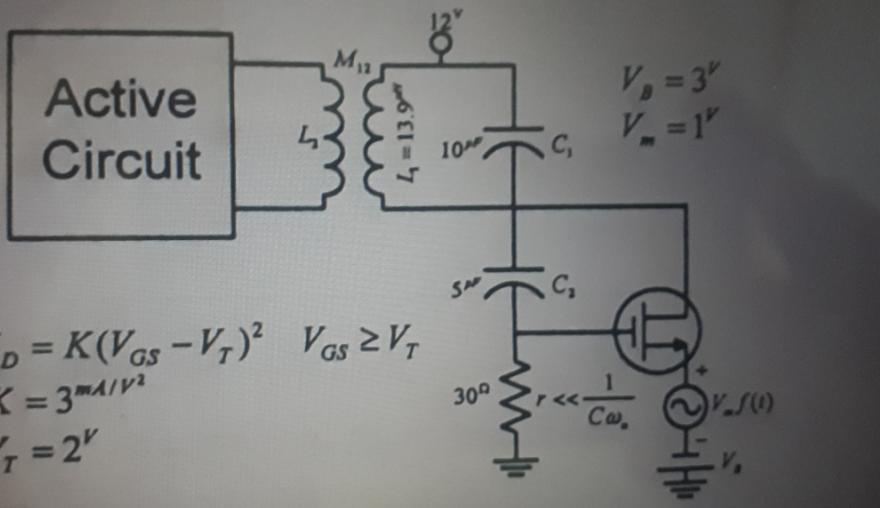

$$I_D = K(V_{GS} - V_T)^2 \quad V_{GS} \geq V_T$$

$$K = 3 \text{ mA/V}^2$$

$$V_T = 2 \text{ V}$$

$$\begin{aligned} & \text{Circuit diagram showing a } 3\text{ }\Omega \text{ resistor in series with a } 12\text{ V DC source, followed by a } 3\text{ V DC source.} \\ & V_{GS} = 3 \rightarrow I_D = K(V_{GS} - V_T)^2 \\ & I_D = 3(3 - 2)^2 = 3 \text{ mA} \end{aligned}$$

$$\begin{aligned} g_m(t) &= 2K(V_{GS} - V_T) = 2 \times 3 \times (-V_m f(t) + V_B - 2) \\ &= 6(1 - f(t)) \end{aligned}$$

$$V_{C_1} \approx V_{C_2} \rightarrow \text{جایزه صفری کوئی نداشته باشد}$$

$$i_{C_2} = C_2 \frac{dV_{C_2}}{dt} \approx C_2 \frac{dV_{C_1}}{dt}$$

$$V_r = i_{C_2} r = r C_2 \frac{dV_{C_1}}{dt}$$

$$i_D = g_m V_r = \frac{6(1 - f(t))}{m \omega} r C_2 \frac{dV_{C_1}}{dt}$$

$$i_D = 6 \times 10^{-3} \times 30 \times 5 \times 10^{-12} (1 - f(t)) dV_{C_1} / dt$$

جزءیت خازن تغیر

$$C_{\text{tot}} = C_1 + C(t)$$

$$C_{\text{tot}}(t) = 10 \text{ pF} + 0.9 \text{ pF} (1 - f(t))$$

$$f(t) = \frac{1}{2\pi \sqrt{L_1 C_{\text{tot}}(t)}} = \frac{1}{2\pi \sqrt{L_1 \times 10.9 \text{ pF} \left(1 - \frac{0.9 f(t)}{10.9}\right)}}$$

$$= \underbrace{\frac{1}{2\pi \sqrt{L_1 \times 10.9 \text{ pF}}}}_{\text{(constant)}} \left(1 + \frac{0.9}{2 \times 10.9} f(t) + \dots\right)$$

$$f_0 = 15.92 \text{ MHz} = \frac{1}{2\pi \sqrt{L_1 \times 10.9 \text{ pF}}}$$

$$\cancel{L_1 = 9.17 \mu\text{H}}$$

$$\Delta f = f_0 \times \frac{0.9}{2 \times 10^{-9}}$$

أجزاء خطأ

معادلة FET لـ Δf هي $\Delta f = f_0 \times \frac{0.9}{2 \times 10^{-9}}$

لذلك $f_0 = \frac{\Delta f}{0.9 \times 10^{-9}}$


$$V_r = i C_2(t) \cdot r = C_2 r \frac{d V_2(t)}{dt} \approx C_2 r \frac{d V_i(t)}{dt}$$

$$V_r = C_2 r j \omega(t) V_i$$

$$|V_r| \approx |C_2 r \omega_0 V_i|$$

$$V_r = 5 \times 10^{-12} \times 3 \times 2\pi \times 15.92 \times 10^6 \times 4$$

$$V_r = 6 \text{ mV}$$

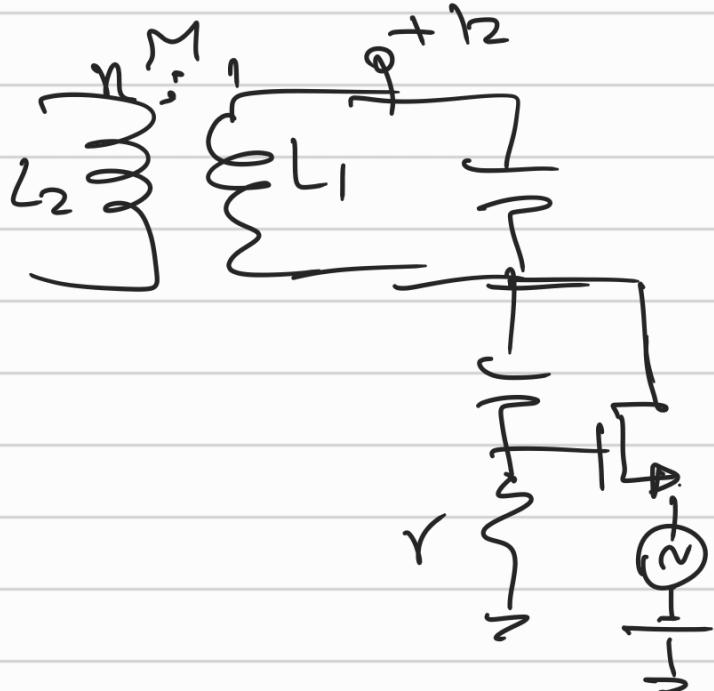



$$n = \frac{M}{L_1}$$

اگر کو امپیو طرف
۵ Volt بین L1 و L2

$$n = \frac{V_2}{V_1} = \frac{5}{4} = 1.25$$

$$M = n L_1 = 1.25 \times 9.17 \mu H$$

V - 4

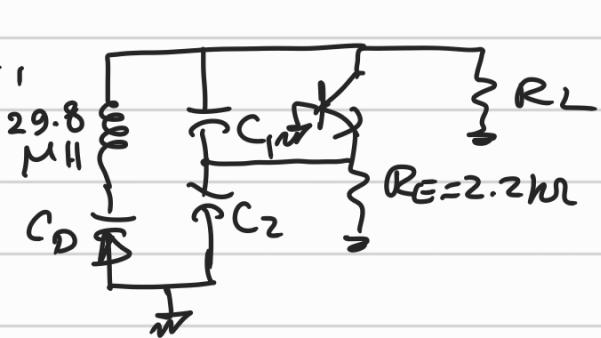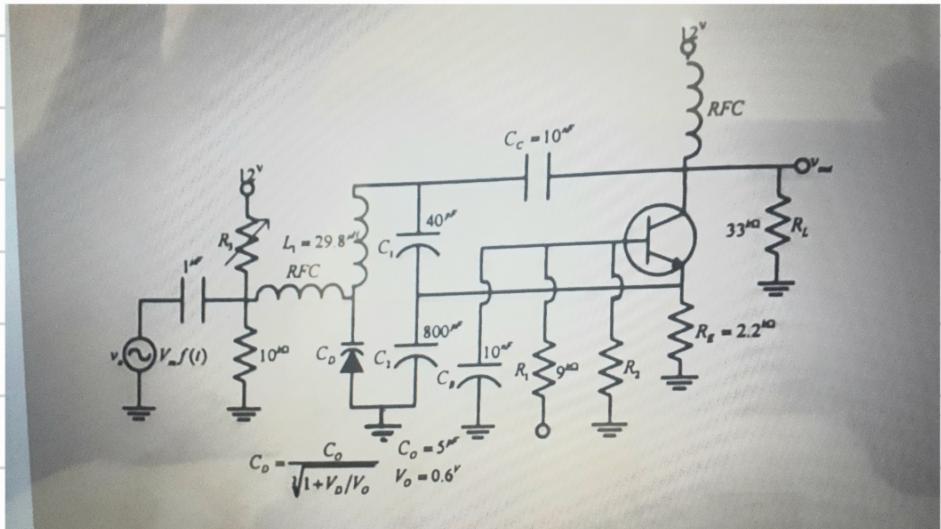

حالت شبه مفرناخ که می تواند
جذب سیگنال را بزرگ کند.

$$j \frac{C_1 C_2}{C_1 + C_2} \omega_0 + \frac{1}{j \omega_0 L_1 + \frac{1}{j \omega_0 C_D}} = 0$$

$$j \frac{C_1 C_2}{C_1 + C_2} \omega_0 + \frac{j \omega_0 C_D}{1 - \omega_0^2 L_1 C_D} = 0$$

$$\frac{C_1 C_2}{C_1 + C_2} = \frac{C_D}{\omega_0^2 L_1 C_D - 1}$$


$$C_D = \frac{\frac{C_1 C_2}{C_1 + C_2}}{\frac{C_1 C_2}{C_1 + C_2} \omega_0^2 L_1 - 1} = \frac{\frac{840}{10^{-12} 40 \times 800 \times (20 \times 10^6)^2 \times 29.8 \times 10^{-1}}} {\frac{840}{10^{-12} 40 \times 800 \times (20 \times 10^6)^2 \times 29.8 \times 10^{-1}}}$$

$$C_D = 2.25 \text{ pF}$$

$$C_D = \frac{C_0}{\sqrt{1 + VD/N_0}} = \frac{SPF}{\sqrt{1 + VD/0.6}} = 2.25 \text{ pF}$$

$$V_D = 2.36 \text{ Volt}$$
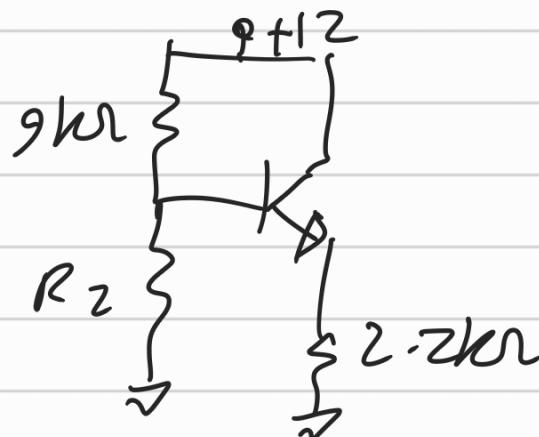
$$V_D = \frac{12}{R_3 + 10k\Omega} \times 10k\Omega \rightarrow R_3 = 40.89k\Omega$$



$$\left. \begin{array}{l} V_o = 11 \text{ Volt} \\ V_o = \frac{V_i}{n} \Rightarrow V_i = 0.523 \end{array} \right\}$$

$$n = \frac{C_1}{9 + C_2} = 0.0476$$

$$G_m = \frac{G_L + n^2 G_E}{n(1 - n/\alpha)} = \frac{1/33 + 0.002267 \times 1/2.2}{0.0476(1 - \frac{0.0476}{1})}$$


$$G_m = 0.691$$

$$V_i = \alpha \cdot V_T \Rightarrow \alpha = \frac{0.523}{0.025} = 20.92$$

$$V_A = I_{EQ} (R_E + (1-\alpha) R_B) . \xrightarrow{\alpha=1} = I_{EQ} \cdot R_E$$

$$g_m = \frac{\alpha I_{EQ}}{V_T}$$

$$V_A = g_m V_T R_E$$

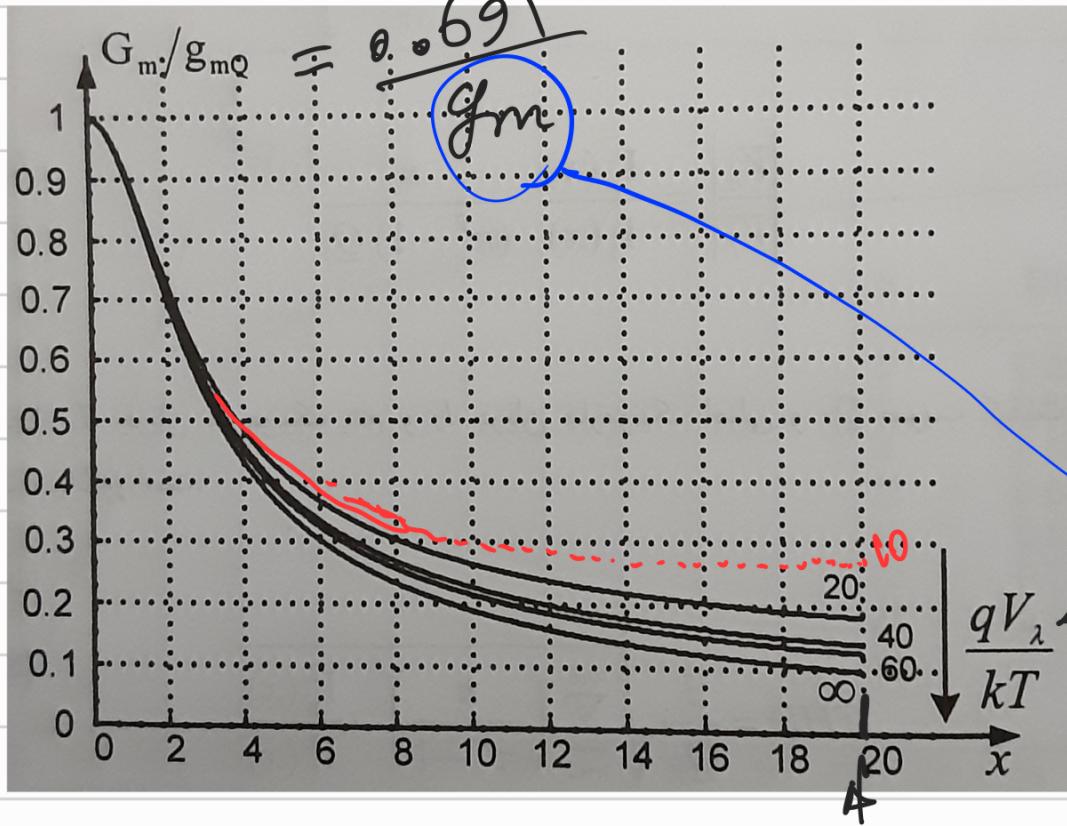

$$\frac{V_A}{V_T} = g_m R_E$$

$$g_m = 5 \text{ mS}$$

~~0.5~~

$$\eta = 20.92$$

$$g_m = \frac{\alpha I_{EQ}}{V_T} \Rightarrow I_{EQ} = 0.025 \times 5 = 0.125 \text{ mA}$$

$$I_{EQ} = \frac{V_{TH} - V_{BE}}{\frac{R_{TH}}{\beta+1} + R_E} \approx \frac{\frac{12}{9+R_2} \times R_2 - 0.7}{2.2} = 0.125 \text{ mA}$$



$$R_2 = 0.796 \text{ k}\Omega$$

$$\frac{C_1 C_2}{C_1 + C_2} = \frac{C_D}{\omega^2(t) L_1 C_D - 1}$$

EINL; J
-

$$\omega^2(t) = \frac{1 + \frac{C_1 C_2}{C_1 + C_2} \times \frac{1}{CD}}{\frac{C_1 C_2}{C_1 + C_2} L_1}$$

$$\omega(t) = \sqrt{\frac{1 + \frac{C_1 C_2}{C_1 + C_2} \times \sqrt{1 + \frac{V_D + V_m f(t)}{V_o}}}{\sqrt{\frac{C_1 C_2}{C_1 + C_2} L_1}}} \quad \omega_0$$

$$\omega(t) = \sqrt{\frac{1 + \frac{C_1 C_2}{(C_1 + C_2) C_0} \sqrt{1 + \frac{V_D}{V_o}}}{\sqrt{\frac{C_1 C_2}{C_1 + C_2} L_1}}} \times \sqrt{1 + \frac{V_m f(t)}{V_o (1 + \frac{V_D}{V_o})}}$$

$$\omega(t) = \omega_0 \cdot \sqrt[4]{1 + \frac{V_m f(t)}{V_o (1 + \frac{V_D}{V_o})}}$$

$$\omega(t) \approx \omega_0 \left(1 + \frac{V_m f(t)}{4V_o (1 + V_D/V_o)} \right)$$

$$\Delta \omega = \frac{\omega_0 V_m}{4V_o (1 + V_D/V_o)} = \frac{125.6 \times 10^6 \times V_m}{4 \times 0.6 (1 + \frac{2.36}{0.6})} = 22 \times 10^6$$

$$V_m = 0.088$$

