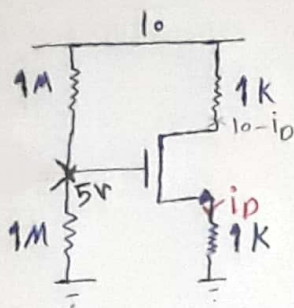


DC



$$V_{TH} = 2V$$

$$\mu_n C_{ox} \frac{W}{L} = \frac{1}{2} \frac{mA}{V^2} = \beta$$

$$\lambda = 0 V^{-1}$$


$$V_{GS} = 5 - i_D \rightarrow \text{من } i_D \text{ min } \rightarrow \text{ } i_D$$

$$i_D = \frac{1}{4} (5 - i_D - 2)^2 \rightarrow 4i_D = (3 - i_D)^2$$

$$i_D^2 - 10i_D + 9 = 0 \rightarrow (i_D - 1)(i_D - 9) = 0 \rightarrow i_D = 1mA$$

$$V_{GD} < V_{TH} \rightarrow V_{GD} = 5 - 10 + i_D = -4 < 2V \rightarrow \text{نقص في الجهد}$$

5.50

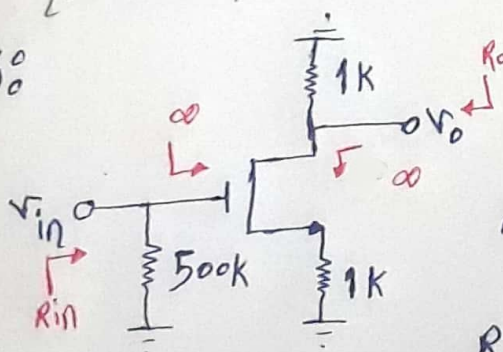


$$g_m = 2\sqrt{\frac{\beta}{2} \times i_D} = 2\sqrt{\frac{1}{4} \times 1} = 1mA/V$$

$$A_v = \frac{v_o}{v_{in}} = \frac{-R_D}{R_S + \frac{1}{g_m}} = \frac{-1}{1+1} = -\frac{1}{2}$$

$$R_{in} = 500k \parallel \infty = 500k\Omega$$
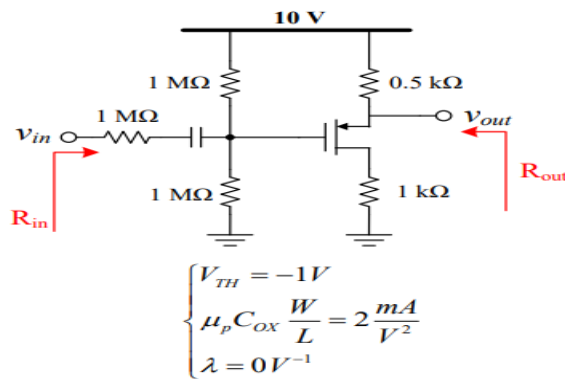
$$R_{out} = 1k \parallel \infty = 1k\Omega$$





DC

$V_{TH} = -1$
 $\beta = 2 \frac{mA}{V^2}$
 $\lambda = 0$
 $V_{SG} = 5 - \frac{i_D}{2}$
 $i_D = K (V_{SG} - |V_{TH}|)^2 \rightarrow i_D = \left(5 - \frac{i_D}{2} - 1\right)^2$

$(i_D - 4)(i_D - 16) = 0 \rightarrow i_D = 4mA$
 $V_{GD} > V_{TH} \rightarrow V_{GD} = 5 - i_D = 1V > -1 \rightarrow$ اشباع
 $g_m = 2\sqrt{K i_D} = 2\sqrt{1 \times 4} = 4mS$
 $\frac{v_o}{v_{in}} = \frac{R_S}{R_S + \frac{1}{g_m}} = \frac{\frac{1}{2}}{\frac{1}{2} + \frac{1}{4}} = \frac{\frac{1}{2}}{\frac{3}{4}} = \frac{2}{3}$
 $\frac{v_{in}}{v_{in}} = ?$
 $A_v = \frac{v_o}{v_{in}} = \frac{1}{3} \times \frac{2}{3} = \frac{2}{9}$
 $R_{in} = 1M + 500k = 1.5M\Omega$
 $R_{out} = \frac{1}{2}k \parallel R_{\pi}$
 $R_{\pi} = \frac{1}{g_m} = \frac{1}{4}$
 $\rightarrow R_o = \frac{1}{2} \parallel \frac{1}{4} = \frac{1}{6}k\Omega$

a) Specify the source resistance so that $I_D = 2.5 \text{ mA}$.

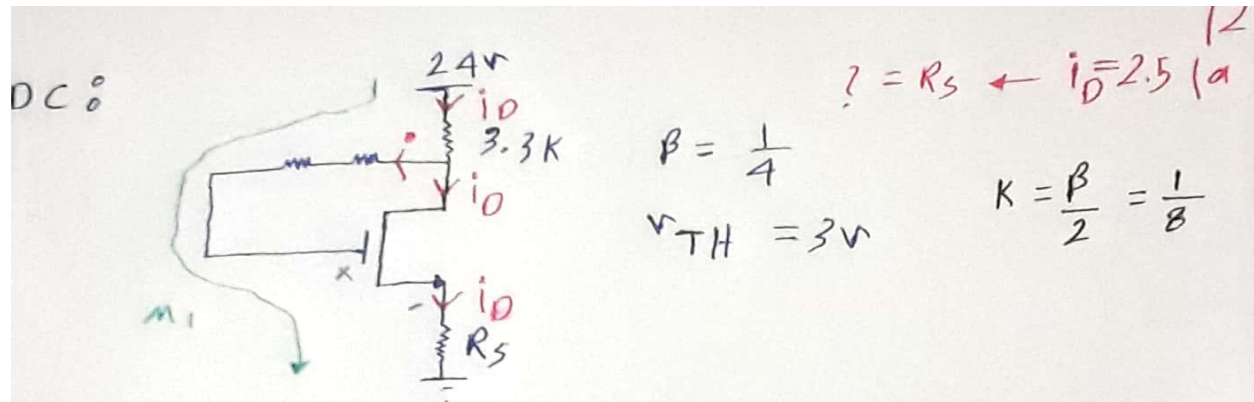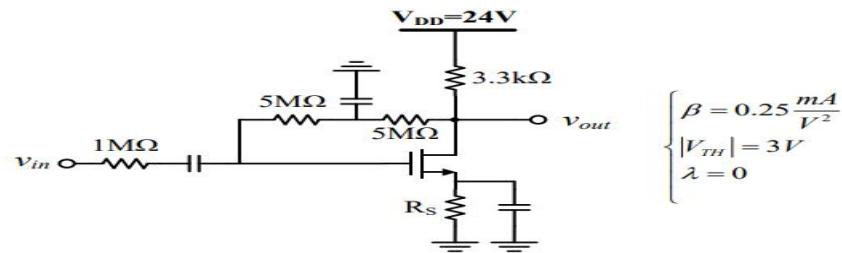b) Calculate the voltage gain and the input and the output resistances.




$$\text{KVL @ } M_1: -24 + 3.3i_D + v_{GS} + R_S i_D = 0 \quad (I)$$

$$v_{GS} = v_{TH} + \sqrt{\frac{i_D}{K}} = 3 + \sqrt{\frac{5 \times 8}{2}} = 7.5 \text{ V} > 3 \text{ V} \quad \text{tr روشن}$$

$$(I) \rightarrow \frac{5}{2} R_S = 24 - v_{GS} - 3.3 \times \frac{5}{2} \rightarrow R_S = 3.3 \text{ k}\Omega$$

$$? = R_{out} \text{ و } R_{in} \quad , \quad \frac{v_o}{v_{in}} = A_v \quad (b)$$
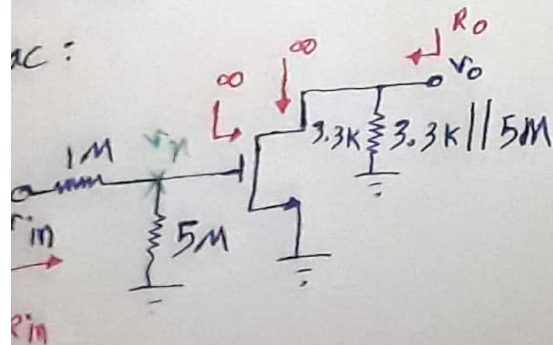
$$r_o = r_{ds} = \infty \quad g_m = 2\sqrt{K i_D} = 2\sqrt{\frac{1}{8} \times \frac{5}{2}} = 1.1 \text{ mS}$$



$$\frac{v_o}{v_{in}} = \frac{v_o}{v_n} \times \frac{v_n}{v_{in}} = ?$$


$$\frac{v_o}{v_n} = -g_m R_D = -1.1 \times 3.3 = -3.63$$

$$\frac{v_n}{v_{in}} = \frac{5 \parallel \infty}{(5 \parallel \infty) + 1} = \frac{5}{6} \rightarrow \frac{v_o}{v_{in}} = -3$$

$$R_{out} = 3.3 \parallel \infty = 3.3 \text{ k}\Omega = R_o$$

$$R_{in} = 1\text{M} + 5\text{M} = 6\text{M}\Omega = R_{in}$$

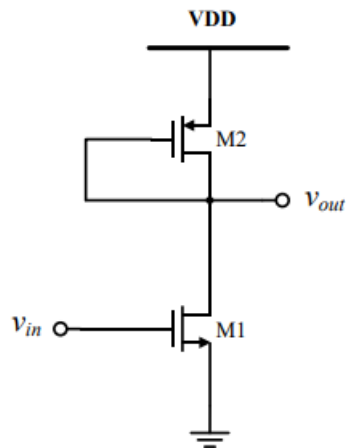- 3- Determine a relation for the voltage gain ($A_v = \frac{v_{out}}{v_{in}}$) of the following circuits. Assume that the transistors operate in saturation and $\lambda \neq 0$.



Handwritten notes and equivalent circuit for the common-source amplifier:



Top right: $\lambda \neq 0$ ترانسistor درنا صبه اشباع و $\frac{v_o}{v_{in}} = -3$


Left side: Small-signal equivalent circuit showing transistors M_1 and M_2 with their respective output resistances r_{o1} and r_{o2} . The input v_{in} is applied to the gate of M_1 , and the output v_o is taken from the common source node.

Right side: Equivalent circuit for the common source node. It shows the input v_{in} connected to the gate of M_1 , which is in parallel with r_{o1} and r_{o2} . The output v_o is taken from the common source node, which is also in parallel with $\frac{1}{g_{m2}}$.

Bottom right: The voltage gain equation:
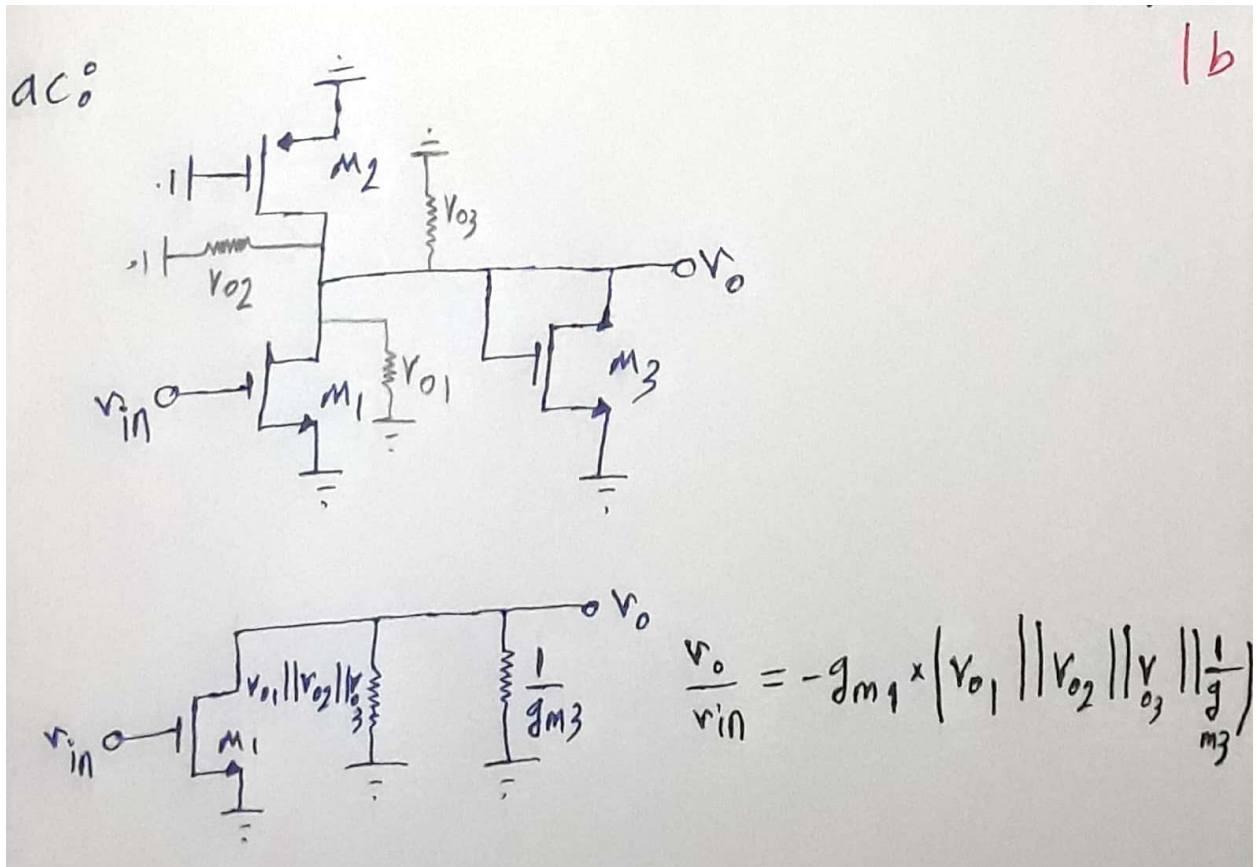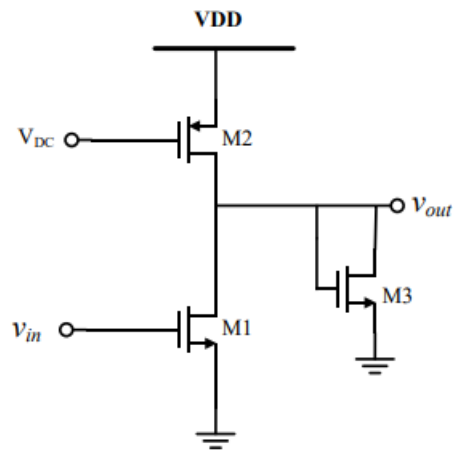
$$\frac{v_o}{v_{in}} = -g_{m1} \times (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}})$$



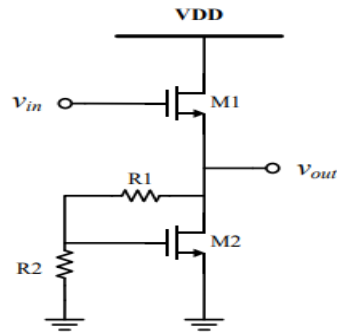

10

روش اول محاسبه R_2

KCL @ A: $g_{m2} v_{gs} - i_T + \frac{v_{gs}}{R_2} = 0 \rightarrow$

$(g_{m2} + \frac{1}{R_2}) v_{gs} = i_T \quad (I)$

KVL @ M_1 : $-v_T + \frac{R_1}{R_2} v_{gs} + v_{gs} = 0 \rightarrow$

$\frac{R_1 + R_2}{R_2} v_{gs} = v_T \rightarrow v_{gs} = \frac{R_2 v_T}{R_1 + R_2} \quad (II)$

$v_T \left(\frac{R_2 g_{m2}}{R_1 + R_2} + \frac{1}{R_1 + R_2} \right) = i_T \rightarrow \frac{v_T}{i_T} = \frac{R_1 + R_2}{R_2 g_{m2} + 1}$



در حد اول محاسبه

$$\frac{v_T}{i_T} = \frac{R_1 + R_2}{R_2 g_{m2} + 1} \times \frac{R_2}{R_2} = \frac{R_1 + R_2}{R_2} \times \left(R_2 \parallel \frac{1}{g_{m2}} \right)$$


$$R_2 = V_{o2} \parallel \left(\frac{R_1 + R_2}{R_2} \parallel \frac{1}{g_{m2}} \right) \checkmark$$

روش دوم برای محاسبه R_2

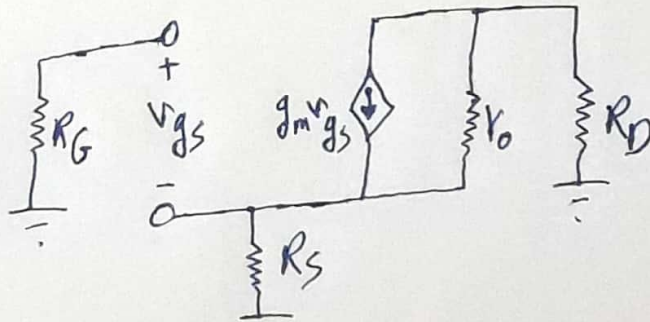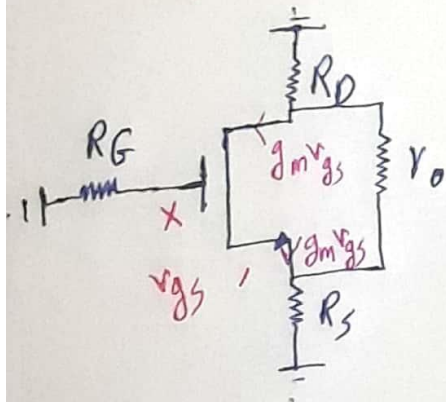روش بخش جریان جست محاسبه R_{in} و R_{out}



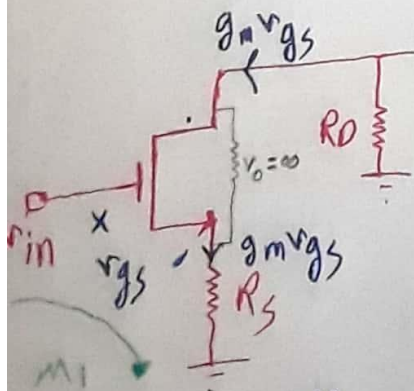مثال: بهره تقویت کننده $\lambda = 0$ از روش بخش جریان جست است. $(\lambda = 0) \Rightarrow r_o = \infty$




$$v_{gs} = \frac{v_{in}}{g_m R_S + 1}$$

$$KCL @ v_o: v_o = -g_m v_{gs} R_D = \frac{-g_m R_D v_{in}}{g_m R_S + 1}$$

$$\frac{v_o}{v_{in}} = \frac{-g_m R_D}{g_m R_S + 1} \times \frac{\frac{1}{g_m}}{\frac{1}{g_m}} = \frac{-R_D}{R_S + \frac{1}{g_m}} = A_v$$

مسابه R_2 از روش بخش بر جان °

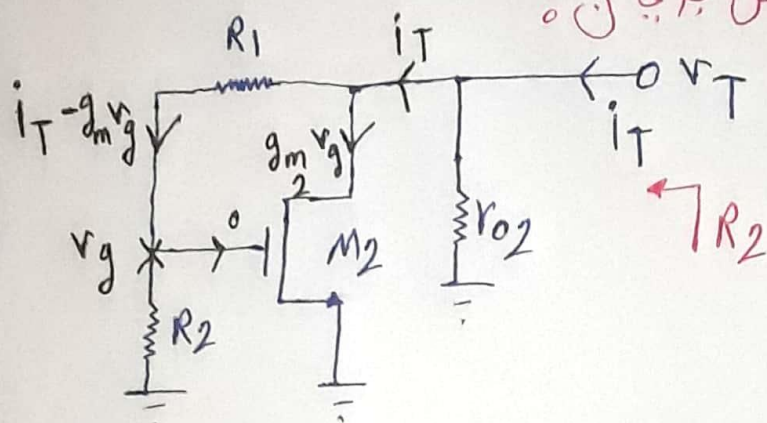


$$R_2 = V_{o2} \parallel \frac{v_T}{i_T} \quad v_g = \frac{R_2 v_T}{R_1 + R_2}$$

$$v_{gs2} = v_g$$



$$KCL @ v_g : \frac{v_g}{R_2} = i_T - g_{m2} v_g \rightarrow \left(\frac{1}{R_2} + g_{m2} \right) v_g = i_T$$

$$\left[\frac{1}{R_1 + R_2} + \frac{R_2 g_{m2}}{R_1 + R_2} \right] v_T = i_T \rightarrow \frac{v_T}{i_T} = \frac{R_1 + R_2}{R_2 g_{m2} + 1} \times \frac{R_2}{R_2}$$

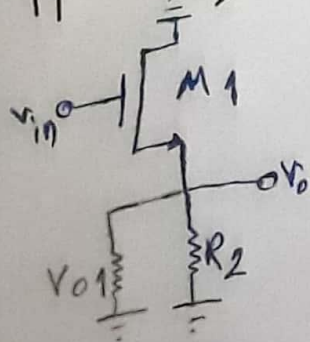
$$\frac{v_T}{i_T} = \frac{R_1 + R_2}{R_2} \left(R_2 \parallel \frac{1}{g_{m2}} \right) \rightarrow R_2 = V_{o2} \parallel \left[\frac{R_1 + R_2}{R_2} \left(R_2 \parallel \frac{1}{g_{m2}} \right) \right]$$



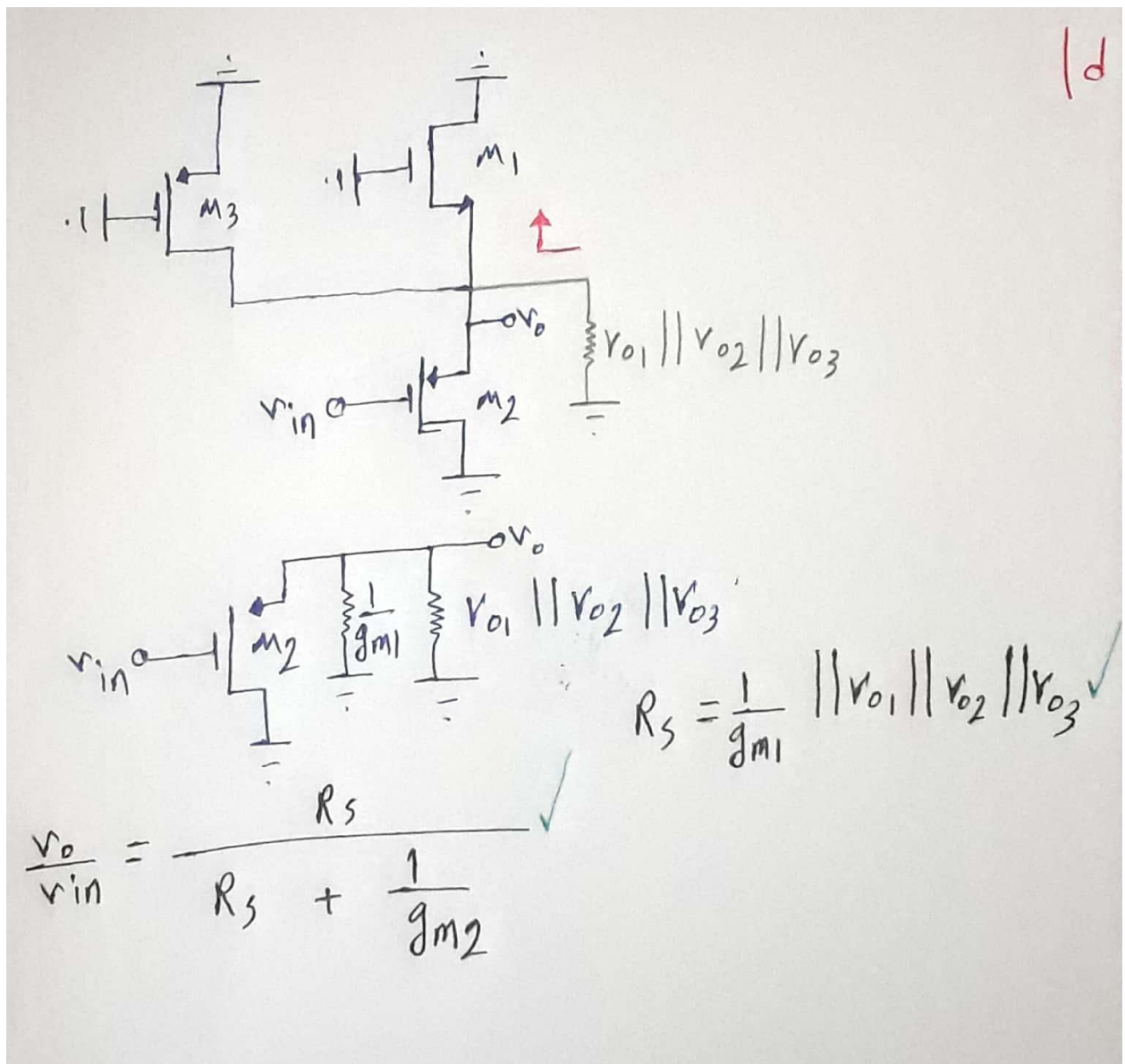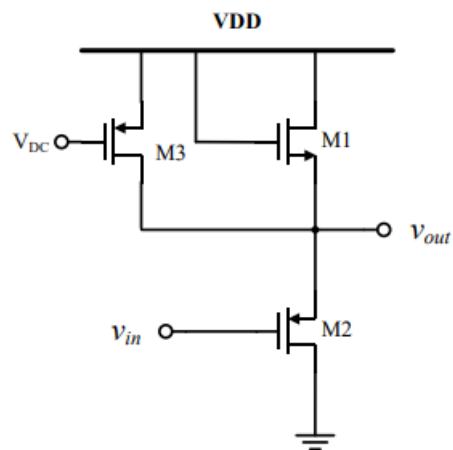
$$\frac{v_o}{v_{in}} = \frac{R_2 \parallel V_{o1}}{R_2 \parallel V_{o1} + \frac{1}{g_{m1}}} \quad \checkmark$$



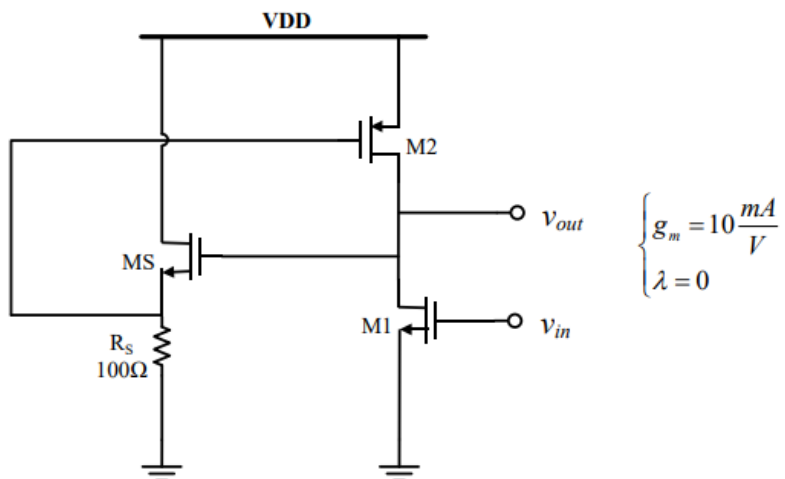- 4- Draw the small-signal model of the following circuit and calculate the voltage gain. Assume that all of the transistors are in saturation.




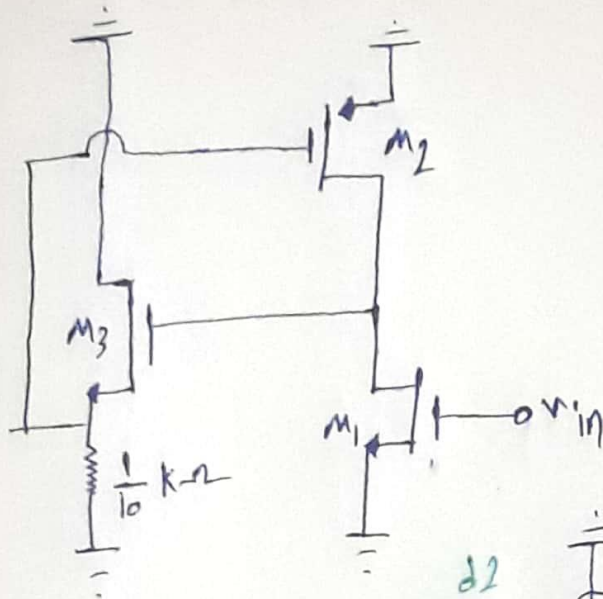4) در ناحیه اشتباع جایس شده $V_{DS} > V_{GS} - V_{th}$ و $V_{GS} > V_{th}$



$$V_o = \infty$$

$$g_m = 10 \text{ mS}$$

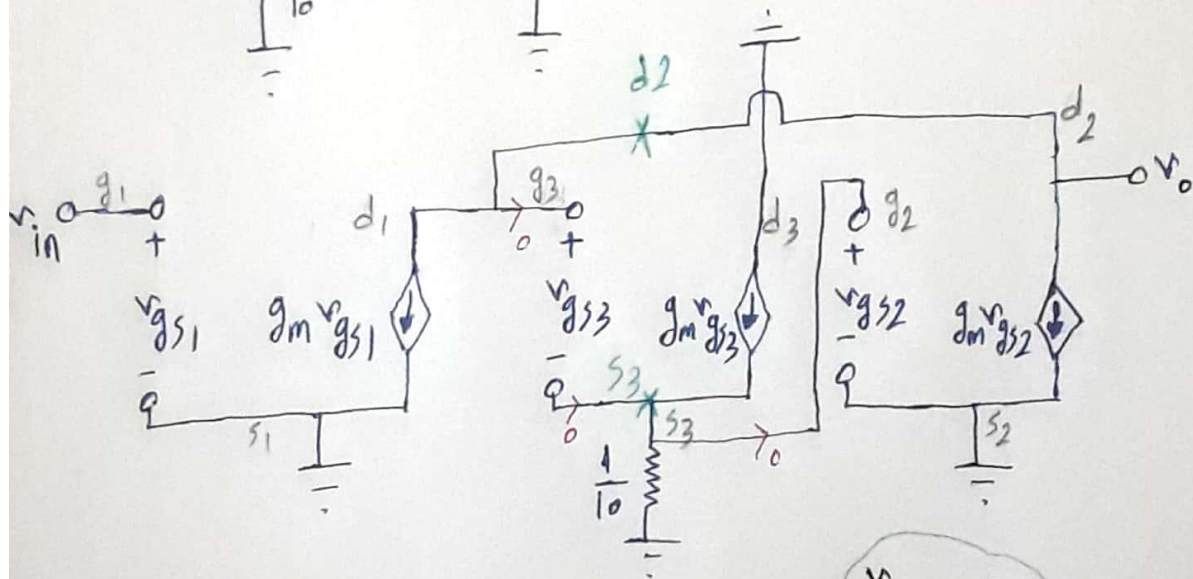

$$v_{gs1} = v_{in} \quad (I)$$


$$\frac{v_o}{v_{in}} = -2$$

$$\text{KCL @ } d2: g_m v_{gs1} = -g_m v_{gs2} \xrightarrow{(I)} v_{gs2} = -v_{in}$$

$$\text{KCL @ } s3: v_{s3} = \frac{1}{10} g_m v_{gs3} = v_{gs3} \quad (II) \quad v_{s3} = v_{gs2} = -v_{in}$$

$$v_{gs3} = -v_{in} \quad v_{gs3} = v_o - v_{s3} \rightarrow v_o = v_{gs3} + v_{s3} = -2v_{in}$$

حل با استفاده از پخش جریان

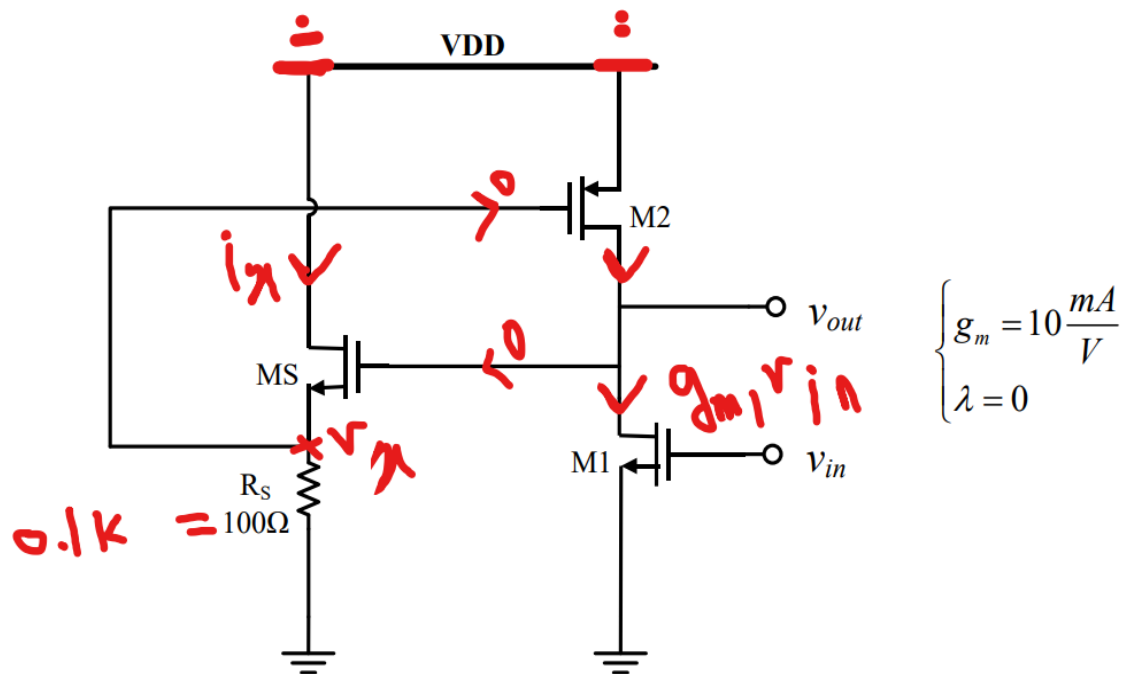




$$v_{gs2} = v_n$$

$$i_{d2} = g_m v_n = -g_m v_{in} \rightarrow v_n = -v_{in} \quad (I)$$

$$i_n = g_m (v_o - v_n) = 10 v_n \rightarrow 2v_n = v_o \rightarrow v_o = -2v_{in}$$


$$A_v = \frac{v_o}{v_{in}} = -2 = \frac{v_o}{v_{in}}$$

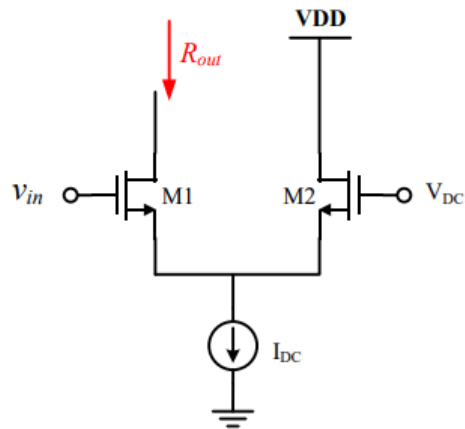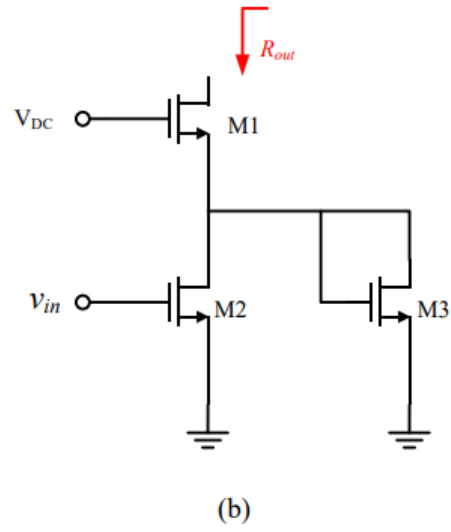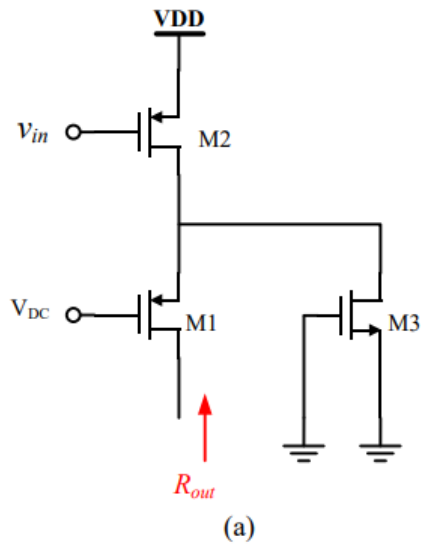5- Specify a relation for the output resistance of the following circuits. Assume $\lambda \neq 0$.



ac)


$$? = R_{out} / 5$$

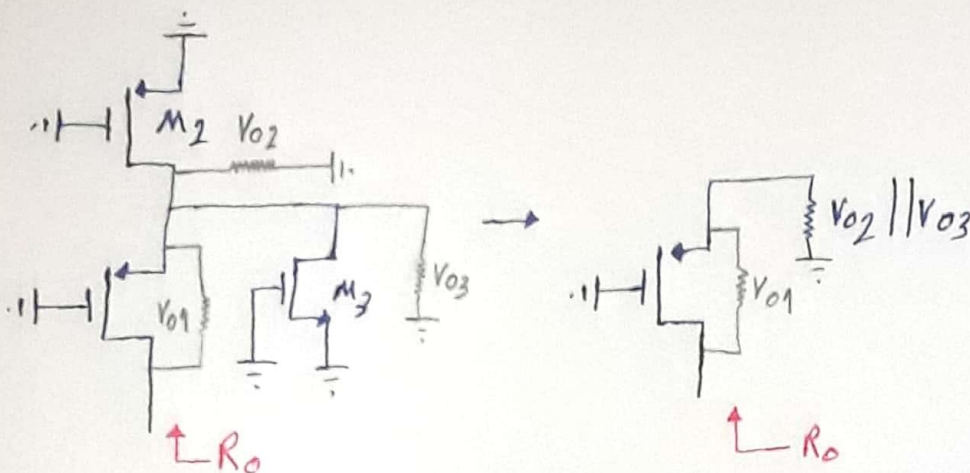

$$R_o \approx r_{o1} (1 + g_{m1} (r_{o2} || r_{o3}))$$

b


ac)

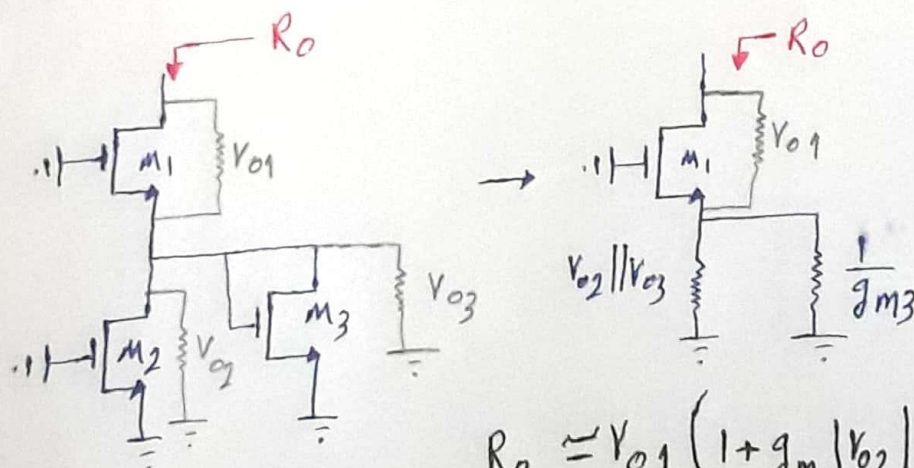

$$R_o \approx r_{o1} (1 + g_{m1} (r_{o2} || r_{o3} || \frac{1}{g_{m3}}))$$

c

5.5)

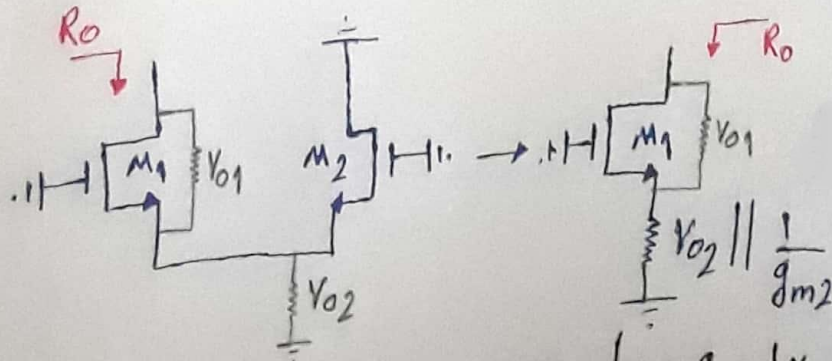

$$R_o = r_{o1} (1 + g_{m1} (r_{o2} || \frac{1}{g_{m2}}))$$