

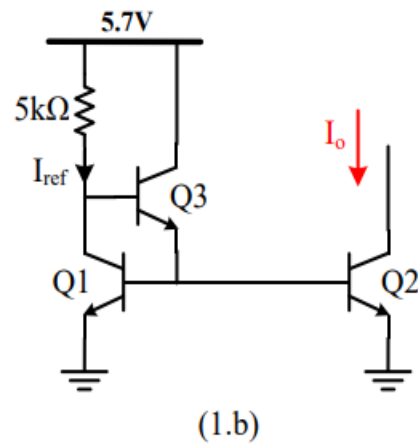


1- For the following circuits, the transistors are the same and  $V_{BE} = 0.7V$ .

- Calculate  $I_{ref}$  in fig. 1.a.
- Determine  $I_o / I_{ref}$  in terms of  $\beta$  and compute its value for  $\beta = 50, \beta = 200, \beta = \infty$ . Discuss about the results (Fig. 1.a).
- In order to alleviate the undesirable effect of  $\beta$  in BJT current mirrors, the circuit which is depicted in fig. 1.b can be used. For this circuit, calculate  $I_o / I_{ref}$  and compare the results with those in (b). Assume  $\beta = 50$ .

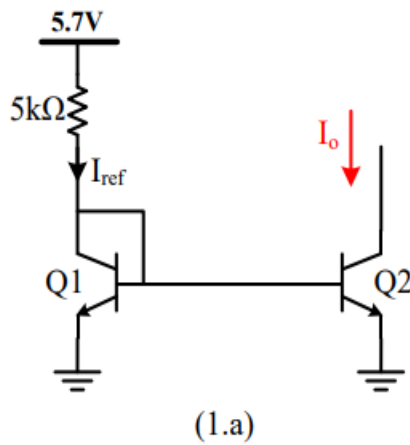

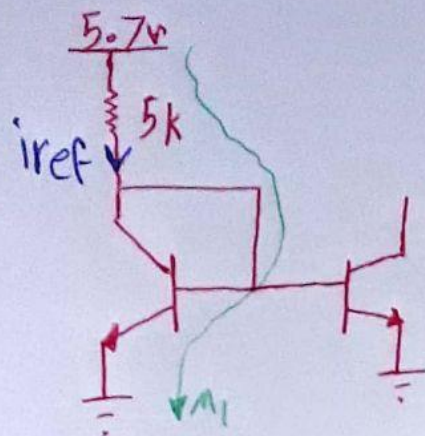


$$V_{BE} = 0.7V \text{ و } i_{ref} = ? \quad (a)$$

$$KVL @ M_1: -5.7 + 5i_{ref} + 0.7 = 0$$

$$i_{ref} = 1mA$$

$$5.7V = V_{CC}$$

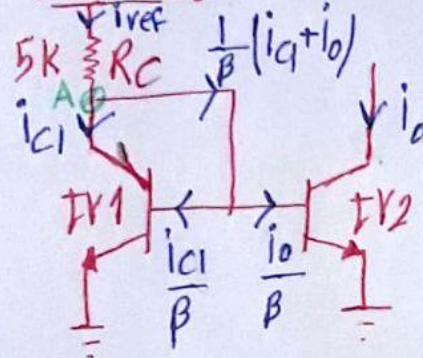

$$\beta = 50, 200, \infty$$

$$? = \frac{i_o}{i_{ref}} \quad (b)$$

$$i_{s1} = i_{s2} \leftarrow \text{ترانزیستور ها مساوی}$$

$$V_{T1} = V_{T2}$$

$$i_c = i_s \exp\left(\frac{V_{BE}}{nV_T}\right)$$

$$V_{BE1} = V_{BE2} \rightarrow i_{c1} = i_o \quad (I)$$

$$KCL @ A_0: i_{ref} = i_{c1} + \frac{1}{\beta}(i_{c1} + i_o) \quad (II) \rightarrow$$


$$i_{ref} = \frac{2i_o}{\beta} + i_o = \left(\frac{\beta+2}{\beta}\right)i_o = i_{ref} \rightarrow$$

$$\frac{i_o}{i_{ref}} = \frac{\beta}{\beta+2}$$

$$\beta = 50 \rightarrow \frac{i_o}{i_{ref}} = 0.96$$

$$\beta = 200 \rightarrow \frac{i_o}{i_{ref}} = 0.99$$
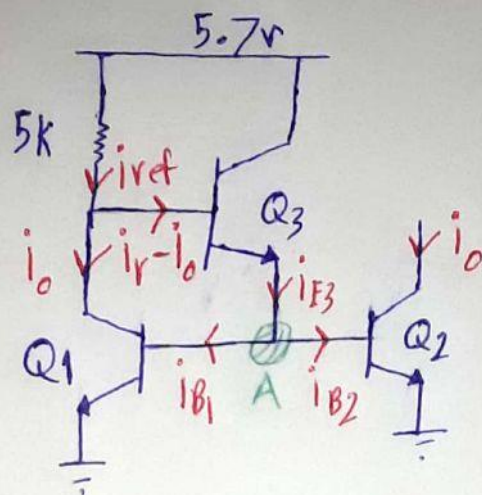
$$\beta = \infty \rightarrow \frac{i_o}{i_{ref}} = 1$$



$$\frac{i_o}{i_{ref}} = ? , \beta = 50 \quad |C$$

$$V_{BE1} = V_{BE2} \rightarrow i_o = i_{C1}$$

$$i_{E3} = (\beta + 1) i_{B3} = 51 (i_r - i_o)$$

$$i_{B1} = \frac{i_{C1}}{\beta} = \frac{i_o}{\beta} = \frac{i_o}{50}$$


$$i_{B2} = \frac{i_o}{\beta} = \frac{i_o}{50}$$

$$KCL @ A: i_{B1} + i_{B2} - i_{E3} = 0 \rightarrow \frac{i_o}{50} + \frac{i_o}{50} - 51 (i_r - i_o) = 0$$


$$51 i_r = \frac{i_o}{25} + 51 i_o \rightarrow 51 i_r = \frac{1276}{25} i_o \rightarrow \frac{i_o}{i_r} = 0.9992$$

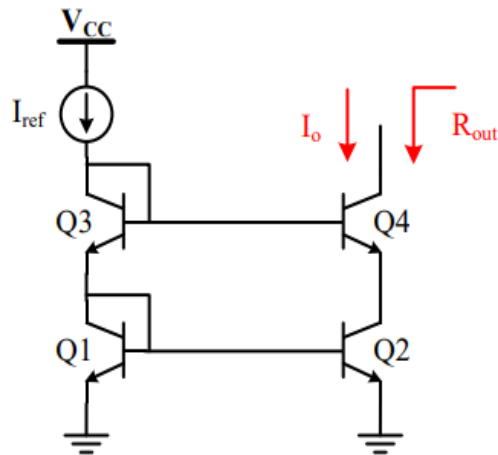0.08% error



- 2- The following circuit is known as the “cascade” current-mirror. Determine the output current and the output resistance (Assume  $\lambda \neq 0$  and neglect  $\beta$  effect). What are the advantages of this configuration over the simple current-mirror scheme?





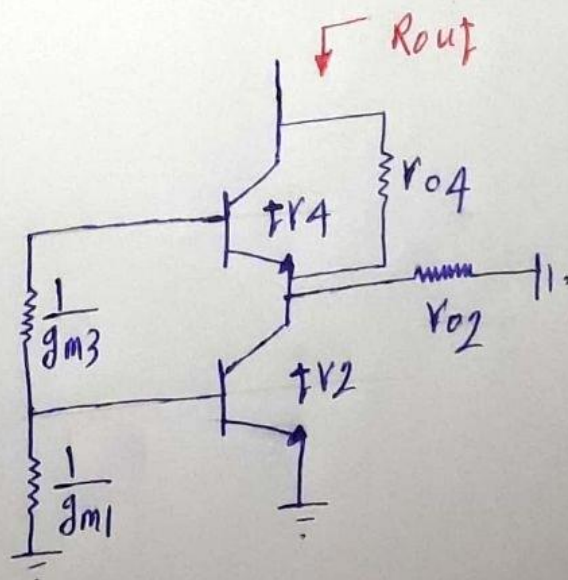

5.5)

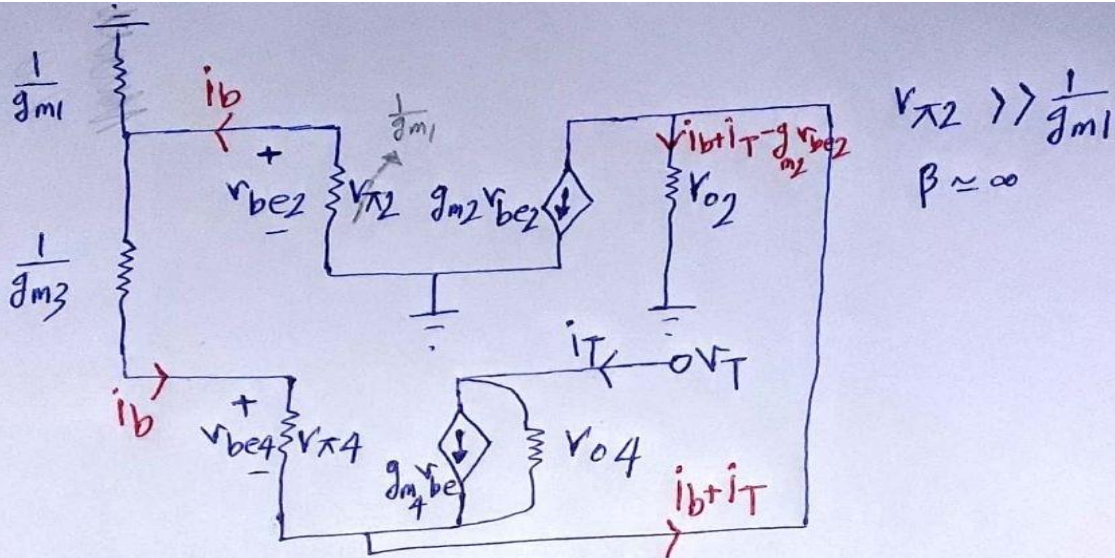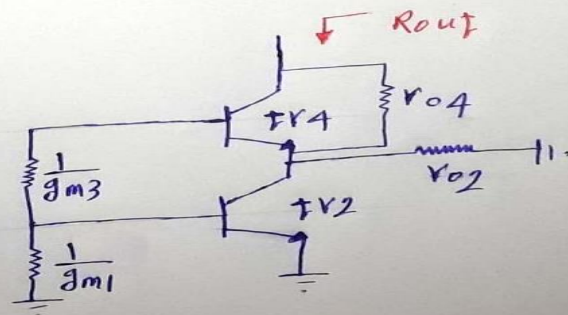

$$r_{\pi 2} \gg \frac{1}{g_{m1}} \\ \beta \approx \infty$$

$$\frac{1}{g_{m1}} i_b + \frac{1}{g_{m3}} i_b + r_{\pi 4} i_b + r_{02} (i_T + i_b - g_{m2} v_{be2}) = 0$$

$$v_{be2} = -\frac{1}{g_{m1}} i_b \rightarrow -\left(\frac{1}{g_{m1}} + \frac{1}{g_{m3}}\right) i_b = r_{\pi 4} i_b + r_{02} (i_T + i_b + \frac{g_{m2}}{g_{m1}} i_b)$$

$$\approx \rightarrow r_{\pi 4} i_b + r_{02} \left(i_T + \frac{g_{m1} + g_{m2}}{g_{m1}} i_b\right) = 0 \rightarrow i_b = \frac{-r_{02} i_T}{r_{\pi 4} + \frac{g_{m1} + g_{m2}}{g_{m1}} r_{02}}$$

$$\text{KVL: } v_T = r_{04} (i_T - g_{m4} r_{\pi 4} i_b) + r_{02} (i_T + \frac{g_{m1} + g_{m2}}{g_{m1}} i_b)$$

$$v_T = r_{04} i_T + r_{02} i_T + \left( \frac{(g_{m1} + g_{m2}) r_{02}}{g_{m1}} - g_{m4} r_{\pi 4} r_{04} \right) \frac{-r_{02} i_T}{r_{\pi 4} + \frac{g_{m1} + g_{m2}}{g_{m1}} r_{02}}$$

$$R_o = r_{02} + r_{04} + \frac{\beta_4 r_{04} r_{02}}{r_{\pi 4} + \frac{g_{m1} + g_{m2}}{g_{m1}} r_{02}}$$

$$i_{C2} \approx i_{C4} \rightarrow r_{02} \approx r_{04} = r_o$$




$$R_{out} = 2V_0 + \frac{\beta_4 V_0^2}{r_{\pi 4} + \frac{g_{m1} + g_{m2}}{g_{m1}} V_0}$$

$$R_{out} \simeq 2V_0 + \frac{\beta_4 V_0^2}{\frac{g_{m1} + g_{m2}}{g_{m1}} V_0} \simeq 2V_0 + \frac{g_{m1} \beta_4 V_0}{g_{m1} + g_{m2}}$$

$$R_{out} \simeq \beta_4 V_0 \left( \frac{g_{m1}}{g_{m1} + g_{m2}} \right)$$

$$\text{if } \{g_{m1} = g_{m2}\} : R_{out} = \frac{\beta V_0}{2}$$

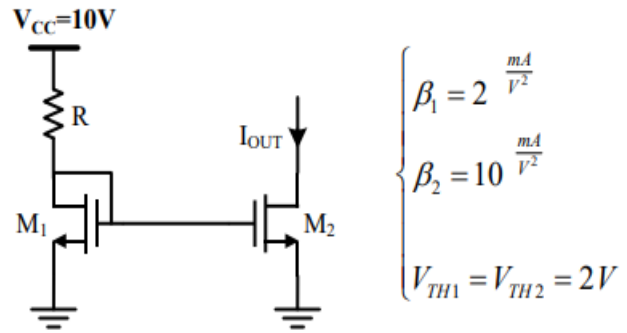
3- Specify the value of  $R$  so that  $I_{OUT} = 5 \text{ mA}$ .





$$R = ?$$

$$i_{out} = 5 \text{ mA}$$

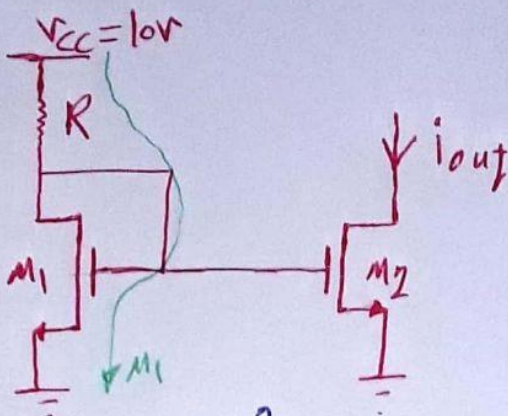

$$\beta_1 = 2$$

$$\beta_2 = 10$$

$$V_{TH1} = V_{TH2} = 2 \text{ V}$$

$$i_D = \frac{\beta}{2} (V_{GS} - V_{TH})^2$$

$$V_{GS1} = V_{GS2} \quad V_{TH1} = V_{TH2}$$

$$\frac{i_{D2}}{i_{D1}} = \frac{\beta_2}{\beta_1} = \frac{10}{2} = 5 = \frac{i_{D2}}{i_{D1}} \quad (I)$$


$$i_{D2} = i_{out} = 5 \text{ mA} \xrightarrow{(I)} i_{D1} = 1 \text{ mA}$$

$$V_{GS1} = V_{TH} + \sqrt{\frac{i_{D1}}{k_1}} = 2 + \sqrt{\frac{1}{1}} = 3 \text{ V}$$

$$\text{KVL @ } M_1: -10 + R \times i_{D1} + V_{GS1} = 0 \rightarrow R = 10 - 3 = 7 \text{ k}\Omega$$



4- In the following circuit,

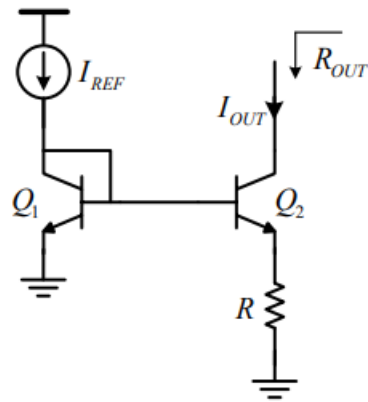- Determine the output resistance. Assume that the current source is ideal.
- Specify  $R$  such a way that  $I_{REF} = 2 \times I_{OUT}$ . The transistors are the same and  $\beta \gg 1$ .



a)  $R_{out} = ?$


ac)

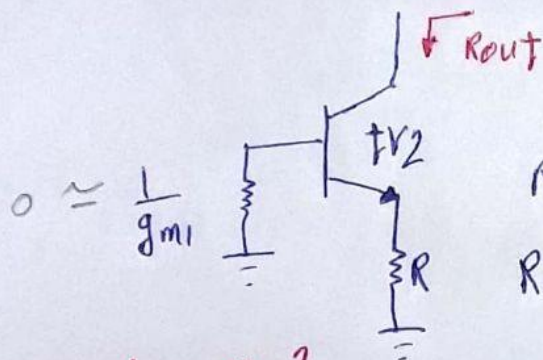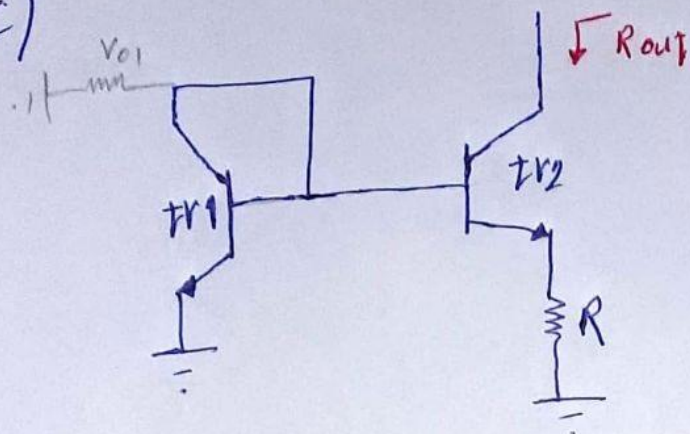

$$R_{out} \approx V_{02} (1 + g_{m2} (R \parallel r_{\pi 2}))$$

$$R_{out} \approx \beta V_{02}$$

b)  $i_r = 2i_o \rightarrow R = ?$

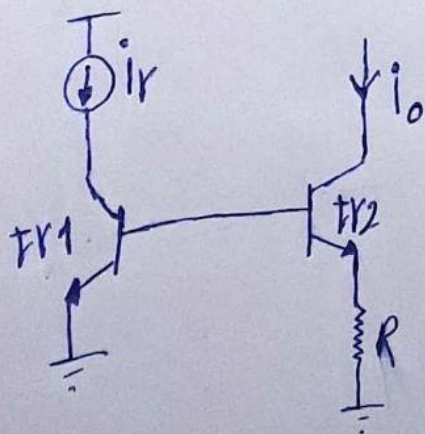

$$-V_{BE1} + V_{BE2} + R i_o = 0$$

$$-V_T \ln\left(\frac{i_r}{i_s}\right) + V_T \ln\left(\frac{i_o}{i_s}\right) = -R i_o$$


$$V_T \ln\left(\frac{i_o}{i_s} \times \frac{i_s}{i_r}\right) = -R i_o$$

$$V_T \ln\left(\frac{i_r}{i_o}\right) = R i_o \rightarrow R = \frac{V_T \ln(2)}{i_o}$$

$$R = \frac{V_T \ln(4)}{i_r}$$

- 5- In the following circuit, all of the transistors are the same. The effective area of the collector "A" of  $Q_2$  is 3 times larger than the effective area of the collector "B" of  $Q_2$ . Calculate the output voltage.

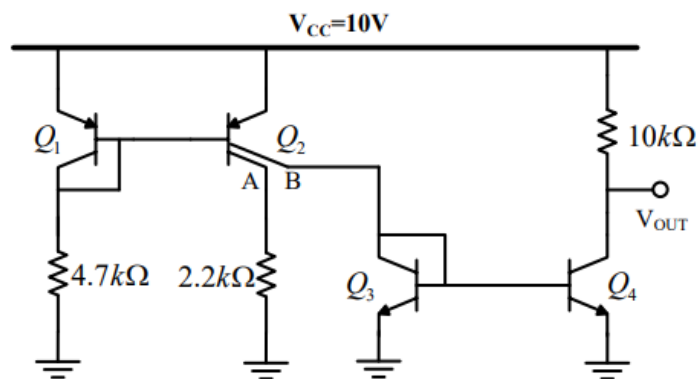
(Hint:  $Q_2$  is a transistors with two collector terminals, which, their currents are proportional to their effective areas. The total effective collector area of  $Q_2$  is the same as that of  $Q_1$ ).





$$V_o = ?$$

15

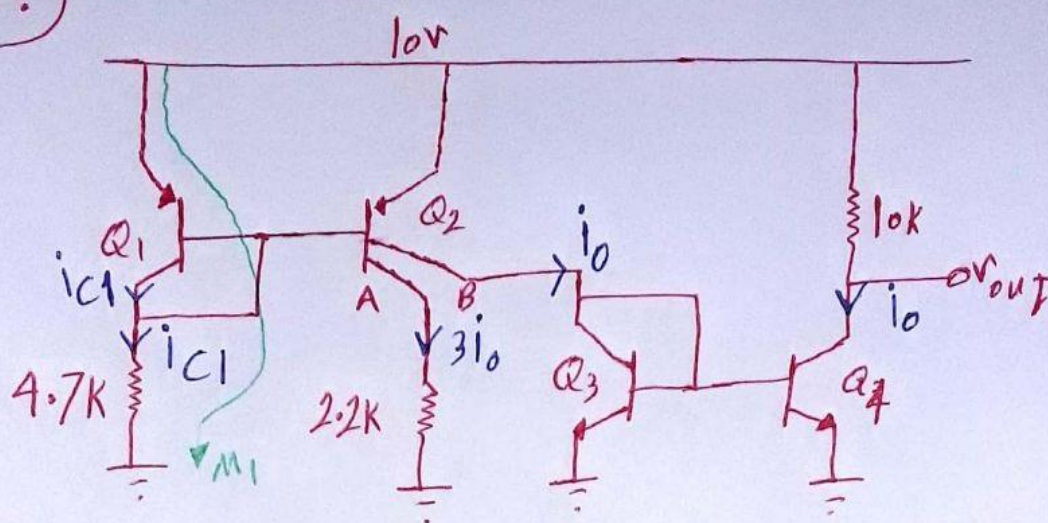

$$A_{s,A} = 3A_{s,B}$$

$$A_{s1} = A_{s2} = A_{s3} = A_{s4}$$

$$V_{BE3} = V_{BE4} \rightarrow i_{C3} = i_{C4}$$

$$i_{C2,A} = 3i_{C2,B}$$

$$i_{C2,A} = 3i_o$$


$$V_{EB1} = V_{EB2} \rightarrow i_{C1} = i_{C2} = 4i_o$$

$$KVL @ m_1: -10 + 0.7 + 4.7i_{C1} = 0$$

$$4.7 \times 4i_o = 9.3 \rightarrow i_o = 0.5 \text{ mA}$$

$$V_o = 10 - 10i_o = 5 \text{ V} = V_o$$

روشن روش حل سوال 5

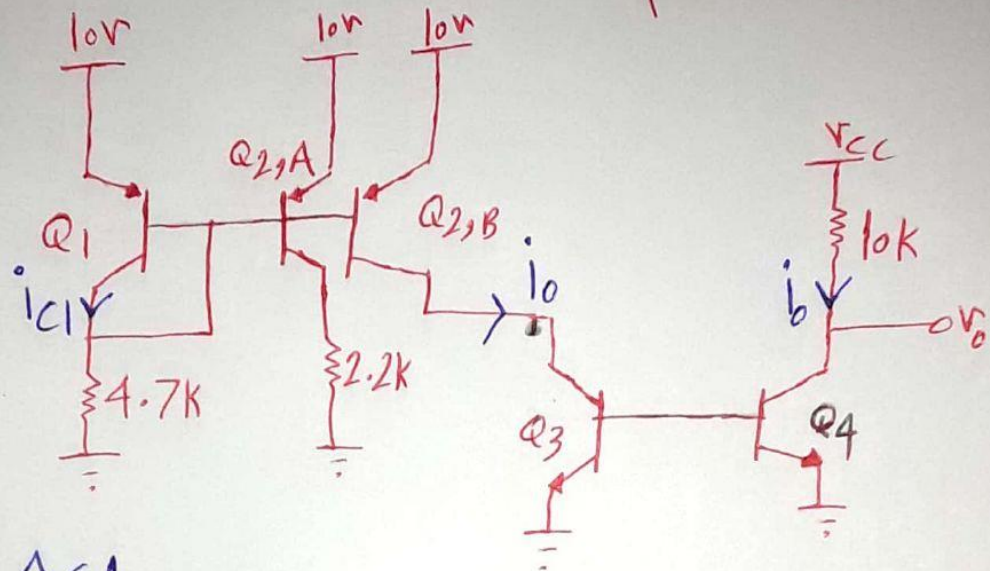

$$A_{s2} = A_{s1}$$

$$A_{s2} = A_{s2,A} + A_{s2,B} = 3A_{s2,B} + A_{s2,B} = 4A_{s2,B}$$


$$A_{s1} = 4A_{s1,B}$$

$$V_{EB1} = V_{EB2,B} \rightarrow i_{C1} = 4i_{C2,B} = 4i_o$$

$$-10 + 0.7 + 4.7i_{C1} = 0 \rightarrow 4.7 \times 4i_o = 9.3 \rightarrow$$

$$i_o \approx 0.5 \text{ mA} \rightarrow v_o = 5 \text{ V}$$

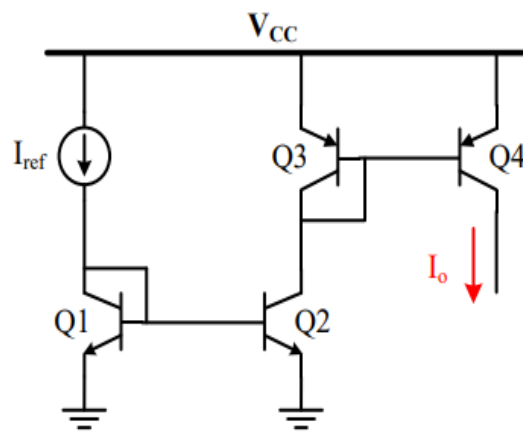
- 6- In the following circuit, specify a relation for  $I_o$  in terms of  $I_{ref}$  (neglect  $\beta$  and  $\lambda$  effects). The collector areas of  $Q_2$  and  $Q_4$  is 2 times larger than  $Q_1$  and the collector area of  $Q_3$  is 3 times larger than  $Q_1$ .





$$A_{2,4} = 2A_1$$

$$A_3 = 3A_1$$

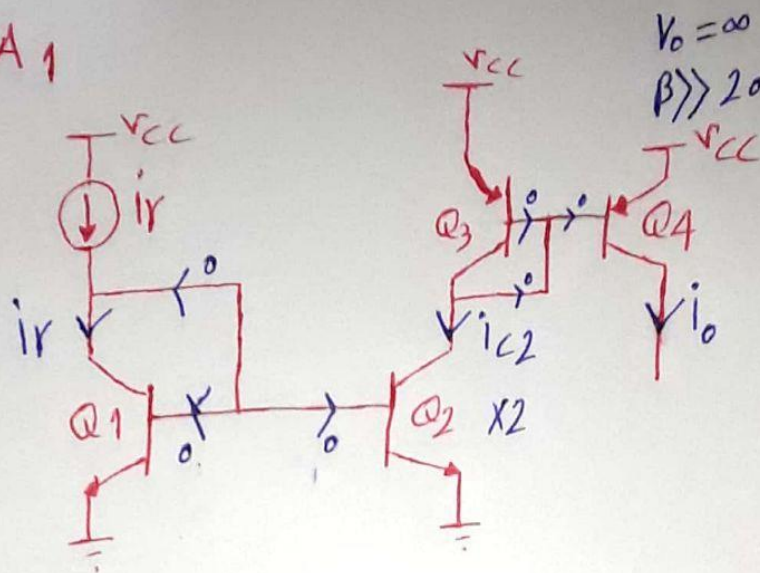

$$V_{BE1} = V_{BE2} \rightarrow i_{C2} = 2i_{C1} = 2i_r$$

$$i_{C3} = i_{C2} = 2i_r$$

$$V_{EB3} = V_{EB4} \quad \frac{A_3}{A_4} = \frac{3A_1}{2A_1} = \frac{3}{2} \rightarrow i_{C4} = \frac{2}{3} i_{C3}$$

$$i_{C4} = \frac{2}{3} \times 2i_r = \frac{4}{3} i_r = i_o \rightarrow i_o = \frac{4}{3} i_r$$