
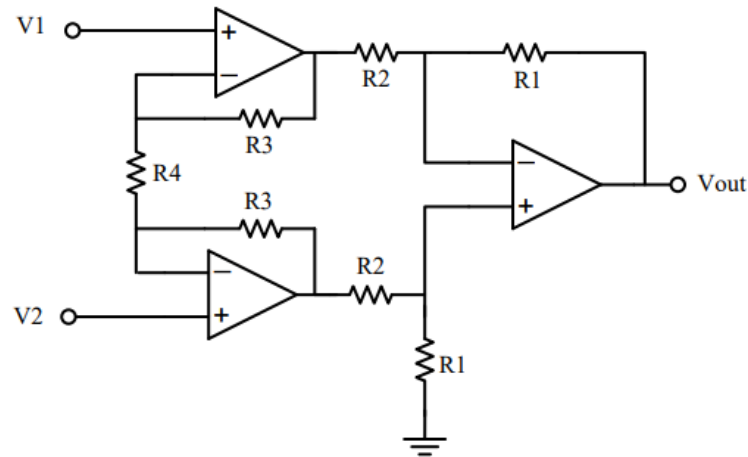


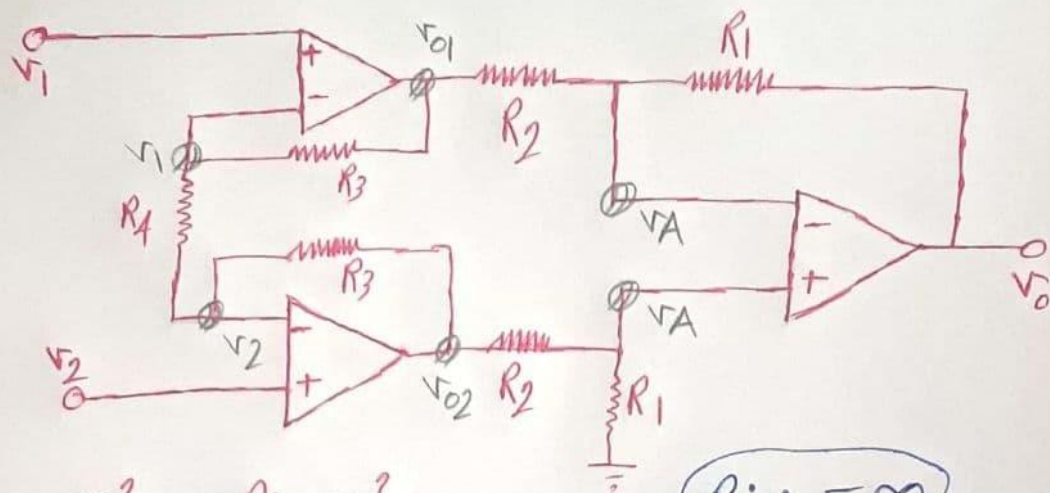- 1- The configuration shown below is known as the “Instrumentation Amplifier” or “IA”. Determine the output voltage in terms of the input voltages. How much is the input resistance seen from the input terminals (V1 and V2). Assume ideal op-amps.





$$\frac{v_0}{v_1 - v_2} = ? \quad R_{in} = ?$$

$$R_{in} = \infty$$

$$\text{KCL @ } v_1: \frac{v_1 - v_2}{R_4} + \frac{v_1 - v_{01}}{R_3} = 0$$


$$\text{KCL @ } v_2: \frac{v_2 - v_1}{R_4} + \frac{v_2 - v_{02}}{R_3} = 0$$


$$\text{KCL @ } v_A: \frac{v_A - v_{01}}{R_2} + \frac{v_A - v_0}{R_1} = 0$$

$$v_A \rightarrow v_A = \frac{R_1 v_{02}}{R_1 + R_2}$$

$$\rightarrow \frac{v_0}{v_1 - v_2} = \left[ \frac{R_1 R_3 \left( \frac{1}{R_3} + \frac{1}{R_4} \right)}{R_2} + \frac{R_1 R_3}{R_2 R_4} \right]$$

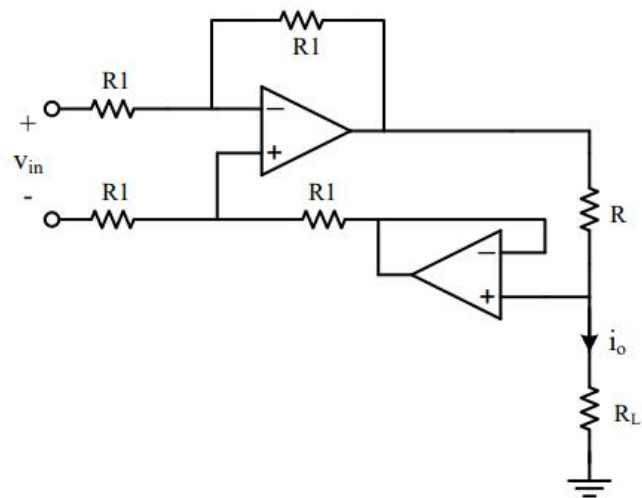- 2- Calculate the output current ( $i_o$ ) in the following circuit. The op-amps are supposed to be ideal one.




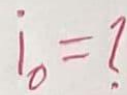


$$KVL @ m_1 \circ i_1 = \frac{v_{in}}{2R_1}$$

$$i_0 = - \frac{v_{in}}{R}$$

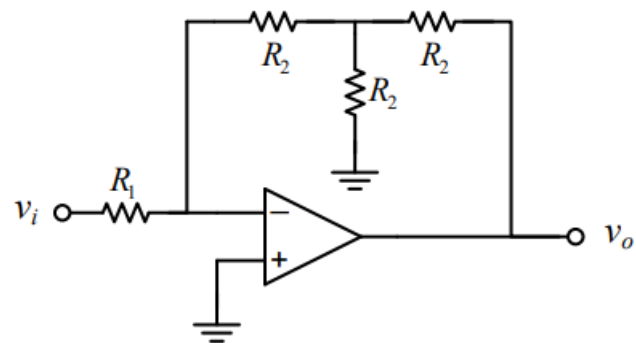3- Determine the voltage gain  $\frac{v_o}{v_i}$  in the following circuit. Assume that the op-amp is ideal.



? = Av 13

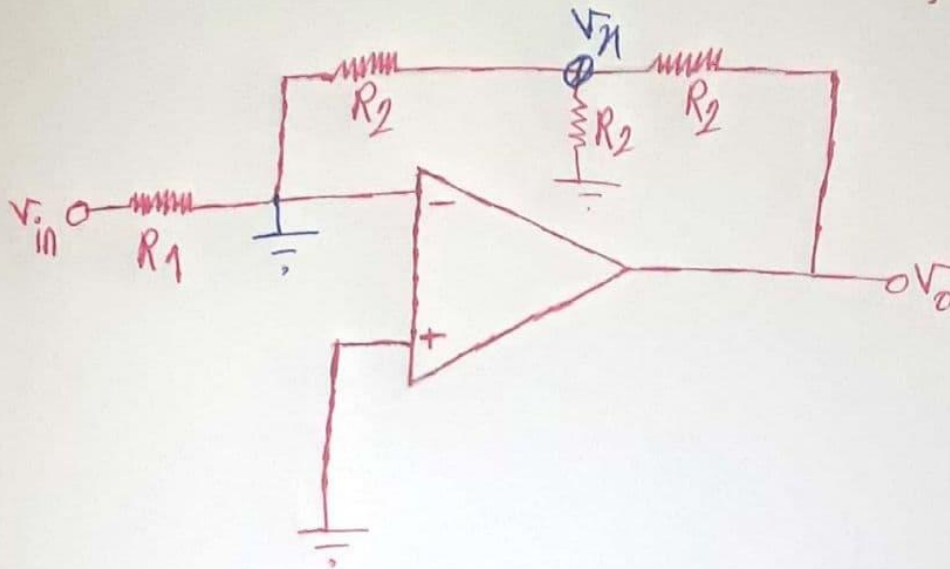


$$\text{KCL @ } \frac{1}{2} : \frac{V_{in}}{R_1} = -\frac{V_n}{R_2} \rightarrow V_n = -\frac{R_2}{R_1} V_{in}$$

$$\text{KCL @ } V_n : \frac{V_n}{R_2} + \frac{V_n}{R_2} = \frac{V_o - V_n}{R_2}$$


$$V_n = \frac{V_o}{3}$$

$$\frac{V_o}{3} = -\frac{R_2}{R_1} V_{in} \rightarrow A_v = -3 \frac{R_2}{R_1}$$

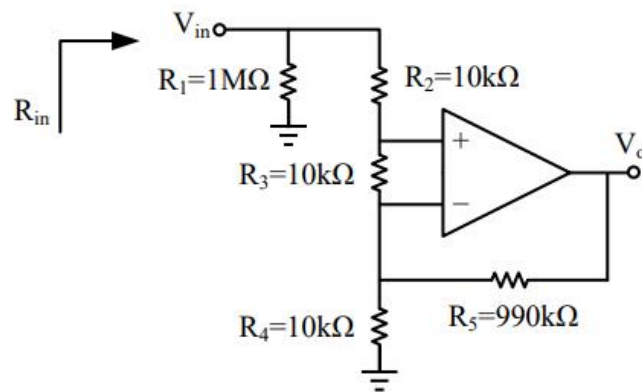- 4- Calculate the input resistance and the voltage gain of the following structure. The op-amp is ideal.





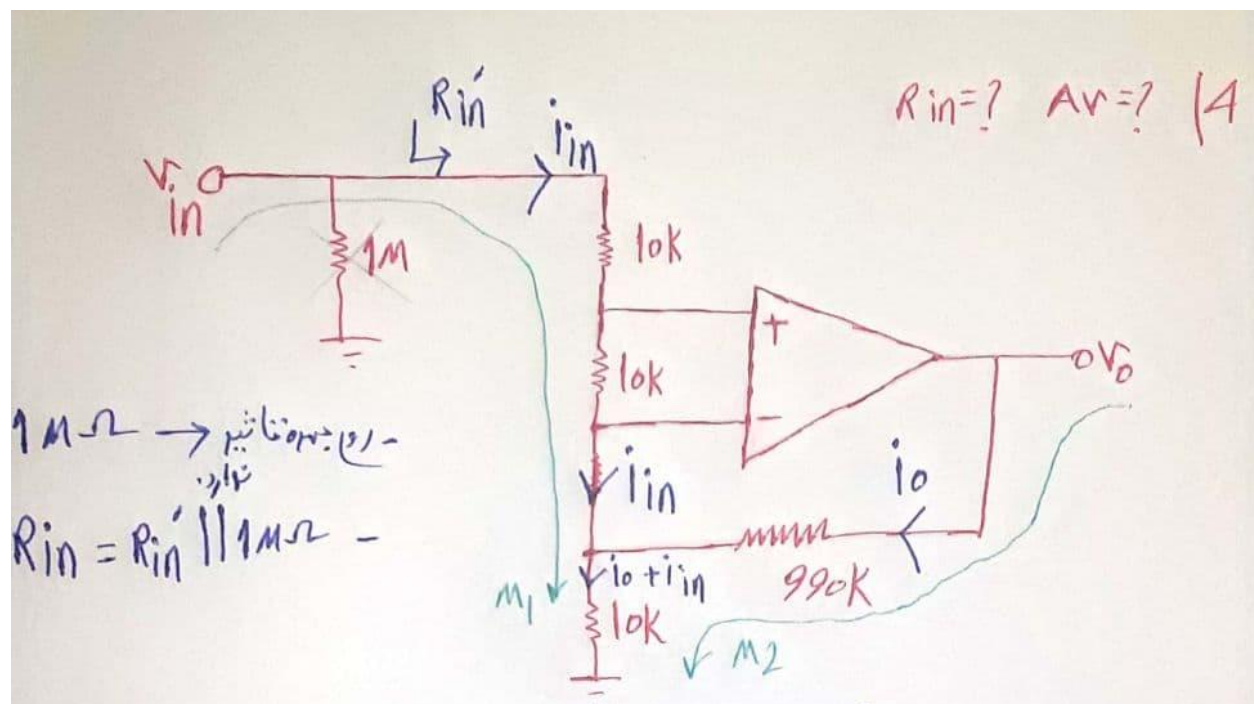

$$KVL @ m_1: -v_{in} + 20i_{in} + 10i_o + 10i_{in} = 0 \rightarrow$$

$$v_{in} = 30i_{in} + 10i_o \quad i_{in} = 0$$

$$\frac{v_{in}}{i_{in}} = \infty = R_{in}' \quad R_{in} = 1M\Omega \parallel \infty \Rightarrow$$


$$R_{in} = 1M\Omega$$

$$KVL @ m_2: -v_o + 990i_o + 10i_o + 10i_{in} = 0 \rightarrow i_o = \frac{v_o}{1000}$$


$$\rightarrow v_{in} = \frac{v_o}{100} \rightarrow A_v = 100$$



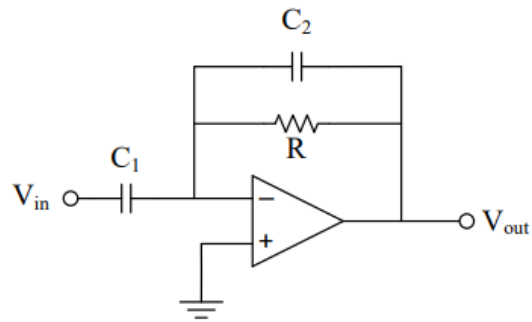- 5- Determine the transfer function of the following circuit and prove that it acts like a filtering circuit. Specify the type of the filter. Assume ideal op-amp.



5

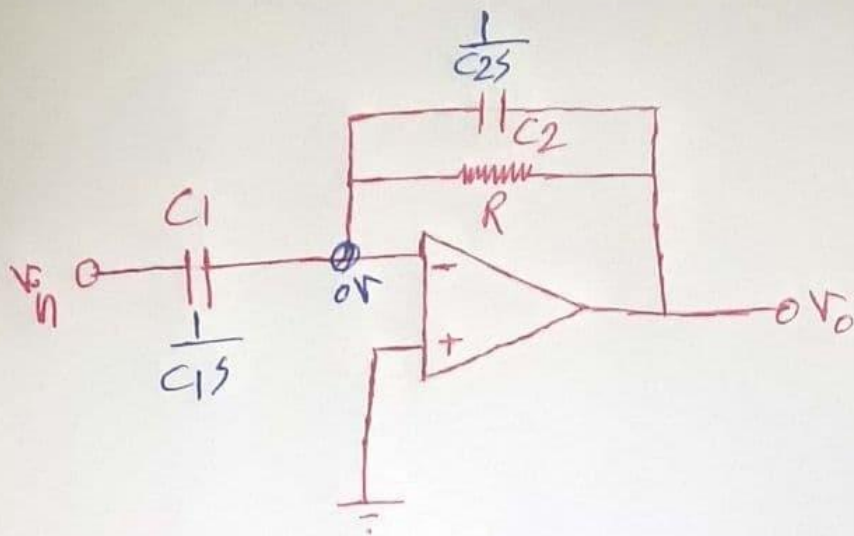

$$KCL @ -op \circ C_1 s V_{in} = -\frac{V_o}{R} - C_2 s V_o \rightarrow$$

$$\frac{V_o}{V_{in}} = -\frac{C_1 s}{\frac{1}{R} + C_2 s} \rightarrow H(s) = \frac{V_o}{V_{in}}(s) = \frac{-RC_1 s}{1 + RC_2 s}$$

$$s=0 \rightarrow H(s=0) = 0 \quad s \rightarrow \infty \rightarrow H(s) \Big|_{s \rightarrow \infty} = -\frac{C_1}{C_2} \rightarrow \text{میلتر بال گذر}$$


$$H(j\omega) = \frac{-RC_1 j\omega}{1 + RC_2 j\omega} \rightarrow |H| = \frac{RC_1 \omega}{\sqrt{1 + (RC_2 \omega)^2}}$$

$$|H|_{(\omega)}^2 = \frac{(RC_1 \omega)^2}{1 + (RC_2 \omega)^2} \rightarrow \text{if } \{C_1 = C_2\} \rightarrow H_{max} = 1$$

$$\frac{(RC\omega_c)^2}{1 + (RC\omega_c)^2} = \frac{1}{2} \rightarrow 2(RC\omega_c)^2 = 1 + (RC\omega_c)^2$$

$$(RC\omega_c)^2 = 1 \rightarrow \omega_c = \frac{1}{RC}$$

$C_1 = C_2$  فرض ہے

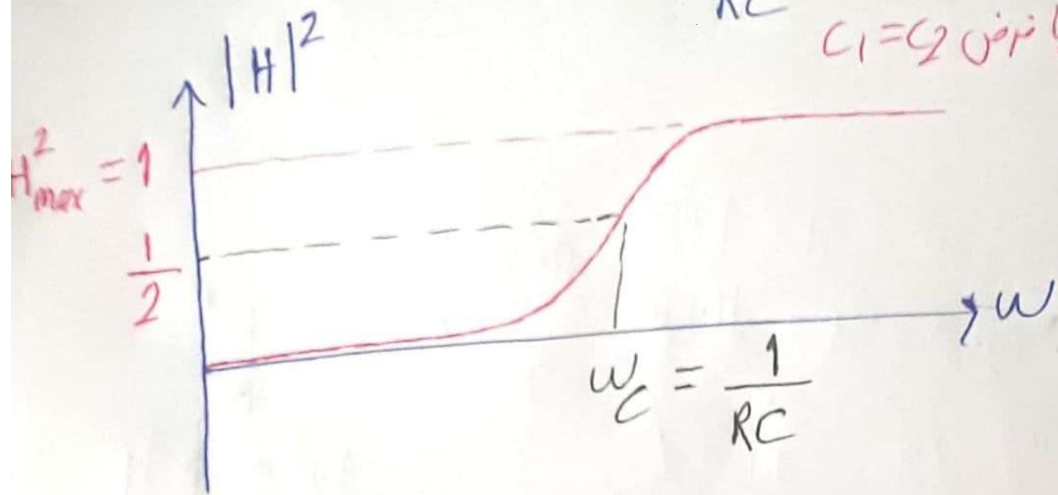


- 6- Design a circuit which its output voltage is according to the following relation.  $V_1$  and  $V_2$  are the input voltages.

$$V_{out} = 4 \times V_1 + 3 \times V_2$$

$$V_{out} = 4V_1 + 3V_2$$


-6

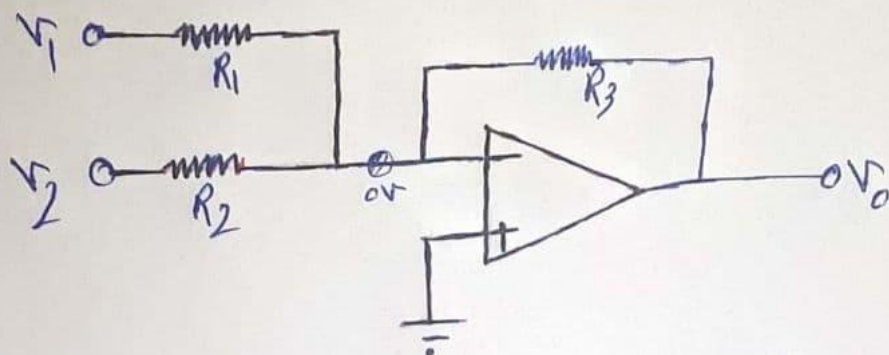

$$\text{KCL @ } v_o: \frac{V_1}{R_1} + \frac{V_2}{R_2} = -\frac{V_o}{R_3} \rightarrow$$

$$V_o = -\left(\frac{R_3}{R_1}V_1 + \frac{R_3}{R_2}V_2\right)$$

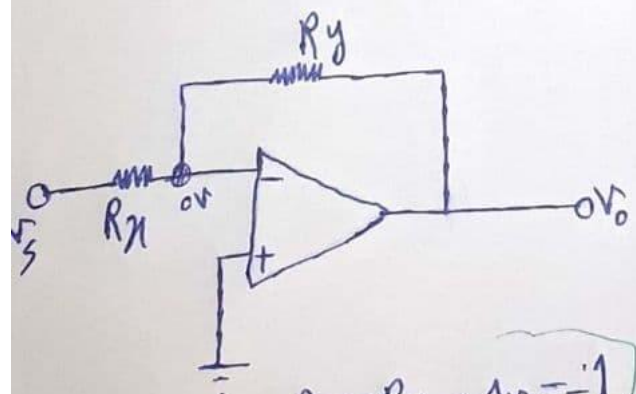
$$\begin{cases} \frac{R_3}{R_1} = 4 \\ \frac{R_3}{R_2} = 3 \end{cases} \begin{cases} R_3 = 1\text{ k}\Omega \\ R_1 = \frac{1}{4}\text{ k}\Omega \\ R_2 = \frac{1}{3}\text{ k}\Omega \end{cases}$$



$$\text{KCL @ } v_s: \frac{V_s}{R_x} = -\frac{V_o}{R_y}$$

$$\frac{V_o}{V_s} = -\frac{R_y}{R_x} \quad R_x = R_y = 1\text{ k}\Omega$$

$$R_x = R_y \rightarrow A_v = -1$$

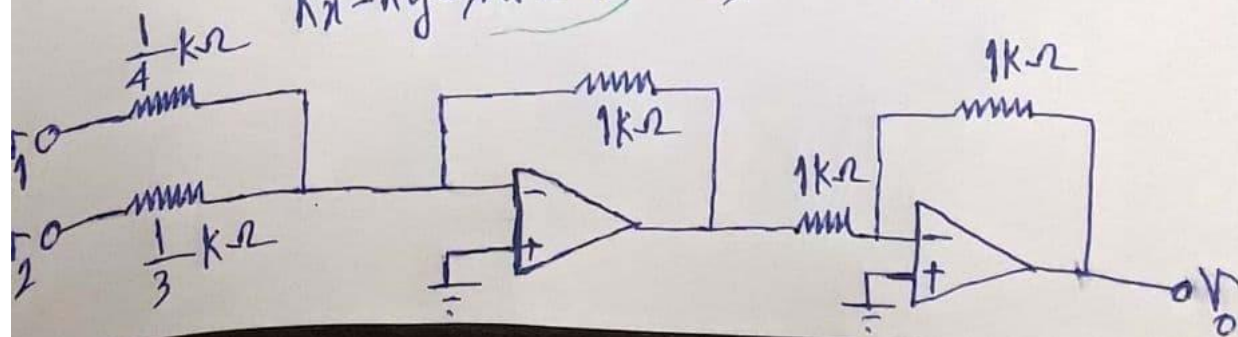


7- Design a circuit which solves the following differential equation.

$$\frac{d^2 v}{dt^2} = -20 \frac{dv}{dt} - 100 v + 25 V$$

$$\ddot{V}_0 = -20 \dot{V}_0 - 100 V_0 + 25 V$$

مقاومت  $R$  خروجی

-7

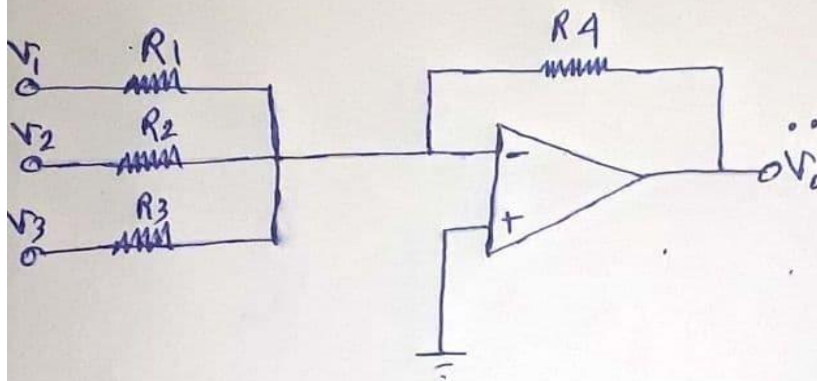

$$\ddot{V}_0 = - \left( \frac{R_4}{R_1} V_1 + \frac{R_4}{R_2} V_2 + \frac{R_4}{R_3} V_3 \right)$$

$$\frac{R_4}{R_1} = 1 \checkmark \quad V_1 = -25 V \checkmark \quad V_2 = V_0 \checkmark$$


$$\frac{R_4}{R_2} = 100 \checkmark \quad \frac{R_4}{R_3} = 20 \checkmark \quad V_3 = \dot{V}_0 \checkmark$$

$$R_4 = 100 k\Omega \rightarrow R_1 = 100 k\Omega$$

$$\rightarrow R_2 = 1 k\Omega$$


$$\rightarrow R_3 = 5 k\Omega$$



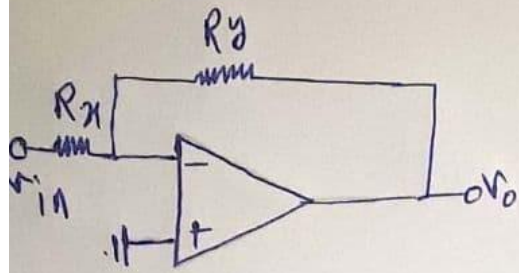

$$\frac{v_o}{v_{in}} = -\frac{R_y}{R_x}$$
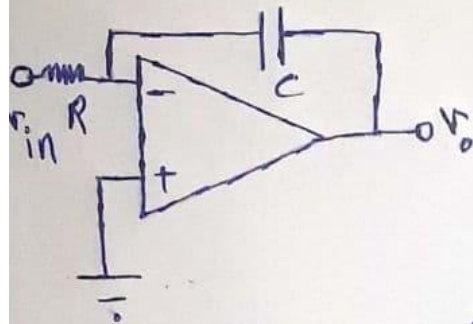
$$R_x = R_y = 1K \rightarrow \frac{v_o}{v_{in}} = -1$$



$$KCL @ -op \circ \frac{v_o}{v_{in}} = -\frac{1}{RCs}$$

$$\xrightarrow{L^{-1}} v_o(t) = -\frac{1}{RC} \int v_{in} dt$$

$$\left. \begin{array}{l} R = 10k\Omega \\ C = 0.1mF \end{array} \right\} \rightarrow v_o(t) = - \int v_{in} dt$$

