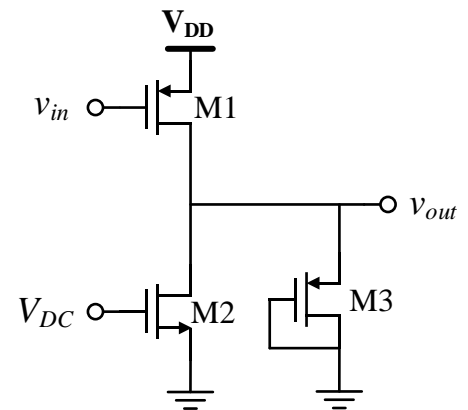





- 1- a) Using the small-signal **model**, determine a relation for the voltage gain ( $A_v = V_{out} / V_{in}$ ) of the following circuit. Assume that the transistors operate in saturation and  $\lambda \neq 0$ .

b) Determine  $R_{out}$ .




- 2- a) Determine the bias points of the transistors.

b) Calculate the voltage gain.

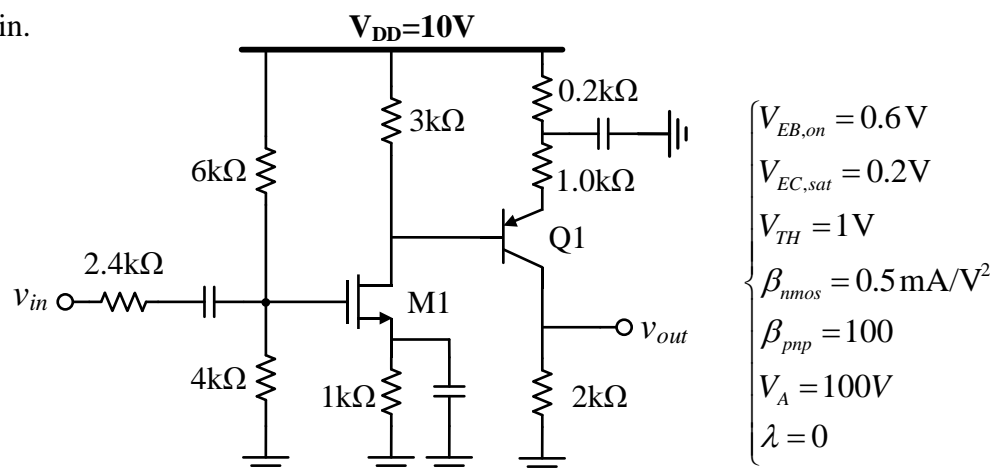

- 3- a) Specify  $R_3$  so that the bias current of the transistors will be equal to 2 mA. Prove that Q1 operates in forward active region.

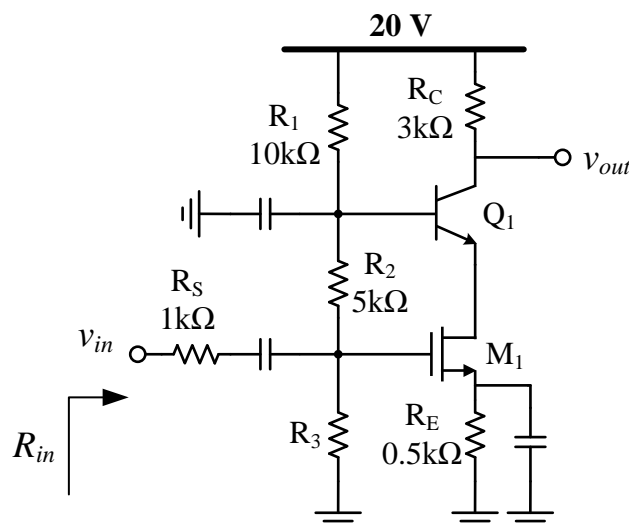b) Calculate the voltage gain ( $A_v = V_{out} / V_{in}$ ) and the input resistance ( $R_{in}$ ). Neglect the base current in DC analysis.



$$\begin{aligned}
 &BJT : \begin{cases} V_{BE} = 0.7V \\ V_{CEsat} = 0.2V \\ V_A = \infty \\ V_T = 25mV \\ \beta = 100 \end{cases} \\
 &MOS : \begin{cases} V_{TH} = 2V \\ \mu_n C_{ox} = 0.5mA/V^2 \\ \lambda = \infty \\ \left(\frac{W}{L}\right) = \frac{2\mu m}{1\mu m} \end{cases}
 \end{aligned}$$

روابط قابل استفاده:

$$R_{seen-base} = r_{\pi} + (\beta + 1)R_E$$

$$R_{seen-collector} = r_O (1 + g_m (R_E \parallel r_{\pi}))$$

$$R_{seen-emitter} = \frac{r_O + R_C}{1 + g_m r_O} \quad \text{if } (R_B = 0)$$

$$R_{seen-emitter} = \frac{r_{\pi} + R_B}{\beta} \quad \text{if } (R_B \neq 0)$$

$$A_{V,CE} = -g_m (R_C \parallel r_O)$$

$$A_{V,ED} = \frac{-R_C}{R_E + 1 / g_m}$$

$$A_{V,CC} = \frac{R_E}{R_E + 1 / g_m}$$

$$A_{V,CB} = g_m (R_C \parallel r_O)$$

حل سوالات کوثر لول اختر رسا، نیک ساد لول تحسینی ۱۴۰۱-۱۴۰۲


حل سوالات لول: معم

تغایر محسوب ←

منابع ورودی صفر

0  $V_{in}$

عبر دلتا ← معم

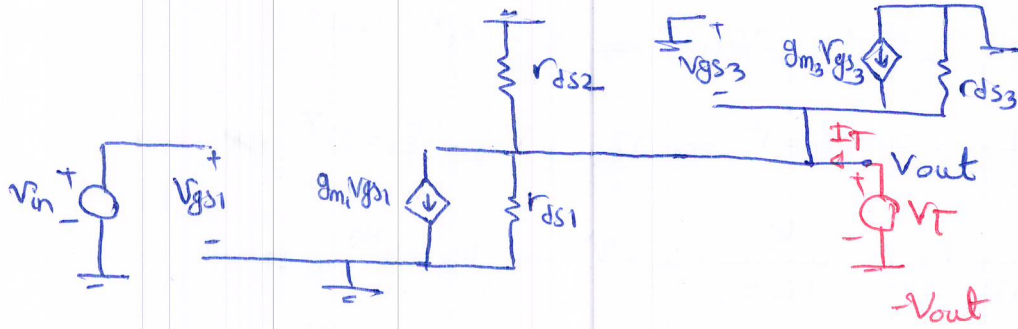

$$KCL @ v_{out}: \frac{v_{out}}{r_{ds1}} + \frac{v_{out}}{r_{ds2}} + \frac{v_{out}}{r_{ds3}} + g_{m3}V_{gs3} + g_{m1}V_{gs1} - I_T = 0$$


$$v_{out} = V_T \Rightarrow \frac{V_T}{I_T} = r_{ds1} || r_{ds2} || r_{ds3} || 1/g_{m3}$$

$$\frac{v_{out}}{r_{ds1}} + \frac{v_{out}}{r_{ds2}} + \frac{v_{out}}{r_{ds3}} - g_{m3}V_{gs3} + g_{m1}V_{gs1} = 0$$

$$\Rightarrow A_V = \frac{v_{out}}{v_{in}} = -g_{m1} (r_{ds1} || r_{ds2} || r_{ds3} || 1/g_{m3}) \approx -g_{m1}/g_{m3}$$

حل سوال دوم: معم

حل DC: معم

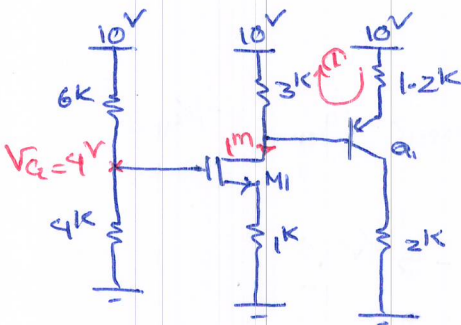

$$I_{D1} = \frac{1}{2} \mu_{n} C_{ox} (W/L) (V_{GS} - V_{TH})^2$$

$$= \frac{1}{2} \times \frac{1}{2} \times (4 - 1)^2 \Rightarrow I_{D1} = 1 \text{ mA}$$

$$V_{DS1} = 3V > 1V \checkmark$$


$$KVL @: -10 + 1.2k I_{E1} + 0.6 + 3k (1^m - I_{B1}) + 10 = 0$$

$$\Rightarrow I_{E1} = I_{C1} = 2 \text{ mA}$$

$$\Rightarrow V_{DS1} = 6V > V_{DS1} - V_{TH} = 2V \checkmark, V_{DS1} = 3.6V > 0.2V \checkmark$$

$$\begin{cases} g_{m1(CM)} = 1 \text{ mA/V} \\ g_{m1(Q)} = 80 \text{ mA/V} \end{cases}$$

حل S.S: معم

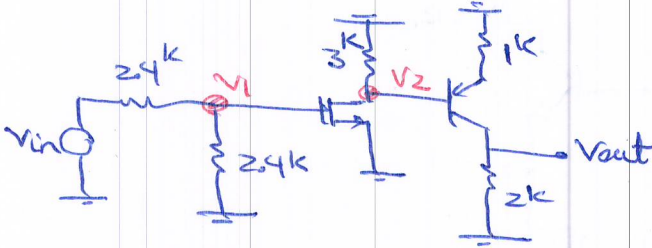

$$\frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_2} \cdot \frac{v_2}{v_1} \cdot \frac{v_1}{v_{in}}$$

$$\frac{v_{out}}{v_2} = \frac{-2k}{1k + 1/80} = -2 \frac{v_2}{v_1} = -g_{m1} (3k || r_{out}(\beta+1)I^k) = -3 \frac{v_2}{v_1}$$

$$\Rightarrow \frac{v_{out}}{v_{in}} = +3 \frac{v_2}{v_1}$$

$$\frac{v_1}{v_{in}} = \frac{24k}{24k + 24k} = \frac{1}{2}$$

معم

محل سوال سوم :  
۲۲۰۰

$$I_{M1} = 2 \text{ mA} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \Rightarrow V_{GS} = 4 \text{ V}$$

$$\Rightarrow V_{S1} = R_E \times I_{M1} = 2 \times 0.5 = 1 \text{ V} \Rightarrow V_{G_{M1}} = V_{GS} + V_{S1} = 5 \text{ V}$$

$$V_{G_{M1}} = \frac{R_3}{R_1 + R_2 + R_3} V_{CC} = \frac{R_3}{15 + R_3} \times 20 = 5 \text{ V} \Rightarrow R_3 = 5 \text{ k}\Omega$$

$$V_{B1} = \frac{R_2 + R_3}{R_2 + R_3 + R_1} V_{CC} = 10 \text{ V} \Rightarrow V_{E1} = 10 - 0.7 = 9.3 \text{ V} \rightarrow V_{DS1} = 8.3$$

$$V_{C1} = V_{CC} - R_C I_{RC} = 20 - 3 \times 2 \text{ mA} = 14 \text{ V} \Rightarrow V_{CEQ1} = 14 - 9.3 = 4.7 \text{ V}$$

$$g_{mQ1} = 80 \text{ mA/V}, \quad g_{mM1} = \frac{2I}{V_{GS} - V_{TH}} = 2 \text{ mA/V}$$

$$A_v = \frac{V_{out}}{v_{in}} = \frac{V_{out}}{v_{e1}} \times \frac{v_{e1}}{v_{g1}} \times \frac{v_{g1}}{v_{in}}$$

$$\Rightarrow \frac{V_{out}}{v_{e1}} = + g_{mQ1} \times R_C = 80 \text{ mA/V} \times 3 \text{ k}\Omega = 240 \text{ V/V}$$

$$\Rightarrow \frac{v_{e1}}{v_{g1}} = - g_{mM1} \times R_{D_{M1}} = - g_{mM1} \times R_{thQ1} = - g_{mM1} \times \frac{1}{g_{mQ1}} = - \frac{1}{40}$$

$$\frac{v_{g1}}{v_{in}} = \frac{R_2 \parallel R_3}{R_2 \parallel R_3 + R_1} = \frac{2.5}{3.5} \Rightarrow A_v = -5 \text{ V/V}$$

$$R_{in} = R_1 + R_2 \parallel R_3 = 1 \text{ k}\Omega + 5 \text{ k}\Omega \parallel 5 \text{ k}\Omega = 3.5 \text{ k}\Omega$$

