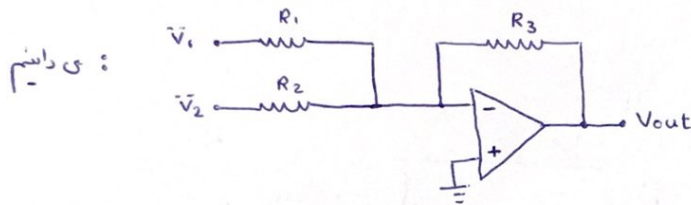


Assignment 10 :

1. Design a circuit which its output voltage is according to the following relation.
 V_1 and V_2 are the input voltage.


$$V_{out} = 4\bar{V}_1 + 3\bar{V}_2$$




$$V_{out} = - \left(\frac{R_3}{R_1} V_1 + \frac{R_3}{R_2} V_2 \right) \rightarrow \begin{cases} \frac{R_3}{R_1} = 4 \Rightarrow R_3 = 4R_1 \\ \frac{R_3}{R_2} = 3 \Rightarrow R_3 = 3R_2 \end{cases} \Rightarrow R_1 = \frac{3}{4} R_2$$

بافتن : $R_2 = 4^k \Rightarrow R_1 = 3^k, R_3 = 12^k$

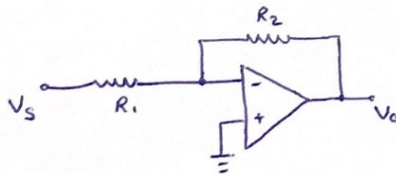بافتن یک بافتن بافتن ۱- در شریف : ختی کردن - مدار



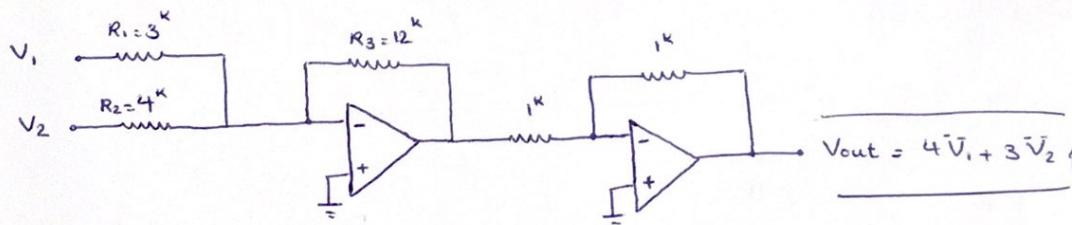
ی دایم : $\frac{V_o}{V_s} = \frac{-R_2}{R_1} \xrightarrow{R_2=R_1=1^k} \boxed{A_v = -1}$



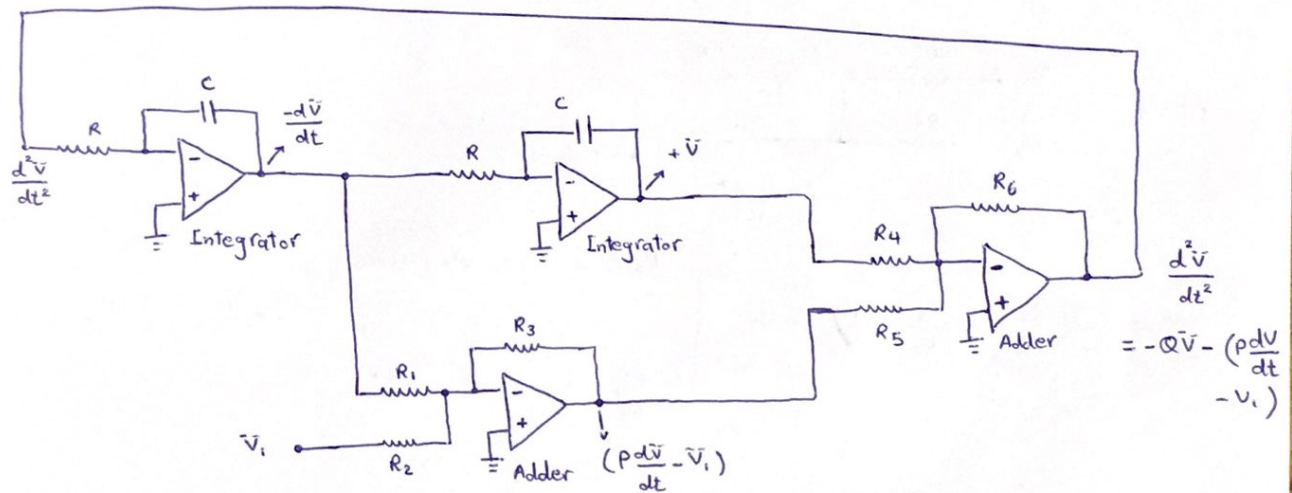2. Design a circuit which solves the following differential equation.

$$\frac{d^2 \bar{v}}{dt^2} = -20 \frac{d\bar{v}}{dt} - 100 \bar{v} + 25$$

معادله کلی: $\frac{d^2 \bar{v}}{dt^2} + P \frac{d\bar{v}}{dt} + Q \bar{v} = \bar{V}_i \Rightarrow \frac{d^2 \bar{v}}{dt^2} = \bar{V}_i - Q \bar{v} - P \frac{d\bar{v}}{dt}$
 $= (-Q \bar{v}) - (P \frac{d\bar{v}}{dt} - \bar{V}_i)$




$$\begin{cases} \frac{R_3}{R_1} = P \\ R_2 = R_3 \end{cases}$$

$$\begin{cases} \frac{R_6}{R_4} = Q \\ R_5 = R_6 \end{cases}$$


$$\frac{d^2 \bar{v}}{dt^2} = 25 - \overset{Q}{100} \bar{v} - \overset{P}{20} \frac{d\bar{v}}{dt}$$
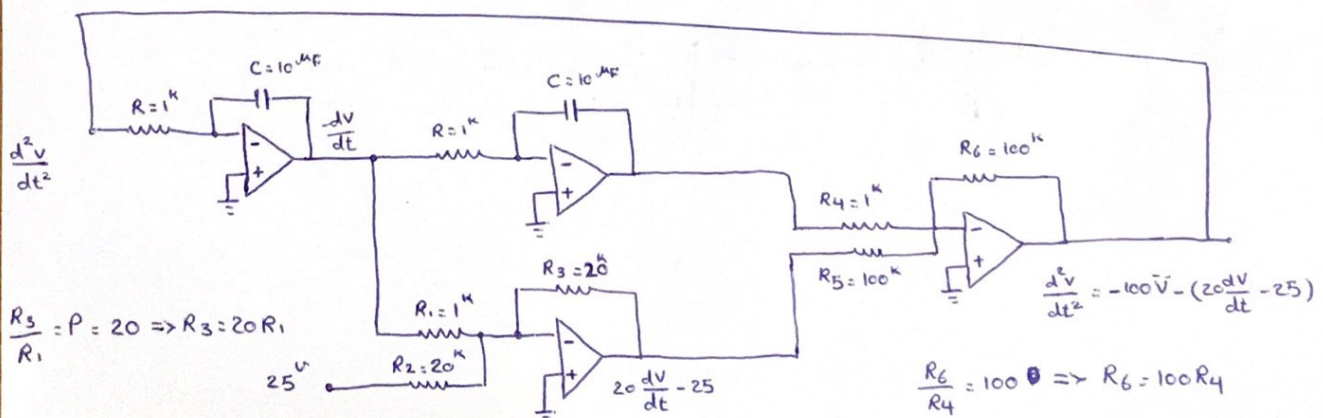
$$= -100 \bar{v} - (20 \frac{d\bar{v}}{dt} - 25)$$



3. In the following circuit which acts as a current source, determine V_s and R such that the output current (I_L) will be 5^{mA} . Assume Ideal opAmp.

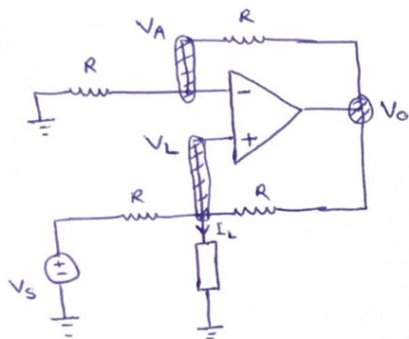b) Considering $V_s = 1^V$ and $R = 1^k$, if the output resistance of the opAmp equal $1^k\Omega$, determine A_v (voltage gain of the opAmp) so that the output resistance of the current source will be $1^M\Omega$.



$$\text{KCL @ } V_A: \frac{V_A - 0}{R} + \frac{V_A - V_o}{R} = 0 \Rightarrow V_o = 2V_A$$

$$V_A = V_L \Rightarrow V_o = 2V_L$$


$$\text{KCL @ } V_L: \frac{V_L - V_s}{R} + \frac{V_L - V_o}{R} + I_L = 0$$

$$\Rightarrow \frac{V_L}{R} - \frac{V_s}{R} + \frac{V_L}{R} - \frac{V_o}{R} + I_L = 0$$

$$\frac{2V_L}{R} - \frac{V_s}{R} - \frac{V_o}{R} + I_L = 0 \xrightarrow{V_o = 2V_L} I_L = \frac{V_s}{R}$$

$$\Rightarrow 5^{mA} = \frac{V_s}{R} \xrightarrow{\text{Assume } R = 1^k} V_s = 5^V$$

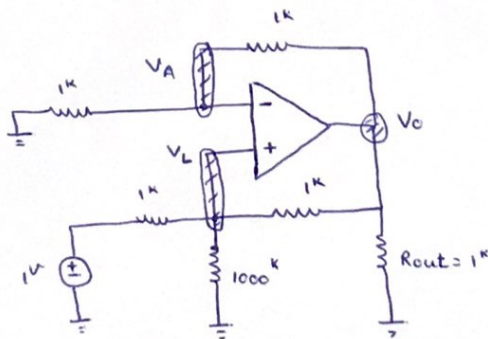b) $\begin{cases} V_s = 1^V \\ R = 1^k \end{cases}$



$$\text{KCL @ } V_A: \frac{V_A - V_o}{1^k} + \frac{V_A - 0}{1^k} = 0 \Rightarrow \frac{2V_A}{1^k} = \frac{V_o}{1^k} \Rightarrow V_A = V_L = \frac{1}{2} V_o \quad (I)$$

$$\text{KCL @ } V_L: \frac{V_L - 1}{1^k} + \frac{V_L - 0}{1000^k} + \frac{V_L - V_o}{1^k} = 0 \Rightarrow V_L \left(\frac{1}{1^k} + \frac{1}{1000^k} + \frac{1}{1^k} \right) - \frac{1}{1^k} = \frac{V_o}{1^k}$$

$$\xrightarrow{(I)} \frac{1}{2} V_o (2.001) - 1 = V_o \Rightarrow 0.0005 V_o = 1 \Rightarrow V_o = \frac{1}{0.0005} = 2000$$

$$A_v = \frac{V_o}{V_s} = \frac{2000}{1^V} = 2000$$