a) rms Load Voltage? 
$$V_{0,rms} = \frac{V_{m}}{\sqrt{2}} \left[ 1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi} \right]^{\frac{1}{2}} = V_{rms} \left[ 1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi} \right]^{\frac{1}{2}}$$

$$I_{rms, scr} = \frac{I_{o,rms}}{\sqrt{2}} = \frac{8.61}{\sqrt{2}} = 6.1 \text{ A}$$

e) 
$$I_{1,rms} \approx 0.84 \left(\frac{480}{50}\right) = 8^{8} \implies THD_{1} = \frac{\sqrt{I_{rms}^{2} - I_{1,rms}^{2}}}{I_{1,rms}} = \frac{\sqrt{(8.61)^{2} - 8^{2}}}{8} = 38 \%$$

=> 154.9 - 240 
$$\sqrt{1-\frac{\alpha}{\pi}+\frac{\sin(2\alpha)}{2\pi}}=0$$
 =>  $\alpha=1.703$  = 97.6°

=> 
$$2.19 - 240\sqrt{1-\frac{\alpha}{\pi}} + \frac{\sin(2\alpha)}{2\pi} = 0$$
 =>  $\alpha = 0.986 = 56.5$ 

$$I_{SCR, rmS} = \frac{I_0}{\sqrt{2}} = \frac{\frac{219}{32}}{\sqrt{2}} = 4.84^A$$
,  $I_{SCR, avg} = \frac{V_m}{z_{RR}} (1+ceg\alpha) = \frac{240\sqrt{2}}{z_{R}(32)} (1+ceg(56.5))$ 

= 2.62 A => Vmax = 240 J2 = 340 V

#5-9 for { S,:ON ; (X, N)

 $V_{O(\omega t)} = V_{m} Sin \omega_{t} ; \quad \alpha \in \mathbb{Z}$   $= V_{m} \left[ \frac{1}{2} - \frac{\alpha}{4\pi} + \frac{Sin(2\alpha)}{8\pi} \right]^{\frac{1}{2}} = \frac{V_{m}}{\sqrt{2}} \left[ 1 - \frac{\alpha}{2\pi} + \frac{Sin(2\alpha)}{4\pi} \right]^{\frac{1}{2}} = \frac{V_{m}}{2} \left[ \frac{1}{2\pi} + \frac{Sin(2\alpha)}{4\pi} \right]^{\frac{1}{2}} = \frac{V_{m}}{2} \leq V_{0,rms} \leq \frac{V_{m}}{\sqrt{2}}$ 

# 5-13 { Z = 15 } Q = 0.646 Rad WZ = 0.754

i(wt):11.3 Sin(wt-0.646) - 1842 1580 0.754 A

X = 115° = 2.01 Rad, B = 3.681 Rad = 211°

Irms: 2.95 A