


بالعربية

امتحان دسجند


9/1/2020

مستين سر اس 3

#1


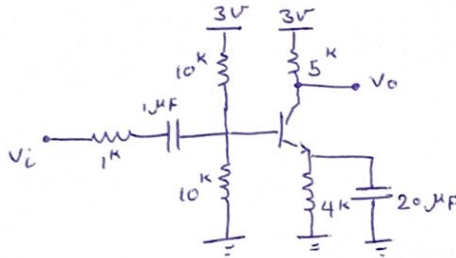


DC Analysis:

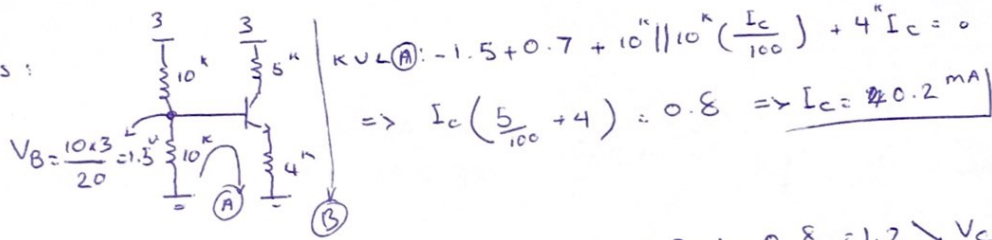

$$\text{KVL in (3): } -3 + 5k(0.2\text{mA}) + V_{CE} + 4k(0.2\text{mA}) = 0 \Rightarrow V_{CE} = 3 - 1 - 0.8 = 1.2 > V_{CE, \text{sat}}$$
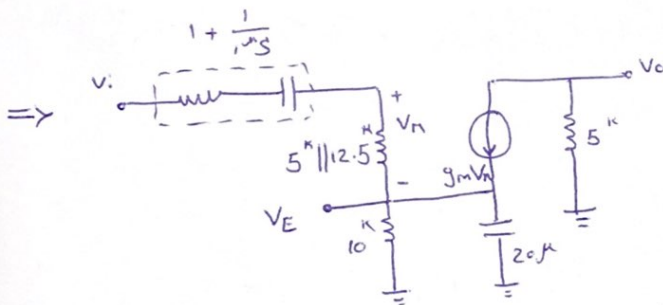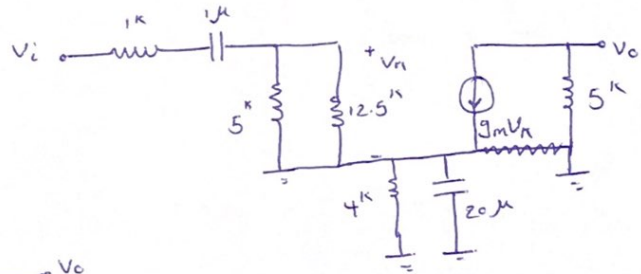
$$\begin{cases} g_m = 40 I_C = 40 \times 0.2 = 8 \text{ mS} \\ r_{\pi} = \frac{100}{8} = 12.5k \end{cases}$$




$$\text{KCL in } V_o: -g_m V_n + \frac{V_o}{5k} = 0 \Rightarrow V_n = \frac{V_o}{8} \Rightarrow V_n = \frac{V_o}{40} \quad (I)$$

$$\text{KCL in } V_E: -g_m \left( \frac{V_o}{40} \right) + 20\mu\text{S}(V_E) + \frac{V_E}{10k} + \frac{V_E}{5k \parallel 12.5k} - \frac{V_o}{40(5k \parallel 12.5k)} = 0$$


$$\Rightarrow V_E \left( 20\mu\text{S} + \frac{1}{10k} + \frac{1}{5k \parallel 12.5k} \right) = V_o \left( \frac{-8}{40} + \frac{1}{40(5k \parallel 12.5k)} \right) \Rightarrow V_E = \frac{-0.193}{0.38k + 20\mu\text{S}} V_o \quad (II)$$

$$\text{KCL in } V_n: \frac{V_n - V_E}{5k \parallel 12.5k} + \frac{V_n - V_i}{1 + \frac{1}{\mu\text{S}}} = 0 \xrightarrow{(I)} 0.007 V_o - \frac{1}{5 \parallel 12.5} \left( \frac{-0.193 V_o}{0.38k + 20\mu\text{S}} \right)$$

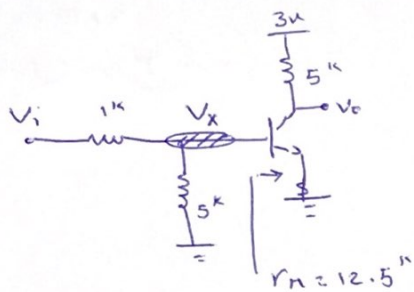
$$+ \frac{1}{1 + \frac{1}{\mu\text{S}}} \left( \frac{V_o}{40} \right) - \frac{V_i}{1 + \frac{1}{\mu\text{S}}} = 0 \Rightarrow \frac{V_o}{V_i}(s) = \frac{(s + 10^6)}{\frac{5 \times 10^{-6} s^3 + 9.55 s^2 + 5700}{(s + 10^6)(20 \times 10^{-6} s + 380)} + 0.007}$$


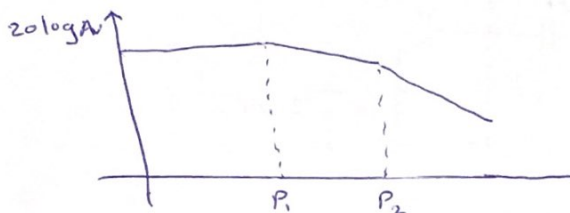
$$A_{v_o} = \frac{V_o}{V_x} \times \frac{V_x}{V_i} = -8(5k) \times \left[ \frac{5k \parallel 12.5k}{(5k \parallel 12.5k) + 5} \right] \approx -16.6$$



#2

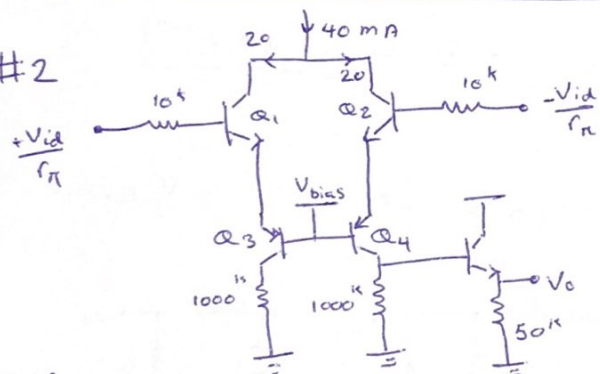

PNP:

$$C_{je} = 2C_{jeo} = 0.6 \text{ PF}$$


$$C_b = g_m \tau_F = 40 \left( \frac{40 \text{ mA}}{2} \right) \times 10^{-15} = 800 \text{ PF}$$

$$C_\pi = C_{je} + C_b = 800.6 \text{ PF}$$

$$C_{jc} = C_\mu = \frac{C_{jco}}{2 \sqrt{1 + \frac{V_{cb}}{V_b}}} = \frac{0.3 \text{ PF}}{\sqrt{1+1}} = 0.21 \text{ PF}$$

~~Q1~~


(a) \$A\_{vdo} = ?\$

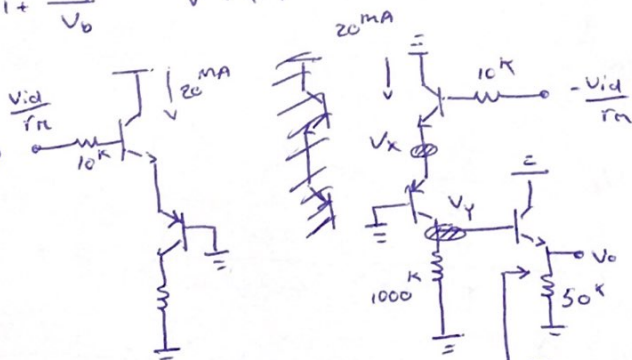

$$A_{vdo} = \frac{V_o}{-V_{id}/r_n} = -r_n \frac{V_o}{V_{id}} = \frac{V_o}{V_Y} \times \frac{V_Y}{V_X} \times \frac{V_X}{-V_{id}/r_n}$$

$$\frac{250}{800} + (250 \times 50k) = 12.5M$$
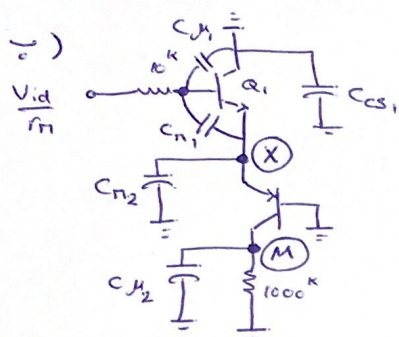
$$A_{vdo} = 0 \quad \text{or} \quad \frac{V_o}{V_Y} = \frac{-R_c}{R_E + r_m} = 0$$




$$x \text{ node: } P_x = \frac{1}{Z_x} = \frac{1}{R_{TH} C_{TH}} = \frac{1}{(C_{n2} + C_{n1}) \left( \frac{r_{m2}}{2} \right)} = \frac{1}{2\pi (8 + 8.6 \text{ pF}) (0.62)}$$

$$\text{in node: } P_{in} = \frac{1}{Z_{in}} = \frac{1}{(10^8 \parallel r_{m1}) (C_{n1} + C_{M1})} = \frac{1}{2\pi [10^8 \parallel 0.3 \times (8 \text{ f})]}$$

$$M \text{ node: } P_M = \frac{1}{Z_M} = \frac{1}{2\pi [2.5 \parallel 1000 \times C_{M2}]} = \frac{1}{2\pi [2.5 \parallel 1000 \times (0.2 \text{ pF})]}$$
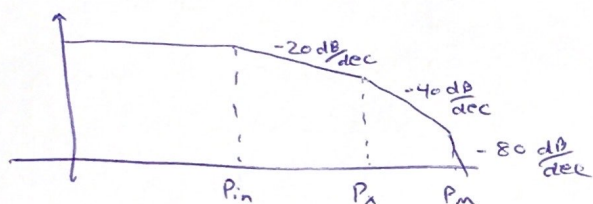
$$A_{vd}(s) = A_{vd0} \times \frac{1}{\left( \frac{s}{P_{in}} + 1 \right) \left( \frac{s}{P_x} + 1 \right) \left( \frac{s}{P_M} + 1 \right)}$$





Hand-drawn schematic of a 10-transistor CMOS circuit. The circuit is powered by  $V_{DD} = 10V$  and  $V_{SS} = -10V$ . It features a  $20\text{ mA}$  current source at the input, a  $1k$  resistor, and a  $50k$  resistor at the output. The circuit includes several PMOS and NMOS transistors labeled  $Q_1$  through  $Q_9$ , with a central biasing network. Inputs are labeled  $in1$  and  $in2$ , and the output is labeled  $v_O$ .

c)  $A_{vdo} = ?$

c) Pole & Zero  $\Rightarrow A_{vd}(s) = ?$

2) bode plot  $\Rightarrow f_{-3dB}, f_u = ?$

n-p-n:  $\beta = 250$ ,  $C_{j0} = 0.3 \text{ pF}$ ,  $C_{cs} = 0.5 \text{ pF}$

$$V_b = 0.8 \text{ V}, \tau_F = 1 \text{ ns}, V_A = 120 \text{ V}$$

PNP:  $\beta = 100$ ,  $C_{jc0} = 0.3 \text{ PF}$ ,  $V_b = 0.8 \text{ V}$



$$\tau_F = 10 \text{ ns}, V_A = 50 \text{ V}$$

الف) for  $Q_9: I_C = 20 \text{ mA} \rightarrow \begin{cases} r_{\pi} = \frac{250}{800} = 312.5 \Omega \\ g_m = 40 I_C = 800 \text{ mmho} \\ r_o = \frac{V_A}{I_C} = 6 \text{ k}\Omega \end{cases}$

for  $Q_7$ :  $I_C = \frac{V_0 + V_{EE}}{50k} = \frac{-9.2 + 10}{50k} = 16 \mu A = 0.016 \text{ mA} \rightarrow \begin{cases} g_m = 0.64 \text{ mho} \\ r_n = \frac{250}{0.64} = 390 \text{ K} \\ r_o = \frac{120}{0.016} = 7500 \text{ K} \end{cases}$

for othe transistors:  $I_C = 10 \text{ mA} \rightarrow \begin{cases} I_m = 400 \text{ mA} \\ r_{\pi PNP} = \frac{100}{400} = 0.25 \text{ K} , r_{\pi NPN} = \frac{250}{400} = 0.62 \text{ K} \\ r_{o PNP} = \frac{50}{10 \text{ mA}} = 50 \text{ K} , r_{o NPN} = \frac{120}{10} = 12 \text{ K} \end{cases}$

→ ac analysis :

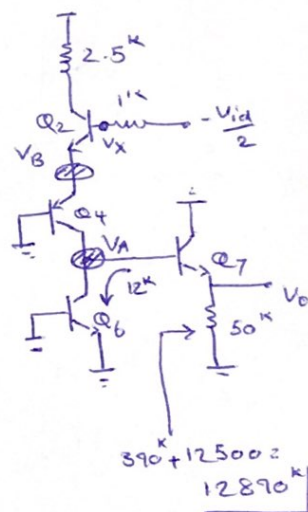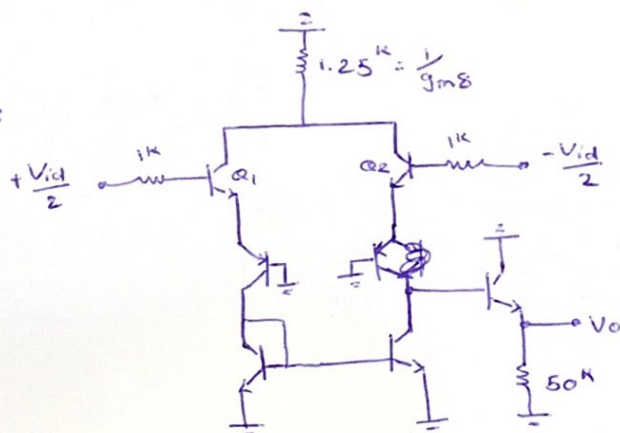


$$-\frac{V_0}{\frac{V_{id}}{2}} = \frac{V_0}{V_A} \times \frac{V_A}{V_B} \times \frac{V_B}{V_K} \times \frac{-V_K}{\frac{V_{id}}{2}} = \left[ \frac{50^K}{50^K + 1.56^K} \right] \times \frac{V_K}{V_{id}}$$



$$\Rightarrow A_{vd} = g_{m_T} \left[ \beta_{NPN} r_{oNPN} \parallel \frac{\beta_{PNP} r_{oPNP}}{2} \right] = 0.64 \left[ \frac{250}{12} \times 50^k \parallel \frac{100 \times 50^k}{2} \right] \approx 0.64 \left( 3000^k \parallel 2500^k \right)$$

$$\Rightarrow A_{vd} = 1363.63 \frac{V}{V}$$

#4

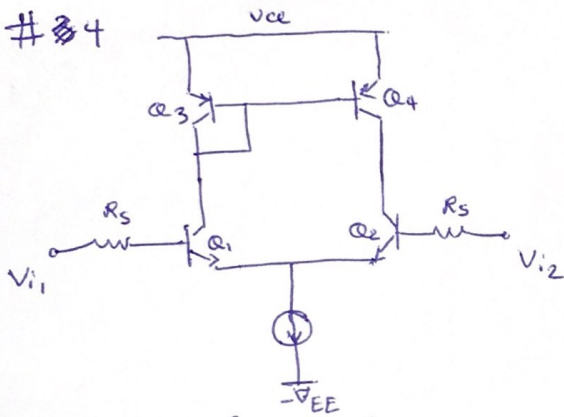

ac circuit

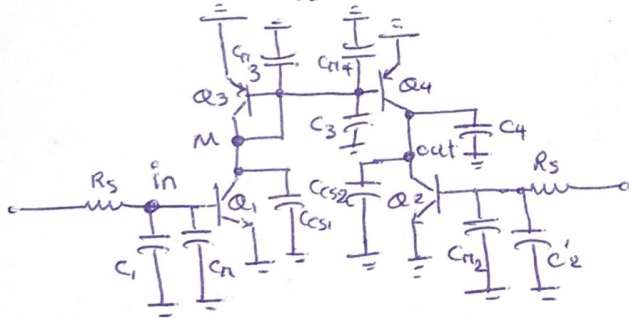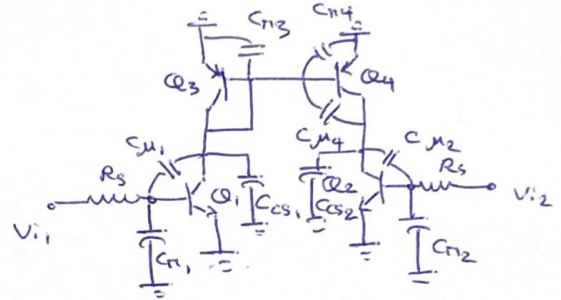

$$P_{in} = \frac{1}{Z_{in}} = \frac{1}{(R_S \parallel r_{n1}) (C_{i1} + C_{n1})}$$

$$P_M = \frac{1}{Z_M} = \frac{1}{(r_{o1} \parallel r_{m3}) (C_{cs1} + C_{n3} + C_{n4} + C_3)}$$

$$P_{out} = \frac{1}{Z_{out}} = \frac{1}{(r_{o4} \parallel r_{o2}) (C_4 + C_{cs2} + C_L)}$$

$$\frac{V_o}{V_{i1}} = \frac{A_{v_o}}{\left(\frac{s}{P_{in}} + 1\right) \left(\frac{s}{P_M} + 1\right) \left(\frac{s}{P_o} + 1\right)}$$

$$\frac{V_o}{V_{i2}} = \frac{-\frac{1}{2} g_m r_o}{\left(\frac{s}{P_{in}} + 1\right) \left(\frac{s}{P_M} + 1\right) \left(\frac{s}{P_o} + 1\right)}$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{V_o}{V_{i1}} + \frac{V_o}{V_{i2}} = \frac{g_m r_o}{A_{v_o}} \cdot \frac{\left(\frac{s}{2P_M} + 1\right)}{\left(\frac{s}{P_{in}} + 1\right) \left(\frac{s}{P_M} + 1\right) \left(\frac{s}{P_o} + 1\right)}$$