
متين گلپايگاني

9174.74

آزمایش ۱

سوال ۲و۳

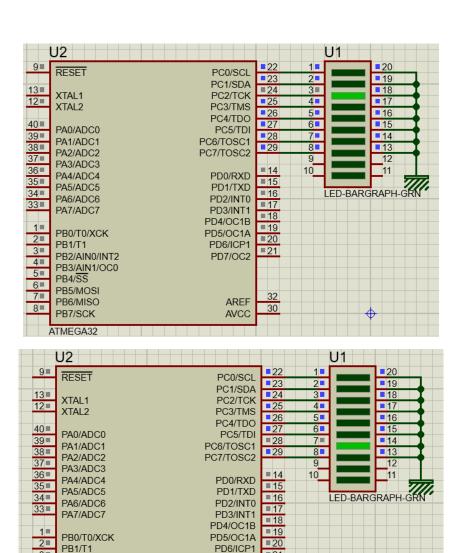

■21

30

×

PD7/OC2

AREF

AVCC

3■

4■

5■

6■

7■

8=

PB2/AIN0/INT2

PB3/AIN1/OC0

PB4/SS

PB5/MOSI

PB6/MISO

PB7/SCK

ATMEGA32

```
46
           //With Loop
47
48 🖨
           for(i=0;i<8;i++){
             PORTC = LED[i];
49
             delay ms(1000);
50
51
           for(i=6;i>=0;i--){
52 白
             PORTC = LED[i];
53
             delay_ms(1000);
54
55
56
57
           //With Shift
58
           for(i=0;i<8;i++){
59 日
             PORTC = 1 << i;
60
             delay_ms(1000);
61
62
63 🖨
           for(i=6;i>=0;i--){
             PORTC = 1 << i;
64
             delay_ms(1000);
65
66
67
```